



**GRT INSITUTE OF
ENGINEERING AND
TECHNOLOGY –TIRUTTANI – 631209**



**Department of Electronics and Communication Engineering
EC8452- ELECTRONIC CIRCUITS II (Regulation 2017)
MULTIPLE CHOICE QUESTIONS**

- 1. A tuned amplifier uses load**
 - a. Resistive
 - b. Capacitive
 - c. LC tank**
 - d. Inductive

- 2. A tuned amplifier is generally operated in operation**
 - a. Class A
 - b. Class C**
 - c. Class B
 - d. None of the above

- 3. At series or parallel resonance, the circuit power factor is**
 - a. 0
 - b. 5
 - c. 1**
 - d. 8

- 4. A resonant circuit contains elements**
 - a. R and L only
 - b. R and C only
 - c. Only R
 - d. L and C**

- 5. At series resonance, voltage across L is voltage across C**

- a. **Equal to but opposite in phase to**
 - b. Equal to but in phase with
 - c. Greater than but in phase with
 - d. Less than but in phase with
6. **To amplify the selective range of frequencies, the resistive load in amplifier is replaced by a**
- a. **Tuned Circuits**
 - b. Inductor
 - c. Transformer
 - d. Capacitor
7. **At parallel resonance, the net reactive component circuit current is**
- a. Capacitive
 - b. **Zero**
 - c. Inductive
 - d. None of the above
8. **For frequencies below resonant frequency, a series LC circuit behaves as a load**
- a. Resistive
 - b. **Capacitive**
 - c. Inductive
 - d. None of the above\
9. **In series resonance, there is**
- a. **Voltage amplification**
 - b. Current amplification
 - c. Both voltage and current amplification
 - d. None of the above
10. **The Q of a tuned circuit refers to the property of**
- a. Sensitivity
 - b. Fidelity
 - c. **Selectivity**
 - d. None of the above
11. **Tuned amplifier is never used in.....**

- a. Radio receiver
- b. Radio transmitter
- c. TV receivers
- d. Public address system**

12. The impedance of an LC parallel resonance circuits becomes

- a. $Z_r = \frac{L}{RC}$**
- b. $Z_r = \frac{LR}{C}$
- c. $Z_r = \frac{LC}{R}$
- d. $Z_r = \frac{RC}{L}$

13. For frequencies below the resonant frequency , a parallel LC circuit behaves as a load

- a. Inductive**
- b. Resistive
- c. Capacitive
- d. None of the above

14. Double tuned circuits are used in stages of a radio receiver

- a. IF**
- b. Audio
- c. Output
- d. None of the above

15. In the double tuned circuit, if the mutual inductance between the two tuned circuits is decreased, the level of resonance curve

- a. Remains the same
- b. Is lowered
- c. Is raised**
- d. None of the above

16. A circuit that removes positive or negative parts of waveform is called

- a. clamper
 - b. clipper**
 - c. diode clamp
 - d. limiter
- 17. What type of diode circuit is used to clip off portions of signal voltages above or below certain levels?**
- a. clipper or limiter**
 - b. clamper
 - c. IC voltage regulator
 - d. none of the above
- 18. Astable multivibrator is _____ in any state.**
- a. Stable
 - b. Unstable**
 - c. Saturated
 - d. Both Stable & Saturated
- 19. Monostable multivibrator can also be termed as _____**
- a. Full astable multivibrator
 - b. Half astable multivibrator**
 - c. Half bistable multivibrator
 - d. Full bistable multivibrator
- 20. Astable circuit acts as a/an _____**
- a. Amplifier
 - b. Oscillator
 - c. Relaxation oscillator**
 - d. Multiplexer
- 21. Bistable circuit is also known as _____**
- a. Latch
 - b. Gate
 - c. Flip-flop**
 - d. Bidirectional circuit
- 22. The monostable multivibrator has one quasi-stable state and one unknown state.**

- a. True
 - b.False**
- 23. Astable multivibrator cannot be used for frequency division.**
- a.True
 - b.False**
- 24. How many stable states in Monostable multivibrator**
- a.One stable state**
 - b.Two stable state
 - c.Three stable state
 - d.No stable state
- 25. How many stable states in Bistable multivibrator**
- a.One stable state
 - b.Two stable state**
 - c.Three stable state
 - d.No stable state
- 26. What is the duty cycle of the output of an astable multivibrator?**
- a. 50%**
 - b. 75%
 - c. 55%
 - d. 100%
- 27. Monostable multivibrator is also referred to as**
- a. One shot**
 - b. Two shot
 - c. Three shot
 - d. Four shot
- 28. A multivibrator is an electronic circuit used to implement.....**
- a. Oscillator
 - b. Timer
 - c. Flip flop**
 - d. All the mentioned
- 29. If you need to design a relaxation oscillator circuits, the most likely device used is**
- a. BJT

- b. UJT
- c. TRIAC
- d. SCR

30. Capacitor discharge interval in monostable multivibrator

- a. Recovery time**
- b. Refresh time
- c. Dynamic time
- d. Static time

1. A tuned amplifier has its maximum gain at a frequency of 2MHz and has a bandwidth of 50KHz.calculate the quality factor.

- a. 40**
- b. 100
- c. 25
- d. 2500

2. The Q of a tuned amplifier is 50. If the resonant frequency for the amplifier is 1000kHz, then bandwidth is

- a. 10kHz
- b. 40 kHz
- c. 30 kHz
- d. 20 kHz**

3. In double tuned circuits two tuned circuits are connected by

- a. Series
- b. Parallel
- c. Mutual coupling**
- d. None of these

4. The bandwidth for double tuned amplifier is 20KHZ.calculate the bandwidth if such three stages are cascaded.

- a. 22KHz
- b. 14.28KHz**
- c. 24.25KHz
- d. 20KHz

5. A tuned circuits has resonant frequency of 1600KHz and a bandwidth of 10KHz.What is the value of its q factor?

- a. 16
- b. 160**

- c. 16000
d. 1600
6. **At parallel resonance, the phase angle between the applied voltage and circuit current is**
- 90°
 - 180°
 - 0°**
 - None of the above
7. **The Q of an LC circuit is given by**
- $2\pi f_r \times R$
 - $R / 2\pi f_r L$
 - $2\pi f_r L / R$**
 - $R^2 / 2\pi f_r L$
8. **Consider the following statements: A clamper circuit**
- adds or subtracts a dc voltage to a waveform**
 - does not change the waveform**
 - amplifies the waveform**
- Which are correct?**
- 1, 2**
 - 1, 3
 - 1, 2, 3
 - 2, 3
9. **What is the expression for time period of waveform produced by monostable multivibrator**
- $T = 0.69(R_1 C_1 + R_2 C_2)$
 - $T = 0.69(R_1 C_1 R_2 C_2)$
 - $T = 1.38(R_1 C_1 + R_2 C_2)$
 - $T = 0.69RC$**
10. **Which of these statements are true?**
- Astable multivibrator can be used for generating square waves**
 - Bistable multivibrator can be used for storing binary information**
- 1

- b. 2
 - c. 1&2**
 - d. None
- 11. Which among the below mentioned oscillators does not adopt any kind of feedback mechanism?**
- a. Wein bridge oscillator
 - b. UJT relaxation oscillator**
 - c. Phase shift oscillator
 - d. All the mentioned
- 12. A RC low pass circuit has $R=1.5\text{Kohm}$ and $C=0.2\mu\text{f}$. what is the rise time of the output when excited by a step input?**
- a. $0.3\mu\text{s}$
 - b. $3\mu\text{s}$
 - c. 0.66ms**
 - d. 6.6ms
- 13. What is the condition at which low pass filter acts as an integrator?**
- a. Time constant $\ll T$
 - b. Time constant $\ll T$**
 - c. Time constant $=T$
 - d. Both Time constant $\ll T$ & Time constant $\ll T$
- 14. What is the time constant of RC circuits?**
- a. $\tau=RC$**
 - b. $\tau=1/RC$
 - c. $\tau=R/C$
 - d. $\tau=C/R$
- 15. Multivibrator which can produce very short pulse or much longer rectangular shaped waveform whose leading edge rises in time with an externally applied triggered pulse is.....**

- a. Astable multivibrator
- b. Monostable multivibrator**
- c. Bistable multivibrator
- d. Schmitt trigger