

(1)

IC 8433 - Linear Integrated Circuits  
Unit 1: Basics of Operational Amplifiers

1) Constant Current Source [Current mirror].

• Constant current source makes use of the fact that transistor in active mode of operation,  $V_C$  is independent of  $I_C$ .

Ckt. → Transistor  $Q_1$  &  $Q_2$  are matched [ $\therefore$  fabricated using IC technology]

→ Base and Emitter of  $Q_1$  &  $Q_2$  are tied together so

→  $Q_1$  is connected as diode by shorting collector & base

 


Fig. Basic BJT Current mirror

The collector current flows through diode connected  $Q_1$ , so establishes voltage across  $Q_1$ . This voltage appears below  $B$  &  $E$  of  $Q_2$ . ( $Q_2$  identical to  $Q_1$ )

$$\beta_E(Q_2) = \beta_E(Q_1) \approx \beta_{ref}$$

As long as  $Q_1$  is maintained in active region

$$I_{C2} = I_o \approx I_{ref}$$

Since  $I_o$  (output current) is reflection (or) mirror of the reference current  $I_{ref}$ . The circuit is referred to as "current mirror".

Mirror effect valid only for large value of  $\beta$

Effect of  $\beta$  on the operation of the current mirror  $\Delta$   
Analysis

Collector currents of  $\text{Q}_1$  &  $\text{Q}_2$  :  $I_{C_1}$  and  $I_{C_2}$

$$I_{C_1} \approx \alpha_F I_{F_S} e^{V_{BE_1}/V_T} - G$$

$$I_{C_2} \approx \alpha_F I_{F_S} e^{V_{BE_2}/V_T} - G$$

From ① & ②

$$\frac{I_{C_2}}{I_{C_1}} = \frac{(\alpha_F I_{F_S}) e^{V_{BE_2}/V_T}}{(\alpha_F I_{F_S}) e^{V_{BE_1}/V_T}}$$

$$= \frac{e^{V_{BE_2}/V_T}}{e^{V_{BE_1}/V_T}} \Rightarrow e^{V_{BE_2}/V_T} \cdot e^{-V_{BE_1}/V_T}$$

$$\therefore \frac{I_{C_2}}{I_{C_1}} = e^{(V_{BE_2} - V_{BE_1})/V_T} - ③$$

$$\therefore V_{BE_2} = V_{BE_1}$$

$$\Rightarrow I_{C_2} = I_{C_1} = I_C = I_0$$

Since  $\text{Q}_1$  &  $\text{Q}_2$  are identical.

$$\boxed{\beta_1 = \beta_2 = \beta}$$

Applying KCL at collector of  $\text{Q}_1$ ,

$$\Rightarrow I_{ref} = I_{C_1} + I_{B_1} + I_{B_2} - ④$$

$$= I_{C_1} + \frac{I_{C_1}}{\beta_1} + \frac{I_{C_2}}{\beta_2} \quad [ \because \beta I_{B_1} = I_{C_1}, \\ I_{C_2} = I_{C_1} - I_C ]$$

$$= I_C + \frac{I_C}{\beta} + \frac{I_C}{\beta}$$

$$I_{ref} = I_C + \frac{2I_C}{\beta} = I_C \left[ 1 + \frac{2}{\beta} \right] - ⑤$$

$$\text{Solving } ④ \quad I_C = \left[ \frac{\beta}{\beta + 2} \right] I_{ref} - ⑥$$

From fig 4ref is,  $I_{ref} = \frac{V_{CC} - V_{BE}}{R_1} = \frac{V_{CC}}{R_1}$  [  $V_{BE} = 0.7V$  (assumed) ] (6)

From (6), if  $\beta > 1$ ,  $\beta(\beta+2)$  is unity and  $I_o = I_{ref}$  which for a given  $R_1$  is constant.

\* Current transfer ratio other than unity by controlling area of the emitter-base junction [EBJ] of  $\text{Q}_2$

Ex : EBJ of  $\text{Q}_2$  = 4 times than of  $\text{Q}_1$ ,

$$I_o = 4 I_{ref}$$

Output resistance of current source is the o/p resistance  $r_o$  of  $\text{Q}_2$

$$r_o = r_{o2} = \frac{V_A}{I_o} \approx \frac{V_A}{I_{ref}}$$

$V_A$  = early voltage

 


fig. volt - Ampere characteristics for  $\text{Q}_2$

Graph:  $V_{CE_2} < 0.3V \Rightarrow \text{Q}_2$  is saturated

for  $V_{CE_2} > 0.3V$ , transistor operates in active region

$I_{C_2}$  is essentially constant

Slight increase in  $I_{C_2}$  due to early effect.

For practical purpose, early voltage assumed infinite

$r_o \rightarrow \infty$  and  $I_{C_2}$  is constant.

## 1.2 WIDLAR CURRENT SOURCE

Cp Amp requires very small collector current

Basic current mirror circuit has a limitation:-

→ <sup>when</sup> low value current source is needed, value of  $R_i$  is high and can't be fabricated

Hence we go for Widlar current source. It is designed for current values of very low magnitude

Construction:-

 


fig Widlar Current Source

In this circuit  $R_E$  is added to output transistor  $Q_2$  this makes  $V_{BE1} > V_{BE2}$

Analysis: Due to  $R_E$ ,  $V_{BE2} < V_{BE1}$ . So,  $I_o \ll I_c$ .

$$I_{C1} = \alpha I_{ES} e^{V_{BE1}/V_T} \rightarrow ①$$

$$I_{C2} = \alpha I_{ES} e^{V_{BE2}/V_T} \rightarrow ②$$

Equating ① & ②

$$\frac{I_{C1}}{I_{C2}} = e^{(V_{BE1} - V_{BE2})/V_T} \rightarrow ③$$

Taking natural logarithm on both sides,

$$\ln \frac{I_{C1}}{I_{C2}} = \frac{V_{BE1} - V_{BE2}}{V_T}$$

$$\rightarrow ④$$

$$V_{BE1} - V_{BE2} = V_T \ln \left[ \frac{I_{C1}}{I_{C2}} \right]$$


Writing KVL for emitter-base loop of  $\text{Q}_2$

$$V_{BE1} = V_{BE2} + (I_{B2} + I_{C2}) R_E$$

$$V_{BE1} - V_{BE2} = (I_{B2} + I_{C2}) R_E \rightarrow ⑤$$

$$= \left[ \frac{I_{C2}}{\beta} + I_{C2} \right] R_E \quad (\because I_B \beta = I_C)$$
 
$$= \left( \frac{1}{\beta} + 1 \right) I_{C2} R_E \rightarrow ⑥$$



From ④ & ⑥

$$V_T \ln \left( \frac{I_{C1}}{I_{C2}} \right) = \left( \frac{1}{\beta} + 1 \right) I_{C2} R_E$$

$$\therefore R_E = \frac{V_T}{\left( 1 + \frac{1}{\beta} \right) I_{C2}} \ln \left( \frac{I_{C1}}{I_{C2}} \right) \rightarrow ⑦$$

Relationship between  $I_{C1}$  &  $I_{ref}$  is obtained by KCL at collector point of  $\text{Q}_1$  (node 'a')

$$I_{ref} = I_{C1} + I_{B1} + I_{B2} \rightarrow ⑧$$

$$= I_{C1} + \frac{I_{C1}}{\beta} + \frac{I_{C2}}{\beta} \quad (\because I_B \beta = I_C)$$

$$= I_{C1} \left[ 1 + \frac{1}{\beta} \right] + \frac{I_{C2}}{\beta} \rightarrow ⑨$$

For identical transistors, assume  $\beta_2 = \beta_1 = \beta$

In Widlar current source,  $I_{C2} \ll I_{C1}$

$\therefore I_{C2}/\beta$  is neglected in eqn ⑨


$$\Rightarrow I_{ref} \approx I_{C1} \left[ 1 + \frac{1}{\beta} \right]$$

$$I_{C1} = \frac{\beta}{\beta+1} I_{ref}$$

$$\text{where, } I_{ref} = \frac{V_{cc} - V_{BE}}{R_i}$$

$$\text{for } \beta \gg 1, I_{C1} \approx I_{ref}$$

### 1.1.3 Wilson Current Source:

 

#### Construction:-

- It is a 3 terminal ckt that accepts an input current of the input terminal and provides mirror current source.
- A mirror current is a copy of input current.
- The main feature of Wilson current source is to provide high output resistances with respective high input resistances.
- High output resistance is achieved due to negative feedback through  $Q_2$ .

#### Analysis:-

From fig.,  $V_{BE1} = V_{BE2}$ ,  $I_{C1} = I_{C2}$  &  $I_{B1} = I_{B2} = I_B$

Apply KCL at node 'B',  $I_{E3} = I_{C2} + I_{B2} + I_{B1}$

$$\begin{aligned} I_{E3} &= I_{C2} + 2I_{B2} \quad (\because I_{B1} = I_{B2}) \\ &= I_{C2} + 2 \frac{I_{C2}}{\beta} \\ &= I_{C2} \left[ 1 + \frac{2}{\beta} \right] \rightarrow \textcircled{1} \end{aligned}$$

From fig., through  $Q_3$

$$\begin{aligned} I_{E3} &= I_{B3} + I_{C3} \quad (\because I_E = I_B + I_C) \\ &= \frac{I_{C3}}{\beta} + I_{C3} \\ &= I_{C3} \left[ \frac{1}{\beta} + 1 \right] \rightarrow \textcircled{2} \end{aligned}$$

From  $\textcircled{1}$  &  $\textcircled{2}$ ,

$$\begin{aligned} I_{C2} \left[ \frac{\beta+2}{\beta} \right] &= I_{C3} \left[ \frac{\beta+1}{\beta} \right] \\ I_{C2} &= I_{C3} \left[ \frac{\beta+2/\beta}{\beta} \right] = I_{C2} \left[ \frac{\beta+2}{1+\beta} \right] \end{aligned}$$

(4)

$I_{C_3}$  is o/p current  $I_o$ ,  $I_{C_2} = I_{C_1}$ , so  $I_C$ ,

$$I_o = I_{C_1} \left( \frac{\beta+2}{1+\beta} \right)$$

At node 'a': (apply KCL)

$$\begin{aligned} I_{ref} &= I_{C_1} + I_{B3} \\ &= I_o \left[ \frac{\beta+1}{\beta+2} \right] + \frac{I_{C_3}}{\beta} \end{aligned}$$

from  $I_{C_3} = I_o$

$$\begin{aligned} I_{ref} &= I_o \left[ \frac{\beta+1}{\beta+2} + \frac{1}{\beta} \right] \\ &= I_o \left[ \frac{\beta(\beta+1) + \beta^2 + 2}{\beta(\beta+2)} \right] \\ I_{ref} &= I_o \left[ \frac{\beta^2 + 2\beta + 2}{\beta^2 + 2\beta} \right] \end{aligned}$$

To find resistance, sub  $I_{ref} = \frac{V_{CC} - 2V_{BE}}{R_L}$

$$\Rightarrow \frac{V_{CC} - 2V_{BE}}{R_L} = I_o \left[ \frac{\beta^2 + 2\beta + 2}{\beta^2 + 2\beta} \right]$$

/  $R_L$  if

$$\text{The difference, } I_o - I_{ref} = \frac{2}{\beta^2 + 2\beta + 2} I_{ref}$$

### 1.2 Current Source as Active loads:


- Current Source can be used as an active load in both analog & digital ICs
- The active load realized using "current source" in place of passive load (i.e. resistor) in the collector arm of differential amplifier makes it possible to achieve high voltage gain without requiring large power supply voltage
- Active load so achieved is basically " $\pi_o$ " of a PNP transistor

### 1.3 Voltage Sources

- Voltage source is a circuit that produces an output voltage  $V_o$ , which is independent of the load driven by the voltage source / output current supplied to the load.
- Voltage source circuit = dual of constant current source
- Application: require voltage reference point with low AC impedance, stable DC voltage not affected by power supply
- Two methods to produce voltage source
  - using the impedance transforming properties of transistor, determines current gain of transistor
  - using an amplifier with negative feedback
 
#### 1.3.1. Voltage Source circuit using Impedance transformation:

- Voltage source circuit using impedance transforming property of transistor is shown.



- Voltage source  $V_s$  derives the base of the transistor through series resistance  $R_s$  and output is taken across the emitter
- From ckt, output AC resistance looking into emitter given by

$$\frac{dV_o}{dI_o} = R_o = \frac{R_s}{\beta + 1} + g_{le} \rightarrow ①$$

with values as high as 100 for  $\beta$

$$R_s = \frac{R_o}{\beta + 1}$$

- Equation is "applicable only for small changes" in the e/P current

- The load regulation parameter indicates the changes in  $V_o$  resulting from large changes in o/p current  $I_o$  (b)
- Reduction in  $V_o$  occurs as  $I_o$  goes from no-load current to full-load current. This determines o/p independence of voltage sources


### 1.3.2 Emitter follower / common collector type voltage source

- It is suitable for differential gain stage used in op-amp. It has a advantage of
  - producing low AC impedance
  - resulting in effective decoupling of adjacent gain stages
- Low o/p impedance of the common collector stage simulates a low impedance voltage source with an o/p voltage level of  $V_o$ .

$$V_o = V_{CC} \left[ \frac{\alpha_2}{R_1 + R_2} \right]$$

- Diode 'D,' used for offsetting the effect of dc value  $V_{BE}$  and compensating temperature dependance of  $V_{BE}$  drop of  $\alpha_1$ .  
 $X_L$  = dotted line shows ckt is biased by current through  $\alpha_1$ .
- Impedance  $R_o$  looking at emitter of  $\alpha_1$ , derived from hybrid  $\pi$  model
 
$$R_o = \frac{V_T}{I_1} + \frac{R_1 R_2}{\beta R_1 + R_2} C$$



Voltage source Temperature compensated avalanche diode

$$V_o = V_B + V_{BE}$$

The o/p resistance  $R_o$  is given as

$$R_o = R_B + \frac{V_T}{I_1}$$

Voltage source using  $V_{BE}$  as reference)

$$V_o = I_2 (R_1 + R_2) = \frac{V_{BE}}{R_2} (R_1 + R_2) = V_{BE} \left( \frac{R_1}{R_2} + 1 \right)$$

The ac o/p resistance  $R_o$  is


$$R_o = \frac{dV_o}{dI_o} = \frac{R_1 + R_2}{1 + g_m R_2}$$

(6)
 
#### 1.4 VOLTAGE REFERENCES

- The ckt that is primarily designed for providing constant voltage independent of changes in temperature is called "Voltage reference".
  - Important characteristics of voltage reference is Temperature Co-efficient of o/p reference voltage, TCR
- $$TCR = \frac{dVR}{dT}$$
- Desirable properties of VR are
    - Reference voltage must be independent of temperature change
    - Reference voltage must have good power supply rejection which is independent of supply voltage as possible.
    - O/p voltage must be as independent of the loading of o/p current.

(\*) Voltage ref. ckt using Temperature compensation scheme:-



Voltage ref. ckt using basic temperature compensation is shown above. Constant current 'I' is supplied to avalanche diode  $D_3$  to provide bias voltage  $V_B$  to base of  $Q_1$ .

Apply KCL at node 'N'

$$\frac{V_B - V_{BE}(Q_1) - V_{BE}(D_1) - V_R}{R_1} = \frac{V_R - V_{BE}(D_2)}{R_2}$$

Assume hatched resistor transistors,

$$V_{BE}(Q_1) = V_{BE}(D_1) = V_{BE}(D_2) = V_{BE}$$

Then,  $V_B$ :

$$\frac{V_B - 2V_{BE} - V_R}{R_1} = \frac{V_R - V_{BE}}{R_2}$$

$$\therefore V_R = \frac{R_2 V_B + V_{BE} (R_1 - 2R_2)}{R_1 + R_2}$$

Differen'tiating  $V_B$  &  $V_{BE}$  partially w.r.t. temperature

$$0 = \frac{R_2}{R_1 + R_2} \frac{\partial V_B}{\partial T} + \left[ \frac{(R_1 - 2R_2)}{R_1 + R_2} \right] \frac{\partial V_{BE}}{\partial T}$$

$$\frac{2R_2 - R_1}{R_2} = \frac{\partial V_B / \partial T}{\partial V_{BE} / \partial T}$$

To be satisfied for obtaining zero temperature co-efficient

Apply KCL at node 'N'

~~$$\frac{V_B - V_{BE}(Q_1) - V_{BE}(D_1) - V_R}{R_1} = \frac{V_R - V_{BE}(D_2)}{R_2}$$~~

Assume hatched transistors,

~~$$V_{BE}(Q_1) = V_{BE}(D_1) = V_{BE}(D_2) = V_{BF}$$~~

~~$$\text{Then, } V_B : \frac{V_B - 2V_{BE} - V_R}{R_1} = \frac{V_R - V_{BE}}{R_2}$$~~

~~$$V_R = \frac{R_2 V_B + V_{BE} (R_1 - 2R_2)}{R_1 + R_2}$$~~

Diff  $V_B$  &  $V_{BE}$  partially w.r.t. temperature

## (1.5) BJT DIFFERENTIAL AMPLIFIER WITH ACTIVE LOADS

(7)

### 1.5.1: Differential amp with active loads.

- Diff Amp are designed with active loads to increase differential mode voltage gain
- Open ckt voltage gain of an op-amp is needed to be as large as possible which is achieved by cascading gain stages which increases phase shift and amp also becomes vulnerable to oscillations.
- Gain is fed by large value of collector resistance

$$\text{Voltage gain, } A_{dm} = -g_m R_c = -\frac{T_c R_c}{V_T} \rightarrow (1)$$

- To increase the gain the  $T_c R_c$  must be very large.
- Limitations in  $T_c$  fabrication:

- large value of resistance needs a large chip area
- for large  $R_c$ , quiescent drop across resistor increases and large power supply will be required to maintain operating current.
- Large monolithic resistor introduces large parasitic capacitances which limits the frequency response of amplifier.
- For linear operation of differential pair, device should not be allowed to enter into saturation.

For these reasons we prefer active loads in differential amplifier.

### 1.5.2 BJT differential amplifiers using active loads:


- Simple active load ckt for a differential amp. is current mirror active loads.
- Active loads comprise of transistors  $\Phi_3$  &  $\Phi_4$  with transistor  $\Phi_3$  connected as a diode with base-collector terminal.
- Ckt drives load resistor  $R_L$
- An AC op voltage is applied to differential amplifier

Various currents of ckt are

$$I_A = I_{\Phi_3} = I_{C1} = \frac{g_m V_{id}}{2} \rightarrow (2)$$

where,  $I_{C_4} = I_{C_3}$  (due to current mirror)
 
$$I_{C_2} = -\frac{g_m V_{id}}{2} \rightarrow (3)$$



- Load current  $I_L$  entering next stage is,

$$I_L = I_{C_2} + I_{C_4} \rightarrow (4)$$

$$\therefore I_L = -\frac{(g_m V_{id})}{2} - \frac{(g_m V_{id})}{2} = -g_m V_{id} \rightarrow (5)$$

- O/P voltage,  $V_o = -I_L R_L \rightarrow (6)$

$$= -(-g_m V_{id}) R_L$$

$$= g_m V_{id} R_L \rightarrow (7)$$

A.C voltage gain of ckt

$$A_V = \frac{V_o}{V_{id}} = \frac{g_m R_L V_{id}}{V_{id}} = g_m R_L \rightarrow (8)$$

- Differential amplifier can amplify differential i/p signals and it provides single-ended o/p with a ground reference. Since  $R_L$  is connected to only one o/p terminal
- This is made use of current mirror active loads.
- O/P resistance  $R_o$  of ckt offered by parallel combination of  $\alpha_2$  (NPN) &  $\alpha_4$  (PNP)

$$\cdot R_o = r_{o2} || r_{o4} \rightarrow (9)$$

## Analysis of BJT differential amplifier with active loads

- Assume,  $\frac{V_{id}}{2} = 0$ , for  $\alpha_1 \approx \alpha_2 \approx \beta = \infty$
- Bias current is divided equally b/w  $\alpha_1$  &  $\alpha_2$   
 $\therefore I_{C1} = I_{C2} = I_{EE}/2 \rightarrow (1)$
- $I_{C1}$  supplied by  $\alpha_3$  is mirrored as  $I_{C4}$  at o/p of transistor  $\alpha_4$ .  
 $\therefore I_{C3} = I_{C4} = I_{EE}/2$  & dc current in collector of  $\alpha_4$  is exactly the current needed to satisfy  $\alpha_2$ .
- When  $\beta$  is very large,  $V_{EC4} = V_{EC3} = V_{BE}$ , the current mirror ratio becomes exactly unity.
- Differential amplifier is completely balanced, o/p voltage

$$V_o = V_{CC} - V_{BE} \rightarrow (2)$$

Q-point :

- The collector currents of all transistors are equal i.e.  $I_{C1} = I_{C2} = I_{C3} = I_{C4} = \frac{I_{EE}}{2} \rightarrow (3)$
- Collector-Emitter voltage of  $\alpha_1$  &  $\alpha_2$  are given by  
 $V_{CE1} = V_{CE2} = V_C - V_E$   
 $= (V_{CC} - V_{EB}) - (-V_{EB}) \approx V_{CC} \rightarrow (4)$
- Collector-Emitter voltage of  $\alpha_3$  &  $\alpha_4$   
 $V_{CE3} = V_{CE4} = V_{EB} \rightarrow (5)$
- O/P offset voltage  $V_{os}$  of differential amplifier arise from mismatch in i/p device  $\alpha_1$  &  $\alpha_2$ , load devices  $\alpha_3$ ,  $\alpha_4$  from base currents of load devices.

$$V_{os} \approx V_T \left[ \frac{\Delta I_{SP}}{I_{SP}} - \frac{\Delta I_{SN}}{I_{SN}} + \frac{2}{\beta} \right] \rightarrow (6)$$

- where ' $\beta$ ' represents the gain of PNP transistor

$$\Delta I_{SP} = I_{S3} - I_{S4} \rightarrow (7)$$

$$I_{SP} = \frac{I_{S3} + I_{S4}}{2} \rightarrow (8)$$

$$\Delta I_{SN} = I_{S1} - I_{S2} \rightarrow (9)$$

$$I_{SN} = \frac{I_{S1} + I_{S2}}{2} \rightarrow (10)$$

Assume 'a' worst case value,  $\pm 4\%$ , for  $\frac{\Delta T_s}{T_s}$  &  $\beta = 20$

$$V_{OS} = V_T (0.04 + 0.04 + 0.1)$$

$$= 2.6 \times 10^{-3} \times 0.18 \approx 4.68 \text{ mV} \quad (2)$$

Eqn (2) shows offset is higher than that of a resistive loaded differential amplifier. This is reduced by use of emitter resistors for  $Q_3$  &  $Q_4$  &  $Q_5$  in current mirror load


 


fig. Improved differential ckt using active load
 
## 1.6 BASIC INFORMATION ABOUT OP-AMPS:

Circuit symbol:

- ckt schematic of an op-amp is a triangle



offset null	
Inverting	1 8 NC
	2 7 V+
non-inverting	3 6 O/P
	4 5 offset null

- It has 2 i/p terminals & one o/p
- Terminal with '-' sign is called "inverting i/p terminal"
- Terminal with '+' sign is called "non-inverting i/p terminal."

Packages: 3 popular packages available

- Metal can (TO) package
- Dual in-line package (DIP)
- flat package or flat pack



(9)

## Op Amp Terminals

- 5 basic terminals : 2 i/p terminals
- 1 o/p terminal
- 2 power supply terminals
  
## Power Supply Connections

- $V^+$  &  $V^-$  power supply terminals connected to 2 dc voltage source
- $V^+$   $\rightarrow$  connected to positive terminal of one source
- $V^{pin}$   $\rightarrow$  " " negative "




Power Supply range :  $\pm 5V$  to  $\pm 22V$

- Common point of 2 supplies must be grounded, twice supply voltage will get applied & damage the op-amp

## (1.7) IDEAL OPERATIONAL AMPLIFIER:

- Schematic symbol of op-amp

 

- It has 2 i/p terminals & one o/p terminal

- '-' & '+' refers to inverting & non-inverting i/p terminal

i.e.  $V_1 = 0$ ,  $V_o = 180^\circ$  out of phase with i/p  $V_2$

$V_2 = 0$ ,  $V_o = \text{inphase with i/p } V_1$

- Op-amp is said to be ideal if it has following characteristics

$\rightarrow$  open loop voltage gain,  $A_{OL} = \infty$

$R_i = \infty$

$R_o = 0$

$\rightarrow$  Bandwidth  $BWL = \infty$

$\rightarrow$  zero offset,  $V_o = 0$ , when  $V_1 = V_2 = 0$

 
 


fig. open loop ckt

fig. Equivalent ckt of an Op Amp

- An ideal op-amp draws no current at both i/p terminals i.e.  $i_1 = i_2 = 0$  ( $\because$  infinite i/p impedance)
- Since gain is  $\infty$ , voltage between inverting & non-inverting terminals i.e. differential i/p voltage  $V_d = V_1 - V_2$  is zero for finite o/p voltage  $V_o$
- The o/p voltage  $V_o$  is independent of current drawn from o/p as  $R_o = 0$ .  
But these op-amp can't be realized in practice  
From equivalent ckt,  $A_{ol} \neq \infty$ ,  $R_i \neq \infty$ ,  $R_o \neq 0$   
 $\therefore$  op-amp is voltage controlled voltage source,  $A_{ol}$  &  $V_d$  are equivalent. Thevenin voltage source &  $R_o$  is Thevenin's equivalent resistance looking back into o/p terminal

$$\begin{aligned}\therefore \text{o/p voltage, } V_o &= A_{ol} V_d \\ &= A_{ol} (V_1 - V_2)\end{aligned}$$

### Open loop operation of Op-Amp.


- The simplest way to use op-amp is in open loop model
- $V_1$  &  $V_2$  are applied at non-inverting & inverting terminal since gain is infinite.  $V_o = +V_{sat}$  or  $-V_{sat}$  as  $V_1 > V_2$  or  $V_2 > V_1$
- o/p assumes one of 2 possible states  $+V_{sat}$  /  $-V_{sat}$   
i amplifier act as switch

(10)

## Feedback in Ideal op-Amp.:

- Utility is improved by providing negative feedback. O/P is not driven into saturation & ckt behaves in linear manner
- Two important negative feedback circuits are
  - current drawn by either of the i/p terminals (inverting/non-inverting) is negligible.
  - The differential i/p voltage  $V_d$  b/w non-inverting & inverting i/p terminals is zero

### Inverting Amplifier:

 

- O/P voltage  $V_o$  is fed back to inverting i/p terminal through  $R_f = R$ , n/w where  $R_f$  is feedback resistor
- I/P signal  $V_i$  (AC/DC) is applied to inverting i/p terminal through  $R_i$  & non-inverting terminal is grounded

Analysis: Assume ideal op-amp

$$V_d = 0, \text{ at node 'a' which is at ground potential} \& \text{ current } i_i \text{ through } R_i \text{ is } i_i = V_i / R_i \rightarrow ①$$

- Op-amp draws no current, all current flowing through  $R_i$  must flow through  $R_f$

$$V_o = IR$$

$$\Rightarrow V_o = -i_i R_f = -V_i \frac{R_f}{R_i} \rightarrow ②$$

Gain of inverting amplifier,

$$A_{CL} = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

Nodal equation at node 'a':  $\frac{V_a - V_i}{R_i} = -\frac{(V_a - V_o)}{R_f}$

$$\frac{V_a - V_i}{R_i} + \frac{V_a - V_o}{R_f} = 0$$


- \* Output stage is designed to provide low output impedance
- \* Output voltage should swing symmetrically with respect to ground
- \* Power supply  $\pm 15V$ .

### DC CHARACTERISTICS :-

- \* Ideal op-amp draws no current from source and also independent of temperature.
- \* But in practical op-amp current is drawn and two inputs responds differently to current and voltage due to mismatch in transistors. e.g. temperature is dependent shifts in operation.
  - ↳ Input bias current
  - ↳ Input offset current
  - ↳ Input offset voltage
  - ↳ Thermal drift.
 
### INPUT BIAS CURRENT :-

- \* Op-amp input is differential amplifier made of BJT FET.
- \* Input transistors must be biased into their linear region by supplying current into bases by external circuit.
- \* In ideal op-amp, Assumption: no current is drawn from input terminal.
- \* Practically, input terminal conduct small value of dc current to bias the input transistors.
- \* Base current entering inverting & non-inverting terminal  $I_B^-$  &  $I_B^+$



- \* Even though both transistors are identical,  $I_B^- \neq I_B^+$  due to internal imbalance between two inputs

(11)

∴ For non-inverting amplifier the voltage gain

$$A_{CL} = \frac{V_o}{V_i} = 1 + \frac{R_f}{R_i}$$


- The gain can be adjusted to unity/more by proper selection of resistor  $R_f$  and  $R_i$ .
- Compared to inverting amplifier, input resistance of non-inverting amplifier is large.

### Voltage follower:

- In non-inverting amplifier if  $R_f = 0$  &  $R_i = \infty$ , we get following fig. i.e. voltage follower

$$A_{CL} = \frac{V_o}{V_i}$$

$$V_o = V_i$$

 


i.e. o/p voltage is equal to i/p voltage both in magnitude and phase, i.e. o/p voltage follower is exactly so ckt is called voltage follower.

- Use of unity gain ckt becoz of i/p impedance is very high in MR & o/p impedance is zero. So it draw negligible current.
- So voltage follower is used as buffer for impedance matching connect high impedance to low impedance
 
### Differential Amplifier:

- ckt that amplifies the difference b/w two signals is called a difference / differential amplifier
- It is very useful in instrumentation ckt.



where 'Va' is voltage at node 'a' node 'a' is at virtual ground  $\underline{[V_a=0]} \Rightarrow \frac{-V_i}{R_i} + \left[ \frac{-V_o}{R_f} \right] = 0 \parallel \frac{-V_i}{R_i} = \frac{V_o}{R_f}$

$$\therefore A_{CL} = \frac{V_o}{V_i} = -\frac{R_f}{R_i}$$

'-' sign indicate a phase shift of  $180^\circ$  b/w  $V_i$  and  $V_o$   
 $R_i \rightarrow$  effective I/P impedance ( $\because$  Inv I/P terminal is at virtual ground)

$\rightarrow$  large value to avoid loading effect


$\hookrightarrow$  limits gain that can be obtained from this ckt  
 $R_L$  (load resistor)

$\hookrightarrow$  at o/p otherwise the I/P impedance of the measuring device such as oscilloscope

$R_i \rightarrow Z_i$  &  $R_f \rightarrow Z_f$

$$\therefore \text{Voltage gain, } A_{CL} = \frac{-Z_f}{Z_i}$$

### Non-Inverting Amplifier:

 

- If signal is applied to non-inverting I/P terminal as feedback is given, ckt amplifiers without Inverting the I/P signal so ckt is called non-inverting amplifier
- Negative feedback s/m as o/p is fed back to inverting I/P
- Differential voltage  $V_d$  at I/P of op-amp is zero & voltage at 'a' is  $V_i$
- $R_f$  &  $R_i$  forms a potential divider

$$V_i = \frac{V_o}{R_i + R_f} R_i$$

No current flows into op-amp

$$\frac{V_o}{V_i} = \frac{R_i + R_f}{R_i} + \frac{R_f}{R_i}$$

- At i/p terminal - differential voltage of op-amp is zero, node 'a' & 'b' are at same potential "V<sub>3</sub>"

Nodal eqn at "a":  $\frac{V_3 - V_2}{R_1} + \frac{V_3 - V_o}{R_2} = 0 \rightarrow ①$

At node "b":  $\frac{V_3 - V_1}{R_1} + \frac{V_3}{R_2} = 0 \rightarrow ②$

Rearranging ①  $\frac{V_3}{R_1} - \frac{V_2}{R_1} + \frac{V_3}{R_2} - \frac{V_o}{R_2} = 0$

$$V_3 \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] - \frac{V_2}{R_1} = \frac{V_o}{R_2} \rightarrow ③$$

Rearranging ②,  $\frac{V_3}{R_1} - \frac{V_1}{R_1} + \frac{V_3}{R_2} = 0$

$$\left[ \frac{1}{R_1} + \frac{1}{R_2} \right] V_3 - \frac{V_1}{R_1} = 0 \rightarrow ④$$

Subtract ④ from ③

$$\Rightarrow \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] V_3 - \frac{V_2}{R_1} = \cancel{\frac{V_o}{R_2}} \quad (1) \\ (-) \left( \left[ \frac{1}{R_1} + \frac{1}{R_2} \right] V_3 - \frac{V_1}{R_1} \right) = \cancel{\frac{V_o}{R_2}}$$

$$\Rightarrow \frac{1}{R_1} (V_1 - V_2) = \frac{V_o}{R_2} \rightarrow ⑤$$

$$\boxed{V_o = \frac{R_2}{R_1} (V_1 - V_2)} \rightarrow ⑥$$

: ckt is very useful in detecting very small difference in signals & gain  $R_2/R_1$  is chosen very large.

## 1.8 General Operational Amplifier stages:

consists of 4 stages

 


fig: Block Schematic of OP-Amp

- first 2 stages are cascaded differential amplifiers used to provide high gain & high o/p resistance
- Third stage act as buffer as well as level shifter
- Buffer is usually emitter follower whose o/p impedance is very high to prevent loading of high gain stage
- Level shifter will adjust dc voltages so  $V_o = 0$ , when  $V_i = 0$
- o/p stage is designed to provide low o/p impedance, o/p voltage should swing symmetrically with respect to ground
- Power Supply =  $\pm 15\text{V}$

### Operational Amplifier internal ckt.

#### (a) Differential amplifier:

- Main purpose is to provide high gain to difference-mode signal, cancel the common-mode signal
- Relative sensitivity of an op-amp to a difference signal as compared to common-mode signal is called "CMRR"
- High the value of CMRR, better is the op-amp
- Cascaded direct coupled amp. can provide high gain down to zero freq as it has no coupling capacitor
- However it suffers from drift due to temperature dependency of  $I_{CQ}$ ,  $V_{BE}$ ,  $b_{FE}$  of transistor, which can be eliminated by using balanced or differential amplifier as shown

 


Fig. Basic differential amplifier

The 4 configurations of differential amp. are

- (i) Differential - i/p, differential - o/p (or) dual - i/p balanced o/p
  - (ii) Differential - i/p, single ended - o/p
  - (iii) Single i/p, differential o/p
  - (iv) Single - i/p, single ended - o/p
- If signal applied at both i/p, it is differential i/p (or) dual  
 → If o/p is measured b/w collectors, it is differential o/p

(b) Transfer characteristics:

The collector current  $i_{c1}$  &  $i_{c2}$  for  $Q_1$  &  $Q_2$  are

$$i_{c1} = \alpha_F I_{ES} e^{V_{BE1}/V_T} \quad \rightarrow ①$$

$$i_{c2} = \alpha_F I_{ES} e^{V_{BE2}/V_T} \quad \rightarrow ②$$

$$\text{From } ① \text{ & } ②, \frac{i_{c1}}{i_{c2}} = e^{(V_{BE1} - V_{BE2})/V_T} \quad \rightarrow ③$$

Apply KVL, for loop has 2 Emitter-base jn.

$$V_1 - V_{BE1} + V_{BE2} - V_2 = 0$$

$$(or) V_{BE1} - V_{BE2} = V_1 - V_2 = V_d$$

where, ' $V_d$ ' is diff. of 2 i/p voltage

It is observed that

$$④ \text{ For } V_d > 4 V_T, i_{c1} = \alpha_F I_{ES}, i_{c2} = 0$$

$$\text{Hence, } V_{o1} = V_{cc} - dF I_Q R_C$$

$$V_{o2} = V_{cc}$$

(13)

$$\textcircled{2} \text{ For } V_d < -4V_T, i_{C1} = 0, i_{C2} = dF I_Q$$

$$\text{Hence } V_{o1} = V_{cc}, V_{o2} \text{ is negligible}$$

\textcircled{3} Differential amp function as a very good limiter

\textcircled{4} It can also fn as automatic gain ctrl

\textcircled{5} B/w value  $-2V_T \leq V_d \leq 2V_T$ , it functions as linear amp.


 


fig. Transfer characteristics of Diff Amp

\textcircled{6} Low frequency Small signal analysis:

 An ideal dual-i/p balanced-o/p differential amplifier is



- It amplifies only differential signl at 2 i/p

- Rejects signal common to these i/p

- Any unwanted signal such as noise, would be rejected

The a.c analysis can be performed either by hybrid  $\pi$  model, or h-parameter model

→ Differential mode gain,  $A_{DM}$

$$(i) \text{ using hybrid } \pi\text{-model, } A_{DM} = \frac{V_{o1} - V_{o2}}{V_d} = -g_m R_c$$

$$(ii) \text{ using h-parameter, } A_{DM} = \frac{V_{o1} - V_{o2}}{V_d} = -\frac{h_{fe} R_c}{h_{ie}}$$

→ Common-mode gain,  $A_{CM}$  using h-parameter

$$A_{CM} = \frac{V_{o1}}{V_{o2}} = \frac{-h_{fe} R_c}{h_{ie} + (1+h_{fe}) 2 R_B}$$

The common-mode rejection ratio (CMRR)

$$CMRR = \left| \frac{A_{DM}}{A_{CM}} \right|$$

(d) Circuits for improving CMRR:-

- For CMRR to be large,  $A_{CM}$  should be less
- With current constant, the CMRR  $A_{CM}$  is zero
- Small signal current flowing through load resistor is zero resulting zero o/p voltage
- IC op-amp μA741 uses a constant current source which very simple & use less number of current circuit is known as current mirror
- It offers large resistance under any circumstances, thereby high value of CMRR.

$$\bar{I}_B = \frac{\bar{I}_B^+ + \bar{I}_B^-}{2}$$



\* For 741, bipolar op amp, bias current is 500nA or less.  
FET input opamp, bias current as low as 50pA at room temp.

\* Consider, basic inverting amplifier,  $V_i = 0V$  &  $V_o = 0V$  but output voltage is offset by,

$$V_o = (\bar{I}_B) R_2$$

for a 741 op amp with  $1M\Omega = R_2$
  
$$V_o = 500 \text{nA} \times 1M\Omega = 500 \text{mV}$$



### INVERTING AMPLIFIER WITH BIAS CURRENT

\* Signal level is measured in millivolts, that is unacceptable, this compensated by  $R_{comp}$  added between non-inverting input terminal and ground.

\* Current  $I_B^+$  flowing through  $R_{comp}$  develops a voltage  $V_1$  across it.

By KVL,  $-V_1 + 0 + V_2 - V_o = 0$

$$V_o = V_2 - V_1$$

\* By properly selecting value of  $R_{comp}$  &  $V_2$  can be cancelled with  $V_1 \rightarrow V_o = 0$

$R_{comp}$  derived

$$V_1 = \bar{I}_B^+ R_{comp}$$

$$\bar{I}_B^+ = \frac{V_1}{R_{comp}}$$

\* Node 'a' is at voltage  $(-V_1)$  because of non-inverting input terminal ( $-V_1$ )

$$V_1 = 0; \text{ we get } \bar{I}_1 = \frac{V_1}{R_1}$$

$$I_2 = V_2$$

For compensation,  $V_o$  should be zero. For  $V_i = 0$ .

From  $V_o = V_2 - V_1$

$$V_2 = V_1$$

$$\text{so that } I_B = \frac{V_1}{R_2}$$

KCL at node 'a' gives


$$I_B^- = I_B^+ + I_1 = \frac{V_1}{R_2} + \frac{V_1}{R_1} = V_1 \frac{(R_1 + R_2)}{R_1 R_2}$$

Assuming  $I_B^- = I_B^+$

$$\frac{V_1 (R_1 + R_2)}{R_1 R_2} = \frac{V_1}{R_{\text{comp}}}$$

$$R_{\text{comp}} = \frac{R_1 R_2}{R_1 + R_2} = R_1 \parallel R_2$$

 \* Effect of input bias current in non-inverting amplifier, compensated by placing  $R_{\text{comp}}$  in series with  $\gamma_1$ .



#### INPUT OFFSET CURRENT

\* The bias current compensation will work only when  $I_B^+ = I_B^-$ . Since of transistors cannot make identical,  $I_B^+ \neq I_B^-$ . This difference is called offset current  $I_{\text{os}}$ .

$$I_{\text{os}} = I_B^+ - I_B^-$$

↑ indicates we can not predict  $I_B^+$  or  $I_B^-$  will be higher.

$I_{os} \Rightarrow$  BJT op amp = 200nA

FET op amp = 10pA

\*  $I_{os}$  produce o/p voltage, even when  $V_i = 0$

$$V_i = I_B^+ R_{comp}$$

$$I_1 = \frac{V_i}{R_1}$$

Net at node 'a' gives,

$$I_{20} = (I_B^- - I_1)$$

$$= I_B^- - \left( I_B^+ \frac{R_{comp}}{R_1} \right)$$

$$V_o = V_2 - V_1, \quad V_2 = V_o + I_B^+ R_{comp}$$
$$V_o = I_{20} R_2 - V_1 = I_{20} R_2 - I_B^+ R_{comp}$$

$$= \left( I_B^- - I_B^+ \frac{R_{comp}}{R_1} \right) R_2 - I_B^+ R_{comp}$$


Sub  $R_{comp}$  value & algebraic Manipulation,

$$V_o = R_2 [I_B^- - I_B^+]$$

$$V_o = R_2 I_{os}$$

\* Effect of  $I_{os}$  is minimized by keeping  $R_2$  small, but  $R_1$  must be kept large but  $R_F$  should also maintained high to obtain high gain.

 \* T-feedback network is used to keep resistance low. and also provides feedback signal by T to TI conversion.



INVERTING AMPLIFIER WITH  
T-FEEDBACK NETWORK

$$R_F = \frac{R_L^2 + 2R_E R_S}{R_S}$$

To design,

$$R_E \ll R_{L/2}$$


then

$$R_E = \frac{R_L^2}{R_L + 2R_E}$$


## INPUT OFFSET VOLTAGE:

- \* Output voltage will not be equal to input voltage due to imbalance inside op-amp. A small voltage is applied at input to get  $V_o = 0$ . This voltage is called input offset voltage  $V_{ios}$ .


OP AMP SHOWING INPUT OFFSET VOLTAGE

 

 - \* Effect of  $V_{ios}$  on % of non-inverting, inverting op-amp is.




NON-INVERTING AMPLIFIER

 

INVERTING AMPLIFIER

 - \* If  $V_i = 0$ , then above two figures become the same.



EQUIVALENT CIRCUIT FOR  $V_i = 0$

- \* Voltage  $V_2$  at '-' terminal is,

$$V_2 = \left( \frac{R_1}{R_1 + R_2} \right) V_o$$

$$V_o = \left( \frac{R_1 + R_2}{R_1} \right) V_2 = \left( 1 + \frac{R_2}{R_1} \right) V_2$$

$$V_{ios} = |V_i - V_2| \text{ and } V_i = 0$$

$$= |0 - V_2| = V_2$$

$$V_o = \left( 1 + \frac{R_2}{R_1} \right) V_{ios}$$

## ↳ TOTAL OUTPUT OFFSET VOLTAGE :

- \* Total output offset  $V_{OT}$  could be either more or less than the offset voltage produced at the output due to input bias current / input offset voltage alone (bcz of  $V_{ICB}$  &  $I_B$  either +ve or -ve wrt ground).

∴ Maximum offset voltage without compensation is

$$V_{OT} = \left(1 + \frac{R_f}{R_i}\right) V_{IOS} + R_f I_B$$

- \* With Biomp., total o/p offset Voltage,

$$V_{OT} = \left(1 + \frac{R_f}{R_i}\right) V_{IOS} + R_f I_\alpha$$

## ↳ THERMAL DRIFT

- \* Bias current, offset current and offset voltage change with temperature.
- \* A circuit carefully nulled at  $25^\circ\text{C}$  may not remain so when the temperature rises to  $35^\circ\text{C}$ . This is called drift.
- \* Offset current drift =  $\text{nA}/^\circ\text{C}$
- \* Offset voltage drift =  $\text{mV}/^\circ\text{C}$
- \* Techniques to minimize effect of drift:
  - ↳ careful printed circuit board layout used to op-amp away from source of heat.
  - ↳ forced air cooling may be used to stabilize the ambient temperature.

## AC CHARACTERISTICS :-

For small signal sinusoidal (AC) applications,

↳ Frequency Response

↳ Slew-rate.

### Frequency Response

\* Ideal op-amp have infinite bandwidth open loop gain is 70 dB with dc signal its gain should remain the same through audio/high radio frequency.


\* Practical op-amp gain, however, decreases at high frequencies.

Gain of op-amp to roll off after certain frequency

\* Block of capacitive component in equivalent ckt  $\rightarrow$  capacitance

↳ Physical characteristics of device (BJT/FET)

 \* Op-amp with <sup>only</sup> one break (corner) frequency  $\rightarrow$  capacitor effect represents by single capacitor C.



HIGH FREQUENCY MODEL OF AN OP-AMP (APPLIED FOR FREQ. > 1000 Hz)

WITH CORNER FREQUENCY ( $f_c$ )

\* High frequency is a modified version of low frequency model with capacitor C at output  $\rightarrow$  one pole due to  $R_oC = 20 \text{ dB/decade}$  roll off.

(17)

## 1.10 AC PERFORMANCE CHARACTERISTICS:

DC characteristics affect the steady state (dc) response of op amp only. For small sinusoidal (ac) applications, one has to know the ac characteristics such as frequency response & slew-rate.

### 1.10.1: Frequency response:

- Ideal op-amp have infinite bandwidth, Open loop gain is 90 dB with dc signal. Its gain should be the same through audio & radio frequency.
- In practical op-amp, however gain decreases at high frequencies. Thus gain of op-amp roll-off after certain frequencies.
- Because of the capacitive component in equivalent ckt, which is caused by physical characteristics of device (BJT/FET)
- Op-amp has one break (corner) frequency  $\rightarrow$  capacitor effect represents by single capacitor  $C$ .

 


Fig. High freq. model of op-amp with single corner freq.

- High freq is a modified version of low freq model with capacitor 'C' at O/P. There is one pole due to  $R_{OC}$  is -20dB/decade roll off.

$$\text{Open loop voltage gain, } V_o = \frac{-jX_C}{R_O - jX_C} AOL V_d$$

$$A = \frac{V_o}{V_d} = \frac{AOL}{1 + j 2\pi f R_{OC}}$$


$$= \frac{AOL}{1 + j(f/f_1)}$$

where  $f_1 = \frac{1}{2\pi R_{OC}} \Rightarrow$  corner freq or upper 3-dB freq of op-amp


$$\text{Magnitude, } |A| = \frac{A_{OL}}{\sqrt{1 + (f/f_1)^2}}$$

$$\text{Phase angle } \phi = -\tan^{-1}(f/f_1)$$

Magnitude vs phase characteristics

 

 fig(a): open loop magnitude characteristics in semilog paper



fig(b): phase characteristics for an op-amp with single break frequency

- (i) for  $f \ll f_1$ ,  $|A|$  of gain is  $20 \log A_{OL}$  in dB
- (ii) At  $f = f_1$ , gain is 3dB down from dc value of  $A_{OL}$  in dB  
 $f_1$  is corner freq.
- (iii)  $f \gg f_1$ , gain rolls-off at the rate of  $-20 \text{dB/decade}$  or  $-6 \text{dB/octave}$

phase characteristics: At  $f=0$ , phase angle =  $0^\circ$

At corner freq.  $f_1$ , phase angle is  $-45^\circ$  (lagging)

At infinite freq., phase angle is  $-90^\circ$

Maximum of  $90^\circ$  phase change occurs with single capacitor

- For practical purpose, zero freq = 1 decade below  $f_1$   
Infinite freq = 1 decade above  $f_1$

Voltage transfer function in S-domain

$$A = \frac{A_{OL}}{1 + j(f/f_1)} = \frac{A_{OL}}{1 + j(\frac{\omega}{\omega_1})} = \frac{A_{OL}}{\frac{\omega_1 + j\omega}{\omega_1}}$$

$$= \frac{A_{OL} \omega_1}{\omega_1 + j\omega} = \frac{A_{OL} \omega_1}{S + \omega_1} \quad (\because S = j\omega)$$

(18)

- A practical op-amp has number of stages, each stage produce capacitive component, due to no of RC pole pairs, there will be number of break frequencies.

$\therefore$  Transfer function of op-amp with 3-break frequencies

$$\begin{aligned} A &= \frac{A_{OL}}{\left(1+j\frac{f}{f_1}\right)\left(1+j\frac{f}{f_2}\right)\left(1+j\frac{f}{f_3}\right)} ; \quad 0 < f_1 < f_2 < f_3 \\ &= \frac{A_{OL}}{\left(\frac{\omega_1 + j\omega}{\omega_1}\right)\left(\frac{\omega_2 + j\omega}{\omega_2}\right)\left(\frac{\omega_3 + j\omega}{\omega_3}\right)} \\ &= \frac{A_{OL} \cdot \omega_1 \cdot \omega_2 \cdot \omega_3}{(s + \omega_1)(s + \omega_2)(s + \omega_3)} ; \quad \text{with } 0 < \omega_1 < \omega_2 < \omega_3 \end{aligned}$$

- For the below figure, as frequency increases, cascading effect of RC pairs comes into effect. Roll-off rate increases successively by  $-20\text{dB/decade}$  at each corner frequency.
- Each RC pole pair introduce lagging phase of maximum upto  $-90^\circ$ .

 


Fig Approximation of open loop gain vs frequency curve

## 1.10.2 Stability of an Op-Amp:


- Op amps are rarely used in open loop configuration because of high gain
- Consider effect of feedback on freq. response  
Op-amp uses resistive feedback n/w,  $V_o = 0$  for inverting amp  
 $\& V_o = 0$  for non-inv amplifier

Closed loop transfer fn: -ve feedback

$$A_{CL} = \frac{A}{1 + A\beta} \rightarrow ①$$

where,  $A$  = open loop voltage gain

$\beta$  = feedback ratio

 

Resistive feedback provided  
in Op-Amp

From ①,

Characteristic eqn  $(1 + A\beta) = 0$

Thus ckt becomes unstable, leads to sustained oscillation

Rewriting,  $1 - (-A\beta) = 0$  leads to, loop gain:  $-A\beta = 1 \rightarrow ②$

$A\beta$  = complex quantity,  $|A\beta| = 1$

Phase condition:  $\angle -A\beta = 0$  (or multiple of  $2\pi$ )  
 $\angle A\beta = \pi$  (or multiple of  $\pi$ )

- In the ckt, feedback n/w is resistive n/w and it doesn't provide any phase shift  $\therefore$  op-amp is in inverting node, provide  $180^\circ$  phase shift at low freq.
- At high freq., additional  $-90^\circ$  phase shift occurs in open loop gain due to corner frequency.
- Two corner frequencies, maximum of phase shift associated with gain  $A$  is  $-180^\circ$
- At high freq., some value of  $\beta$ , magnitude of  $A\beta = 1$ , when  $A$  has additional phase shift of  $180^\circ$ , which makes total phase shift = 0
- Amplifier begins to oscillate as both magnitude & phase condition laid down, oscillation is just the starting point of instability

Instability  $\rightarrow$  unbounded CLP

$$(1 + A\beta) \leq 1$$

$A\beta \geq 0$  i.e. negative

$\rightarrow$  Then  $A_{CL} > A$ , i.e. closed loop gain increases & leads instability

$\rightarrow$  Phase contribution = zero

- At low frequency, additional phase contribution of  $A$  is zero,  
 $A\beta > 0$ ,  $A_{CL} \leq A$ , SLM is stable

- At high frequency, SLM 'A' have 3 corner freq. or 3 RC pole pair,  
possible of open loop gain  $A$  to contribute a maximum  
of  $-270^\circ$  phase shift  
 $\therefore A\beta = -ve$ , instability occurs.

- For stable operation, the ratio of change b/w closed loop gain  
and open-loop gain should not exceed  $-20 \text{ dB/decade}$ .
- At high freq., for lower closed loop gain, the feedback  
become significant & regenerative. It creates sustained oscillation.

For quantitative discussion about stability,

Transfer fn. of op-amp characterized by 3 poles

$$A = \frac{-A_{OL} \omega_1 \omega_2 \omega_3}{(s+\omega_1)(s+\omega_2)(s+\omega_3)}, \quad \text{OL } \omega_1 < \omega_2 < \omega_3 \rightarrow (3)$$

Poles of open loop Transfer fn are  $-\omega_1, -\omega_2, -\omega_3$

- Closed loop poles are  $A_{CL}$  that is given by the  
root characteristic eqn. (from freq. response)

$$\boxed{1 + A\beta = 0}$$

$$\Rightarrow A = \frac{A_{OL} \omega_1 \omega_2 \omega_3}{(s+\omega_1)(s+\omega_2)(s+\omega_3)}$$

Sub 'A' in above eqn

$$\Rightarrow 1 + \frac{\beta A_{OL} \omega_1 \omega_2 \omega_3}{(s+\omega_1)(s+\omega_2)(s+\omega_3)} = 0$$

$$\Rightarrow (s+\omega_1)(s+\omega_2)(s+\omega_3) + \beta A_{OL} \omega_1 \omega_2 \omega_3 = 0 \rightarrow (4)$$

$$(or) \left. \begin{aligned} & S^3 + S^2(\omega_1 + \omega_2 + \omega_3) + S(\omega_1\omega_2 + \omega_1\omega_3 + \omega_2\omega_3) \\ & + \omega_1\omega_2\omega_3 + \beta A_{OL} \omega_1\omega_2\omega_3 \end{aligned} \right\} = 0$$

$$\Rightarrow \left. \begin{aligned} & S^3 + S^2(\omega_1 + \omega_2 + \omega_3) + S(\omega_1\omega_2 + \omega_1\omega_3 + \omega_2\omega_3) \\ & + \omega_1\omega_2\omega_3 (1 + \beta A_{OL}) \end{aligned} \right\} = 0 \rightarrow (5)$$

Roots of cubic eqn., depends on  $\beta A_{OL}$ , dc loop gain

- $\beta A_{OL} = 0$ , roots at  $-\omega_1, -\omega_2, -\omega_3$  lie at -ve real axis.
- For small value of  $\beta A_{OL}$ , roots lie on left half of S-plane with one real root, 2 complex conjugate roots (a.d)
- Critical value of  $\beta A_{OL}$  makes system unstable

$$\boxed{a_3 S^3 + a_2 S^2 + a_1 S + a_0 = 0} \rightarrow (6)$$

Comparing (5) & (6)

$$a_3 = 1 ; a_2 = \omega_1 + \omega_2 + \omega_3 ; a_1 = \omega_1\omega_2 + \omega_1\omega_3 + \omega_2\omega_3 \rightarrow (7)$$

$$a_0 = \omega_1\omega_2\omega_3 (1 + \beta A_{OL})$$

Apply Routh's Stability criterion,  
 or (i) All co-efficients of  $a_3, a_2, a_1$  &  $a_0$  should be positive

$$(i) a_1 a_2 - a_3 a_0 = 0$$

$$\text{Sub } \boxed{S = j\omega} \text{ in } (6) \Rightarrow a_3 (j\omega)^3 + a_2 (j\omega)^2 + a_1 (j\omega) + a_0 = 0$$

$$\Rightarrow a_3 (-j\omega^3) + a_2 (-\omega^2) + a_1 (j\omega) + a_0 = 0$$

$$\Rightarrow (a_0 - a_2 \omega^2) + j\omega (a_1 - a_3 \omega^2) = 0$$

Real & imaginary parts are equal to zero

$$a_0 - a_2 \omega^2 = 0$$

$$\therefore \omega_{osc} = \pm \sqrt{\frac{a_0}{a_2}}$$

$$a_1 - a_3 \omega^2 = 0$$

$$\omega_{osc} = \pm \sqrt{\frac{a_1}{a_3}}$$

Sub  $a_0, a_1, a_2, a_3$  from (7)

$$\Rightarrow \omega_{osc} = \sqrt{\frac{a_1}{a_3}} = \sqrt{\omega_1\omega_2 + \omega_1\omega_3 + \omega_2\omega_3}$$

$$\Rightarrow a_0 = \frac{a_1 a_2}{a_3} \text{ from Routh criteria (i)} \rightarrow (8)$$

(20)

$$\Rightarrow \omega_1, \omega_2, \omega_3 [1 + (\beta A_{OL})_c] = \frac{(\omega_1 \omega_2 + \omega_1 \omega_3 + \omega_2 \omega_3)(\omega_1 + \omega_2 + \omega_3)}{1} \\ (\text{or}) \quad (\beta A_{OL})_c = 2 + \frac{\omega_1}{\omega_2} + \frac{\omega_1}{\omega_3} + \frac{\omega_2}{\omega_1} + \frac{\omega_2}{\omega_3} + \frac{\omega_3}{\omega_1} + \frac{\omega_3}{\omega_2} \rightarrow (5)$$

If it is desired that amplifier should remain stable, then  $A_{OL}$  must satisfy the condition,  $\boxed{\beta = 1}$ .

$$\text{i.e. } A_{OL} < 2 + \frac{\omega_1}{\omega_2} + \frac{\omega_1}{\omega_3} + \frac{\omega_2}{\omega_1} + \frac{\omega_2}{\omega_3} + \frac{\omega_3}{\omega_1} + \frac{\omega_3}{\omega_2}$$

### 1.10.3 FREQUENCY COMPENSATION:

In applications where one desires large BW and low closed loop gain, suitable compensation techniques are used. Two types are

- (i) External compensation
- (ii) Internal compensation

#### (i) External Compensation:

- Some op-amps are made to be used with externally connected compensating network so that roll-off is  $-20\text{dB/decade}$  over a wide range of frequency.
- Two methods : (a) Dominant pole
- (b) Pole-zero(lag)

#### (a) Dominant pole Compensation:

- 'A' is uncompensated transfer fn. of op-amp in open loop
- Introduce dominant pole by adding RC network in series with op-amp (or) capacitor 'C' to ground, which have high resistance

Compensated transfer function 'A' becomes,

$$\begin{aligned} A' &= \frac{V_o}{V_i} \\ &= A \cdot \frac{-j/\omega_c}{R - j/\omega_c} \\ &= \frac{A}{1 + j f / f_d} \end{aligned}$$

$$\text{where, } f_d = \frac{1}{2\pi R C}$$

 


fig. Dominant pole compensation

$$A' = \frac{A_{OL}}{(1 + j \frac{f}{f_d})(1 + j \frac{f}{f_1})(1 + j \frac{f}{f_2})(1 + j \frac{f}{f_3})}; f_d < f_1 < f_2 < f_3$$

- Capacitor 'c' is chosen so that modified loop gain drops to 0 dB with slope of -20dB/decade at frequency where the pole of uncompensated transfer function A contribute negligible phase shift
- $f_d = \frac{\omega_d}{2\pi}$  chosen to make A' pass through 0dB at pole  $f_d$  of uncompensated A

Value of capacitor calculated

$$f = \frac{1}{2\pi R C}$$

Disadvantage:

Reduces open loop bandwidth drastically

Advantage:

Noise immunity of system is improved. Since noise from components outside band width are eliminated

Pole-Zero Compensation:

- Uncompensated transfer fn. A is altered by adding both pole & zero

- Zero should be at high frequency than pole
- Transfer fn. of compensating n/w is

$$\frac{V_o}{V_i} = \frac{Z_2}{Z_1 + Z_2} = \frac{R_2}{R_1 + R_2} = \frac{1 + j f / f_1}{1 + j f / f_0}$$

(21)

 


fig. Pole-Zero compensation

- Compensating n/w is designed to produce zero at 1<sup>st</sup> corner freq  $f_1$  of uncompensated transfer fn A
- This zero will cancel effect of pole at  $f_1$ . Pole at  $f_0 = \frac{\omega_0}{2\pi}$  which is selected to  $A'$  and is passed through 0dB at  $f_2$  of uncompensated T.F. A.
- Assume compensating n/w doesn't load the amplifier, i.e.  $R_2 \gg R_1$

Overall Transfer fn become


$$\begin{aligned}
 A' &= \frac{V_o}{V_i} = \frac{V_o}{V_2} \cdot \frac{V_2}{V_i} \\
 &= A \cdot \frac{R_2}{R_1 + R_2} \cdot \frac{1 + j f / f_1}{1 + j f / f_0} \\
 &= \frac{A_{OL}}{(1 + j \frac{f}{f_1})(1 + j \frac{f}{f_2})(1 + j \frac{f}{f_3})} \cdot \frac{R_2}{R_1 + R_2} \cdot \frac{1 + j f / f_1}{1 + j f / f_0} \\
 &= \frac{A_{OL}}{(1 + j \frac{f}{f_2})(1 + j \frac{f}{f_3})(1 + j f / f_0)} ; 0 < f_0 < f_1 < f_2 < f_3
 \end{aligned}$$

$R_2 \gg R_1$ , so that  $\frac{R_2}{R_1 + R_2} \approx 1$

Now select  $R_2$  &  $C_2$  so that zero of compensating n/w is equal to pole at the freq  $f_1$  (lowest)

 (ii) Internally Compensated Op-Amp

- Relatively broad bandwidth of uncompensated op-amp is not needed
- Internally compensated op-amps can be used to amplify slow changing signals : doesn't require good high freq response



- Stable regardless of value of closed loop gain
- IC 741 has  $C_1$  of  $30\text{ pF}$  internally shunt off signal current and reduce available o/p signal at higher frequencies
- $C_1 \Rightarrow$  internal compensating ckt, cause open loop gain to roll off at  $-20\text{ dB/decade}$  & stable ckt
- IC 741  $\rightarrow 1\text{ MHz}$  gain bandwidth product

 


fig. frequency response of HA741 op-amp

## SLEW RATE

- \* The rise time of an amplifier is defined as the time the output takes to change from 10 to 90% of final value for a step i/p  $0.35/BW$  ( $BW$ : bandwidth of amplifier)
- \* Ideal response time should be zero seconds as  $BW$  is infinite for ideal op-amp i.e., output voltage respond to any change in input.
- \* Rise time is usually specified for small signals  $\Rightarrow$  when peak output voltage is less than Volt, for large signal output ( $V_m > 1V$ ) opamps speed is limited by slew rate.
- \* Opamps slew rate is related to frequency response.
- \* Opamps with wide bandwidth will have higher (better) slew rates.
- \* Slew rate is defined as maximum rate of change of output voltage caused by a step input voltage and is usually specified in  $V/\mu s$ .
- \* An ideal slew rate is infinite which means that op-amps output voltage change instantaneously in response to input step voltage.
- \* Practical opamp slew rate is  $0.1V/\mu s$  to above  $1000V/\mu s$ .
- \* Slew rate improves with higher closed loop gain and dc supply voltage.  $\rightarrow$  also function of temperature and decreases with an increase in temperature.

## Causes of Slew Rate :-

- \* Capacitor within /outside op-amp prevents oscillation, but this capacitor prevents output voltage immediately to fast changing input. The rate at which voltage across capacitor increases is

$$= \frac{dV_c}{dt} = \frac{I}{C}$$

$I$  = maximum current furnished by op-amp to capacitor

- \* For obtaining faster slew rate, op-amp should have higher current small compensating capacitor

For 741,  $I = 15\text{mA}$ .

$$\therefore SR = \frac{dV_o}{dt} \Big|_{max} = \frac{I_{max}}{C} = \frac{15\text{mA}}{30\text{pF}} = 0.5 \text{V/}\mu\text{s}$$

\* Slew rate limits the response speed of all large signal waveshapes

\* For sine wave input, effect of slew rate

$$\text{if } \rightarrow V_g = V_m \sin \omega t.$$

$$\text{Then o/p, } V_o = V_m \sin \omega t.$$

\* The rate of change of output is given by

$$\frac{dV_o}{dt} = V_m \omega \cos \omega t.$$

\* Maximum rate of change of output occurs, when  $\cos \omega t = 1$  is

$$SR = \frac{dV_o}{dt} \Big|_{max} = \omega V_m.$$

$$\text{Therefore, } \text{slew rate} = 2\pi f \cdot V_m \text{ } \text{V/}\mu\text{s}$$

$$= \frac{2\pi f V_m}{10^6} \text{ V/}\mu\text{s.}$$

where  $f$  = input frequency (Hz)


$V_m$  = peak output amplitude

If frequency / amplitude of input signal is increased to exceed slew rate of opamp, output will be distorted.

\* Thus, maximum input frequency  $f_{max}$  at which we obtain undistorted output voltage of peak value  $V_m$  is given by

$$f_{max} (\text{Hz}) = \frac{\text{Slew Rate} \times 10^6}{6.28 \times V_m}$$

 $f_{max}$  = full power response It is maximum frequency of a large amplitude sine wave with which opamp can handle without distortion.




## OPEN Loop Op-Amp Configuration:-

- \* Open loop indicates no feedback from output to input.
- \* When connected in open-loop, op-amp functions as a very high gain amplifier.
- \* 3 open loop configuration of op-amp, [based on no of ip's used]
  - ↳ Differential amplifier
  - ↳ Inverting amplifier
  - ↳ Non-inverting amplifier.
- \* Op-amp amplifies both ac and dc input signals. So input can be ac or dc voltages
 
### ↳ OPEN Loop DIFFERENTIAL AMPLIFIER:-

- \* In this configuration, inputs are applied to both inverting and non-inverting input terminals of the op-amp and it amplifies the difference between two input voltage.



OPEN Loop DIFFERENTIAL AMPLIFIER.

- \* The input voltages are represented by  $V_{in1}$  and  $V_{in2}$ . The source resistance  $R_{in1}$  and  $R_{in2}$  are negligibly small in comparison with the very high input resistance offered by op-amp thus voltage drop across these source resistances is assumed to be zero.
- \* The output voltage  $V_o$  is given by

$$V_o = A(V_{in1} - V_{in2})$$

voltage gain = output voltage  
(A)

A times difference b/n

2 inputs voltages

- \* Large signal voltage gain A is called Open-loop gain A.


#### INVERTING AMPLIFIER :-

- \* In this configuration, input signal is applied to the inverting input terminal of op-amp. and non-inverting input terminal is connected to the ground.
- \* The output voltage is  $180^\circ$  out-of-phase with respect to the input and output voltage  $V_o$  is

$$V_o = -AV_i$$

- \* Thus, in an inverting amplifier, the input signal is amplified by open loop gain A and phase shifted by  $180^\circ$ .

OPEN LOOP INVERTING AMPLIFIER.

 

#### NON-INVERTING AMPLIFIER :-

- \* The input signal is applied to the non-inverting input terminal of the op-amp and inverting input terminal is connected to the ground.
- \* Input signal is amplified by open-loop gain A and output is in phase with the input signal

$$V_o = AV_i$$

- \* Voltage bias slightly greater than zero, output is driven into saturation.

either in negative or positive saturation or switches between both. This prevents the use of open loop configuration of op-amps in linear application.

(24)

#### » LIMITATIONS OF OPEN LOOP OP-AMP CONFIGURATION:-

- \* Clipping of output waveform occurs due to output voltage exceeds the saturation level of op-amp.
- \* Due to very high open-loop gain of op-amp. This makes it possible to amplify very low frequency signal (mV or even less) so amplification done accurately without any distortion.
- \* Open-loop gain of op-amp is not constant & varies with changing temperature & variation in power supply.
- \* Bandwidth of open loop op-amp is negligibly small. This makes open-loop config. unsuitable for osc applications.
- \* IC41 - B.W = 5Hz
- \* Open loop configuration not used in linear applications in non-linear applications such as comparators, square wave generators & astable multivibrators.

#### CLOSED LOOP OP-AMP CONFIGURATIONS:-

- \* Op-amp utilized in linear application by providing a feedback from output to input.
- \* If signal feedback is out-of phase by  $180^\circ$  w.r.t to input then feedback is referred to as "Negative feedback" or "Regenerative feedback".
- \* If signal feedback is in-phase with that of input, then feedback is referred to as "Positive feedback" or "Regenerative feedback".
- \* Op-amp that uses feedback is called a CLOSED LOOP AMPLIFIER.


- ↳ Inverting amplifier (voltage - shunt feedback)
- ↳ Non-inverting amplifier (voltage - series feedback)

#### ↳ INVERTING AMPLIFIER:-

- \* Input signal drives the inverting input of op-amp ~~open-loop gain~~ through resistor  $R_1$ .
- \* Op-amp has an open-loop gain of  $A$ ,  $\text{O/P}$  signal is much larger than the error voltage.
- \* Because of phase inversion, output signal is out of phase  $180^\circ$  with input signal.
- \* Feedback signal opposes the input signal and the feedback is negative / degenerative.
 
#### \* VIRTUAL GROUND:

- \* Virtual ground is a ground which acts like a ground. May not have physical connection to ground. This property of an ideal op-amp indicates that inverting non-inverting terminals of op-amp are same potential.
- \* Non-inverting input is grounded for inverting amplifier, so inverting input of op-amp is also at ground potential.
- \* Virtual ground is at fixed ground potential (or).
- \* Input current is so small as to appear to zero.
- \* If voltage applied at inverting  $\text{I/P} \rightarrow V_{\text{id}} = \text{differential voltage}$  is negligibly small,  $\text{I}_0 = 0$  so, inverting input act as virtual ground.
- \* Virtual ground where voltage with respect to ground is zero. yet no current can flow on it



CLOSED LOOP INVERTING AMPLIFIER.

\*  $Z_i = R_1$  ( . . . inv i/p = virtual ground)

$$\therefore I_1 = \frac{V_i}{R_1}$$

\* This current must flow through  $R_2$ , bcoz, virtual ground accepts negligible current.

$$V_o = -I_2 R_2 = -\frac{R_2}{R_1} V_i$$

Closed loop Voltage gain  $A_v$ ,

$$A_v = \frac{V_o}{V_i} = -\frac{R_2}{R_1}$$

#### » NON-INVERTING AMPLIFIER

- \* Input signal drives non-inverting i/p of op-amp. Op-amp provides an internal gain A
- \* External resistors  $R_1$  &  $R_2$  from the feedback voltage divider etc. with an attenuation factor of B
- \* Feedback voltage is at inverting i/p, it opposes i/p voltage at the non-inverting i/p terminal  $\Rightarrow$  ac feedback is negative/degenerative.

Differential voltage  $V_{ID}$  at the input of the op-amp is zero, hence at node  $a$ , is at same voltage as that of non-inv terminal

$y_p$  terminal

\*  $R_1$  &  $R_2$  form a potential divider,

$$\therefore V_i = \frac{R_1}{R_1+R_2} \times V_o$$

No no current flow into op-amp

$$\frac{V_o}{V_i} = \frac{R_1+R_2}{R_1} = 1 + \frac{R_2}{R_1}$$

\* Voltage gain for non inv amplifier is

$$A_v = \frac{V_o}{V_i} = 1 + \frac{R_2}{R_1}$$

\* Feedback factor of the feedback voltage divider network

$$\beta = \frac{R_1}{R_1+R_2}$$

\* closed loop gain is

$$A_v = \beta = \frac{R_1+R_2}{R_1}$$

$$A_v = 1 + \frac{R_2}{R_1}$$

$A_v$  always  $\gg 1$ . depends on ratio of feedback resistance

\* closed loop gain doesn't drift with temperature change

or op amp replacement

\* Input resistance of the op amp is extremely large.

## Unit II - Applications of Operational Amplifiers

### Syllabus:

Sign changers - scale changers - phase shift ckt, voltage followers - VtoS \*  
 Sign changers - scale changers - phase shift ckt, voltage followers - VtoS \*  
 Sign changers - scale changers - phase shift ckt, instrumentation amplifier, Integrators,  
 D to V converters, adder, subtractor, Instrumentation amplifier, comparators,  
 Differentiators, Logarithmic amplifier, Antilogarithmic amplifier, band-pass  
 Schmitt triggers, precision rectifiers, peak detector, clippers & clampers,  
 Low-pass, high-pass and band-pass Butterworth filters

(WWW - What, Why, Where)

Introduction: (WWW - What, Why, Where)

① What does this unit deals about?  
 As we have discussed about electronics of op-amp  
 (ac/dc characters, limitations, open/closed loop configuration), we take  
 a look at the applications of an op-amp.

② Why we study this?

- op-amp has countless applications which form basic building block
- of analog sm (both linear & non-linear)
- Linear applications (Toper's filter, differentiator)
- non-linear applications (filter, filters)

③ Where this unit applied in practice?

They are very useful in industrial instrumentation, communication  
 & general signal processing.

### 2.1 Sign changer: (Phase Inverter)

The basic inverting amp configuration using an op-amp with  
 input impedance  $Z_i$  and feedback impedance  $Z_f$  is shown.

 


fig. inverting op-amp with  
Shunt f/b

closed loop voltage gain :  $-\frac{Z_f}{Z_i}$

Impedance  $Z_i$  &  $Z_f$  are equal in magnitude & phase, then  
 closed loop voltage gain is  $-1$ .

→ which cause  $180^\circ$  phase shift at o/p  $\rightarrow$  it is called as "Phase inverter".

### 2.2 Scale changer:

- Referring to the same <sup>below</sup> fig., if ratio  $Z_f/Z_i = k$ , a real constant, then closed loop gain is  $-k$
- O/P voltage is multiplied by  $-k$
- Scaled o/p is available at o/p
- In such applications,  $Z_f$  &  $Z_i$  are selected as precision resistors for obtaining precise & scaled value of i/p voltage.

 


fig. Scale changer

### 2.3 Phase shift circuits:

- produce phase shift depends on frequency & maintain <sup>constant</sup> gain
- Also called as "Constant-delay filters" or "all pass filters."
- Diffr b/w i/p & o/p voltage remain constant when freq is changed over operating freq.

#### (a) Phase lag ckt

- Constructed by connecting both inverting & non-inverting modes
  - Assume i/p voltage  $V_i$  drive simple inverting amp
  - Inverting gain =  $-1$
  - Non-Inverting gain =  $1 + \frac{R_f}{R_i}$
- $$= 1 + 1 \\ = 2 \quad (\because R_f = R_i)$$

 


Fig. phase lag ckt

 


fig Bode plot for phase lag ckt

From ckt,

$$V_o(j\omega) = -V_i(j\omega) + 2 \frac{1}{1+j\omega RC} V_i(j\omega) \rightarrow ①$$

$$= V_i(j\omega) \left[ -1 + \frac{2}{1+j\omega RC} \right]$$

$$= V_i(j\omega) \left[ \frac{-1-j\omega RC + 2}{1+j\omega RC} \right]$$

$$\therefore V_o(j\omega) = V_i(j\omega) \left[ \frac{1-j\omega RC}{1+j\omega RC} \right]$$

The relationship b/w O/P & I/P can be expressed by

$$\frac{V_o(j\omega)}{V_i(j\omega)} = \frac{1-j\omega RC}{1+j\omega RC} \rightarrow ②$$

The phase angle is given by

$$\theta = -\tan^{-1}(\omega RC) - \tan^{-1}(\omega RC) = -2\tan^{-1}(\omega RC) \rightarrow ③$$

When  $\omega=0$ , phase angle approaches zero

$$\omega=\infty, \quad " \quad " \quad -180^\circ$$

$$\therefore ③ \Rightarrow \boxed{\theta = -2\tan^{-1}(f/f_c)} \rightarrow ④$$

$$\text{where, } f_c = \frac{1}{2\pi R C} \rightarrow ⑤$$

When  $f = f_c$  in eqn ④, phase angle  $\theta = -90^\circ$

(b) Phase-lead ckt

 
 


fig. phase-lead ckt

 
 


fig 1(b) Bode plot for phase-lead ckt

- Ckt  $\Rightarrow$  RC ckt form high pass nw
- O/P voltage  $v_o$  derived by

$$v_o(j\omega) = -v_i(j\omega) + 2 \left( \frac{j\omega RC}{1+j\omega RC} \right) v_i(j\omega)$$

$$\therefore \frac{v_o(j\omega)}{v_i(j\omega)} = \frac{-1 + j\omega RC}{1 + j\omega RC} \rightarrow \textcircled{6}$$


Eqn \textcircled{6}  $\rightarrow$  ratio of magnitude is constant & phase is obtained as in eqn \textcircled{3}. It is to be noted that Nr has a -ve real part & overall phase is

$$\begin{aligned} \theta &= 180^\circ - \tan^{-1}(\omega RC) - \tan^{-1}(\omega RC) \\ &= 180^\circ - 2\tan^{-1}(\omega RC) \rightarrow \textcircled{7} \end{aligned}$$

- Frequency  $\rightarrow 0$ , phase angle  $\rightarrow 180^\circ$
- Freq  $\uparrow$ , leading phase  $\downarrow$  & finally  $\rightarrow 0$  at high freq
- Eqn \textcircled{7}  $\rightarrow \boxed{\theta = 180^\circ - 2\tan^{-1}(f/f_0)}$   $\rightarrow \textcircled{8}$

where,  $f_0 = \frac{1}{2\pi RC}$

#### 4 Voltage follower :-

 

(3)

- If  $R_i = \infty$ ,  $R_f = 0$  in non-inverting amplifier, then amplifier acts as a unity-gain amplifier or voltage follower

$$\text{i.e } A_V = 1 + \frac{R_f}{R_i} \quad (\text{or}) \quad \frac{R_f}{R_i} = A_V - 1$$

Since,  $\frac{R_f}{R_i} = 0$ , we have  $A_V = 1$

- O/P voltage = I/P voltage, both in magnitude & phase ( $V_o = V_i$ )
- Sine o/p follows i/p voltage, it is called as Voltage follower
- Also referred as source follower, buffer amplifier, isolation amplifier, unity gain amplifier
- High i/p impedance of  $M\Omega$ , low o/p impedance
- Used as a buffer b/w a high impedance source & a low impedance matching applications


## 2.5 V-to-I and I-to-V converters:

### (a) Voltage to current converter (Transconductance amplifier)


To convert voltage signal to a proportional o/p current, 2 types of circuits can be considered

(i) V-I converter with floating load

(ii) V-I converter with grounded ..

 

fig(a) floating load

 

fig(b) grounded load

→ Fig(a) shows voltage to current converter in which load is shorted.

Voltage at node 'a' is  $v_i$

$$v_i = i_L R_1 \quad (\text{as } I_B = 0)$$

$$(a) \quad i_L = \frac{v_i}{R_1}$$

- O/p voltage  $v_i$  is converted as o/p current as  $i_L/R_1$

→ Fig(b) shows V-I converter with grounded load. Let  $v_o$  be the voltage at node 'a'

$$\text{Apply KVL} \Rightarrow i_1 + i_2 = i_L$$

$$\frac{v_i - v_1}{R} + \frac{v_o - v_1}{R_2} = i_L$$

$$v_o - 2v_1 + v_o = i_L R$$

$$v_1 = \frac{v_i + v_o - i_L R}{2}$$

∴ op-amp is in non-inverting mode, gain is  $1 + \frac{R}{R} = 2$

$$\text{The o/p voltage, } v_o = 2v_1 = v_i + v_o - i_L R$$

$$\text{that is, } v_i = i_L R$$

$$\Rightarrow i_L = v_i / R$$


(b) Current to voltage converter (Transresistance amplifier)

- Photo cell, photodiode, photovoltaic cell gives an o/p current that is proportional to incident radiant energy / light

Current through these devices is converted to voltage using I to V converter, thereby light is measured.

- Op-amp is used as I to V converter

 • '−' i/p terminal → virtual ground, no current flow through  $R_S$  &  $i_S$  current flows through feedback resistor  $R_F$



- $V_o = I_s R_f$
- lowest current that this ckt can measure will depend upon bias current  $I_B$  of op-amp i.e.  $\mu A 741$  ( $I_B = 30\text{nA}$ ) can be used to detect lower current
- sometimes,  $R_f$  is shunted with capacitor  $C_f$  to reduce high frequency noise & possibility of oscillation

## 2.6 Adder / Summing Amplifier

- Op-amp maybe used to design a ckt whose o/p is sum of several i/p signals which is known as "Summing amplifier" or "Summer"
- Inverting & non-inverting Summer are discussed as follows.

### (a) Inverting summing amplifier

- summing amplifier with 3 i/p voltage  $v_1, v_2, v_3$ , 3 i/p resistors  $R_1, R_2 \& R_3$  and a feedback resistor  $R_f$  is shown below

 


fig. Inverting summing amplifier

- On analysing, assume op-amp is ideal. i.e.  $A_{OL} = \infty, R_i = \infty$
- i/p bias current assumed to be zero, no voltage drop across  $R_{\text{comp}}$
- non-inverting terminal is grounded
- Voltage at node "a" is zero as non-inverting terminal is grounded

Nodal eqn. by KCL at "a"

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} + \frac{V_o}{R_f} = 0$$

$$V_o = - \left[ \frac{V_1 R_f}{R_1} + \frac{V_2 R_f}{R_2} + \frac{V_3 R_f}{R_3} \right]$$

- Thus o/p is inverted & weighted sum of i/p's. In special case, when  $R_1 = R_2 = R_3 = R_f$ , we have

$$\boxed{V_o = -(V_1 + V_2 + V_3)}$$

In which o/p is inverted sum of i/p signals. We may also set

$$R_1 = R_2 = R_3 = 3R_f, \text{ in which}$$

$$\boxed{V_o = -\left(\frac{V_1 + V_2 + V_3}{3}\right)}$$

- Thus o/p is average of i/p signal (inverted)

Effective resistance,  $R_i = R_1 \parallel R_2 \parallel R_3$


$$R_{\text{comp}} = R_i \parallel R_f = R_1 \parallel R_2 \parallel R_3 \parallel R_f$$

### (b) Non-inverting summing amplifier:

- Summer that gives a non-inverted sum is non-inverting summing amplifier.
- Let voltage at '-' i/p terminal be  $V_a$
- Voltage at '+' i/p terminal also  $V_a$
- The nodal eqn at node 'a' is given by

$$\frac{V_1 - V_a}{R_1} + \frac{V_2 - V_a}{R_2} + \frac{V_3 - V_a}{R_3} = 0$$
 
$$\Rightarrow \boxed{V_a = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}}$$



- The op-amp & 2 resistors  $R_f$  &  $R$  constitute a non-inverting amplifier

$$\text{with } V_o = \left(1 + \frac{R_f}{R}\right) V_a$$

$$\therefore \text{o/p voltage is } \boxed{V_o = \left(1 + \frac{R_f}{R}\right) \frac{\left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}\right)}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}\right)}}$$

which is non-inverted weighted sum of i/p

$$\text{Let } R_1 = R_2 = R_3 = R = R_f/2$$

$$\text{then, } \boxed{V_o = V_1 + V_2 + V_3}$$

A basic diff amplifier, used as a Subtractor is shown.

 


fig Subtractor

- If all resistors are equal, o/p voltage derived by using Superposition principle
- O/P  $V_{o1}$  due to  $v_1$  make  $v_2 = 0$ . ckt becomes non-inverting amplifier having i/p voltage  $v_1/2$  at non-inverting i/p terminal & o/p becomes

$$V_{o1} = \frac{v_1}{2} \left(1 + \frac{R_f}{R}\right) = v_1$$

- Wing O/P  $V_{o2}$  due to  $v_2$  is


$$V_{o2} = -v_2$$

$\therefore$  o/p voltage due to both i/p can be written as

$$\boxed{V_o = V_{o1} + V_{o2} = v_1 - v_2}$$
 
### Adder-Subtractor

- To perform addition & subtraction with single op-amp using the ckt shown.



fig(a) Op-amp adder-subtractor

 
 
 


fig (b) Simplifier ckt for  $V_2 = V_3 = V_4 = V_o$

- The o/p voltage can be obtained by "Superposition Theorem". To find o/p voltage  $V_{01}$  due to  $V_1$ , make all other i/p voltage  $V_2, V_3 \& V_4 = 0$ . Fig(b) is the simplified ckt of an inverting amplifier & o/p voltage is,

$$\frac{V_{01}}{(V_1, V_2)} = \frac{R}{R/2} \quad (\because \frac{V_o}{V_i} = -R_f/R)$$

$$\Rightarrow V_{01} = -\frac{R}{R/2} \cdot \frac{V_1}{2} = -V_1$$

- Similarly by Thevenin's theorem,

$$V_{02} = -V_2$$

- $V_{03}$  due to  $V_3$ , make other  $V_1, V_2, V_4 = 0$ . The voltage  $V_a$  at non-inverting terminal is,

$$V_a = \frac{R/2}{R+R/2} \cdot V_3 = \frac{V_3}{3}$$

- o/p voltage  $V_{03}$  due to  $V_3$  alone is

$$V_{03} = \left[ 1 + \frac{R}{R/2} \right] V_a = 3 \left( \frac{V_3}{3} \right) = V_3$$

- Similarly  $V_{04}$  due to  $V_4$  is  $V_{04} = V_4$

- Thus o/p voltage  $V_o$  due to all 4 i/p voltages is given by

$$V_o = V_{01} + V_{02} + V_{03} + V_{04}$$

$$= -V_1 - V_2 + V_3 + V_4$$

$$= (V_3 + V_4) - (V_1 + V_2)$$

: The ckt is an adder-subtractor


 


fig ckt for  $V_1 = V_2 = V_4 = 0$

 


### 2.8 Instrumentation Amplifier:-

- In industrial / consumer applications, we need to measure & control physical quantities. Some examples are measurement & control of temperature, humidity, light intensity, water flow, etc which are measured with the help of transducers. The o/p of transducer has to be amplified so that it can drive the indicator or display. This fn is performed by an instrumentation amplifier.

- The important features of Instrumentation amp are
  - high gain accuracy
  - high CMRR
  - high gain stability with low temperature co-efficient
  - low dc offset
  - low OIP impedance, (vi) high IIP Impedance

 ① Consider basic differential amp as shown below



DA using single op. amp

$$\text{OIP Voltage } \ddot{V}_o = -\frac{R_2}{R_1} V_2 + \frac{1}{1 + \frac{R_3}{R_4}} V_1 \left( 1 + \frac{R_2}{R_1} \right)$$

$$V_{o2} = -\frac{R_2}{R_1} V_2 \quad \rightarrow ①$$

$$V_{o1} = \left( 1 + \frac{R_2}{R_1} \right) V_a \quad \rightarrow ②$$

$$\text{where, } V_a = \frac{R_4}{R_3 + R_4} V_1 \quad \rightarrow ③$$

$$③ \text{ in } ② \quad V_{o1} = \left( 1 + \frac{R_2}{R_1} \right) V_1 \left( \frac{R_4}{R_3 + R_4} \right) \rightarrow ④$$

$$\text{We know OIP voltage } \ddot{V}_o = V_{o1} + V_{o2} \rightarrow ⑤$$

Sub ① & ④ in ⑤.

$$\begin{aligned} V_o &= -\frac{R_2}{R_1} V_2 + \left( 1 + \frac{R_2}{R_1} \right) V_1 \left( \frac{R_4}{R_3 + R_4} \right) \\ &= -\frac{R_2}{R_1} V_2 + \left( 1 + \frac{R_2}{R_1} \right) V_1 \left( \frac{1}{\frac{R_3 + R_4}{R_4}} \right) \\ &= -\frac{R_2}{R_1} V_2 + \left( 1 + \frac{R_2}{R_1} \right) V_1 \left( \frac{1}{\frac{R_3}{R_4} + 1} \right) \\ V_o &= -\frac{R_2}{R_1} \left[ V_2 - \left( \frac{R_1}{R_2} + 1 \right) V_1 \left( \frac{1}{\frac{R_3}{R_4} + 1} \right) \right] \end{aligned} \rightarrow ⑥$$

$$\text{If } \frac{R_1}{R_2} = \frac{R_3}{R_4}$$

$$\Rightarrow V_o = -\frac{R_2}{R_1} \left[ V_2 - \left( \frac{R_1}{R_2} + 1 \right) \left( \frac{1}{\frac{R_1}{R_2} + 1} \right) V_1 \right]$$

$$\boxed{V_o = -\frac{R_2}{R_1} (V_2 - V_1) = \frac{R_2}{R_1} (V_1 - V_2)} \rightarrow ⑦$$

## Drawbacks of single RA IA:

(i)  $R_1 = R_3$  &  $R_2 = R_4$

o/p voltage  $\Rightarrow (R_3 + R_4)$  for  $V_1$   
 $R_1$  for  $V_2$


$$(R_3 + R_4) \gg R_1$$

o/p  $V_1$  is heavily loaded bcz of low impedance

(ii) gain  $R_2/R_1$  is insufficient for high gain applications

## ② Three op amp or improved instrumentation amplifier.

fig Improved IA

 

• op-amp  $A_1, A_2$ :  $V_d = 0$ , for  $V_1 = V_2$  i.e under common mode,

Voltage across 'R' is zero

(a) no current flow through  $R$  &  $R'$ ,  $A_1$  acts as voltage follower

$$\therefore V_1' = V_1 \text{ & } V_2' = V_2$$

(b) If  $V_1 \neq V_2$ , current flows through  $R$  &  $R'$ ,  $(V_2' - V_1') > (V_2 - V_1)$

high CMRR

• Voltage at '+' terminal of  $A_3$   $\boxed{V_{O2} = \frac{R_2}{R_1+R_2} V_2'}$  (Superposition theorem)

$$\text{Here, } V_{O2} = -\frac{R_2}{R_1} V_2' \rightarrow ⑨$$

$$V_{O1} = \left(1 + \frac{R_2}{R_1}\right) V_a \rightarrow ⑩$$

$$\text{Sub } ⑨ \text{ in } ⑩ \Rightarrow V_{O1} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_2}{R_1+R_2}\right) V_2' \rightarrow ⑪$$

$$\therefore \text{o/p voltage } V_o = V_{O1} + V_{O2}$$

$$\Rightarrow V_o = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_2}{R_1+R_2}\right) V_1' - \frac{R_2}{R_1} V_2'$$

(7)

$$V_o = \frac{R_2}{R_1} V_2' + \left( \frac{R_1 + R_2}{R_1} \right) \left( \frac{1}{R_1 + R_2} \right) V_1'$$

$$= \frac{R_2}{R_1} V_2' + V_1' \frac{R_2}{R_1}$$

$$\boxed{V_o = \frac{R_2}{R_1} (V_1' - V_2')} \rightarrow (12)$$

(c) 'I' flows in 'R'  $\Rightarrow \boxed{I = (V_1 - V_2) / R} \rightarrow (13)$

$$V_1' = IR' + V_1 = R' \left( \frac{V_1 - V_2}{R} \right) + V_1$$

$$\boxed{V_1' = \frac{R'}{R} (V_1 - V_2) + V_1} \rightarrow (14)$$

$$V_2' = -IR' + V_2 = R' \left( \frac{V_1 - V_2}{R} \right) + V_2$$

$$\boxed{V_2' = -\frac{R'}{R} (V_1 - V_2) + V_2} \rightarrow (15)$$

WKT,  $V_o = \frac{R_2}{R_1} (V_1' - V_2')$  from eqn (12)

$$= \frac{R_2}{R_1} \left[ \left( \frac{R'}{R} (V_1 - V_2) + V_1 \right) - \left( -\frac{R'}{R} (V_1 - V_2) + V_2 \right) \right]$$

$$= \frac{R_2}{R_1} \left[ \frac{R'}{R} (V_1 - V_2) + V_1 + \frac{R'}{R} (V_1 - V_2) - V_2 \right]$$

$$= \frac{R_2}{R_1} \left[ 2 \frac{R'}{R} (V_1 - V_2) + (V_1 - V_2) \right]$$

$$\therefore \boxed{\{ V_o = \frac{R_2}{R_1} [(V_1 - V_2) [2 \frac{R'}{R} + 1]] \}} \rightarrow (16)$$

As the above eqn depends upon resistance, if we change the resistance value, the o/p voltage can be controlled.


Instrumentation Amplifier using transducer bridge.

③ Instrumentation Amplifier using transducer bridge whose resistance change

- ckt use resistive transducer,  $R_T$  whose resistance change physical qty to be measured.

- Bridge initially balanced by dc supply voltage  $V_{dc}$ , so  $V_1 = V_2$

fig IA using transducer bridge

 


- Physically changes, resistance  $R_T$  also changes

### Applications:


- ① Temperature indicator
- ② . controller
- ③ Light Intensity meter
- ④ analog weighing scale
- ⑤ measurement of flow of thermal conductivity

ICs represents IA are: LH 0036, μA725, TLC 7605, AD521, AD524  
AD624, etc

### 2.9 INTEGRATOR:

 

fig(a) Op-amp integrator

 

fig(b) freq response of a basic & lossy integrator

- One of simplest op-amp ckt. that consists of capacitor is integrator
- As name suggests it performs the mathematical function integration
- The nodal eqn at node "N" is analyzed as follows.

$$i = \frac{V_i - V_N}{R} = \frac{V_i - 0}{R} = \frac{V_i}{R} \rightarrow ①$$

$$\text{Also, } i = C \frac{d}{dt} (V_N - V_o) = C \frac{d}{dt} (-V_o) \rightarrow ②$$

Equating ① & ②

$$-C \frac{dV_o}{dt} = \frac{V_i}{R}$$

$$\frac{dV_o}{dt} = -\frac{V_i}{RC}$$

$$\text{Integrating, } \boxed{V_o = -\frac{1}{RC} \int V_i dt} \rightarrow ③$$

- Thus ckt provides o/p voltage proportional to time integral of i/p and  $RC$  is the time constant of integrator. The negative sign in o/p  $\rightarrow$  inverting indicator
- A simple RC low pass ckt can work as an integrator, when time constant is very large.
- The operation of integrator can be studied in frequency domain

$$V_o(s) = -\frac{1}{sRC} V_i(s) \rightarrow ④$$

In steady state, put  $\boxed{s=j\omega}$  we get

$$V_o(j\omega) = -\frac{1}{j\omega RC} V_i(j\omega) \rightarrow ⑤$$

So, the magnitude of gain or integrator transfer fn. is

$$|A| = \left| \frac{V_o(j\omega)}{V_i(j\omega)} \right| = \left| -\frac{1}{j\omega RC} \right| = \frac{1}{\omega RC} \rightarrow ⑥$$

(a) At  $\omega=0$ , magnitude  $\rightarrow \infty$


(b) At dc,  $\cdot 'c'$   $\rightarrow$  open ckt, no -ve feedback

Integrator doesn't face freq. problem as faced in differentiator

## Practical Integrator ckt (lossy integrator):

- Integrator gain at low freq. can be limited to avoid saturation
- Parallel combination of  $R$  and  $C$  behaves like practical capacitor
- It dissipates power unlike an ideal capacitor. For this reason, the ckt is called as "lossy integrator"

Analysis

 

The nodal eqn. is

$$\begin{aligned} \frac{v_i(s)}{R} + sC v_o(s) + \frac{v_o(s)}{R_f} &= 0 \\ \Rightarrow v_o(s) &= -\frac{v_i(s)}{R + R_f sC} = -\frac{1}{R} v_i(s) \\ v_o(s) \left( \frac{R_f sC + 1}{R_f} \right) &= -\frac{1}{R} v_i(s) \\ v_o(s) &= \frac{-R_f v_i(s)}{RR_f sC + R} = \frac{-R_f v_i(s)}{R_f [R s C + R/R_f]} \\ \therefore \boxed{v_o(s) &= -\frac{1}{sCR + R/R_f} v_i(s)} \end{aligned}$$

$$\Rightarrow |A| = \left| \frac{v_o}{v_i} \right| = \sqrt{\omega^2 R^2 C^2 + R^2 / R_f^2}$$

★

## 2. DIFFERENTIATOR:

- One of the simplest of op-amp ckt. that contain capacitor is the differentiating amplifier, or differentiator. As name suggests it perform mathematical operation "differentiation", i.e. o/p waveform is derivative of i/p waveform.

 


fig. Op-amp differentiator

Analysis:

The node 'N' is at virtual ground potential i.e.  $V_N = 0$

The node 'N' is at virtual ground potential i.e.  $V_N = 0$

The current through capacitor,  $i_C = C \frac{d}{dt} (V_i - V_N)$

$$= C \frac{d}{dt} (V_i - 0)$$

$$\boxed{i = C \frac{dV_i}{dt}} \rightarrow ①$$

The current through feedback resistor is,  $i = \frac{V_N - V_o}{R_f} = \frac{0 - V_o}{R_f}$

$$\boxed{i = \frac{-V_o}{R_f}} \rightarrow ②$$

Equating both current ① & ②

$$\frac{-V_o}{R_f} = C \frac{dV_i}{dt}$$

$$\Rightarrow \boxed{V_o = -R_f \frac{dV_i}{dt}} \rightarrow ③$$

Thus o/p voltage  $V_o$  is constant ( $-R_f C$ ) times the derivative of i/p voltage  $V_i$  and the ckt is called as "differentiator".

" $-$ " sign  $\rightarrow 180^\circ$  phase shift of the o/p waveform  $V_o$


" $-$ " sign  $\rightarrow 180^\circ$  phase shift of the o/p waveform  $V_o$

Phase equivalent of eqn. ③ is  $V_o(s) = -R_f C V_i(s)$


Put  $s = j\omega$  & magnitude can be return as

$$|A| = \left| \frac{V_o}{V_i} \right| = | -j\omega R_f C | = \omega R_f C \rightarrow ④$$

Freq response is  $|A| = f/f_a$ , where  $f_a = \frac{1}{2\pi R_f C}$

 

(a) practical differentiator

 

(b) freq response

- P D eliminates problem of instability & high freq noise
- The TF for the ckt is

$$\frac{V_o(s)}{V_i(s)} = -\frac{Z_f}{Z_1} = -\frac{sR_f C}{(1+sR_f C)(1+sCR)}$$

For  $\boxed{CR_f = CR}$ , we get  $\Rightarrow \frac{V_o(s)}{V_i(s)} = -\frac{sRC}{(1+sRC)^2} = -\frac{sRC}{(1+jf/f_b)^2} \rightarrow (5)$

where,  $f_b = \frac{1}{2\pi RC}$

normally connected to (+) i/p terminal

- A resistance  $R_{comp}$  is normally connected to (+) i/p terminal to compensate i/p bias ckt

A good differentiator may be designed as per below :-

(a) choose  $f_a = \text{highest freq of i/p signal}$

(b) choose  $f_b = 10 f_a$  (say) & calculate values of  $R$  and  $C_f$

$$\text{So } RC = R_f C_f$$

# LOGARITHMIC AMPLIFIER & ANTILOG AMPLIFIER

## Logarithmic amplifier:

[Transistor configuration]

Practical applications of logarithmic amplifier are signal mixing to find RMS value, square value, etc of signals.

The fundamental log-amp ckt is shown:

 


fig fundamental log-amp

- Here a grounded base transistor is in feedback path
- collector is at virtual ground. Ifp current is equal to  $I_c$
- i.e  $I_i = I_c \rightarrow ①$

- Collector current is given as

$$I_c = I_s (e^{V_{BE}/V_T} - 1) \quad \text{where } V_T = \frac{kT}{q}$$

$I_s$   $\rightarrow$  emitter saturation current

$k$   $\rightarrow$  Boltzmann's constant

$T$   $\rightarrow$  absolute temperature (in K)

- Since exponential term is far greater than 1, eqn ② becomes

$$I_c \approx I_s e^{V_{BE}/V_T} \rightarrow ③$$

- Here the base voltage becomes zero, hence  $V_{BE} \Rightarrow V_E$

$$I_c \approx I_s e^{V_E/V_T} \rightarrow ④$$

- Apply KCL at node,

$$I_i = \frac{V_i - V_N}{R} = \frac{V_i - 0}{R} = \frac{V_i}{R} \rightarrow ⑤$$

Equating ③ & ④

$$\Rightarrow \frac{V_i}{R} = I_s e^{V_E/V_T}$$

$$\frac{V_i}{I_s R} = e^{V_E/V_T} \rightarrow ⑥$$

Taking log on both sides,

$$\ln\left(\frac{V_i}{I_{SR}}\right) = \ln e^{\frac{V_F}{V_T}} \\ = \frac{V_F}{V_T} \rightarrow \textcircled{7}$$

therefore,  $V_F = V_T \ln\left(\frac{V_i}{I_{SR}}\right) \rightarrow \textcircled{8}$

Wk7, the magnitude of  $V_o$  &  $V_F$  are same but there is a  $180^\circ$  phase shift b/w them. Thus,  $\boxed{V_o = -V_F}$

then  $V_o = -V_T \ln\left(\frac{V_i}{I_{SR}}\right) \rightarrow \textcircled{9}$

OP Voltage is  $\boxed{V_o = -\frac{kT}{q} \ln\left(\frac{V_i}{V_{ref}}\right)} \rightarrow \textcircled{10} \quad (I_{SR} = V_{ref})$

### Problem Identification:

- This ckt has a problem. ' $I_s$ ' varies from transistor to transistor and with temperature.
- A stable  $N_{ref}$  can't be obtained.
- This is eliminated by the below ckt, temperature compensation Log-amp ckt

 


fig. Log-amp with saturation current & temp. compensation

Here  $V_1 = -V_t \ln(V_i/V_{ref})$   $\rightarrow$  (1)

Also,  $V_2 = -V_t \ln\left(\frac{V_{ref}}{I_s R_1}\right) \rightarrow$  (2)

$$\begin{aligned} \text{Whr } V_o &= V_2 - V_1 \\ &= -V_t \ln\left(\frac{V_{ref}}{I_s R_1}\right) + V_t \ln\left(\frac{V_i}{I_s R_1}\right) \\ &= +V_t \left[ -\ln\left(\frac{V_{ref}}{I_s R_1}\right) + \ln\left(\frac{V_i}{I_s R_1}\right) \right] = +V_t \ln\left(\frac{\frac{V_i}{I_s R_1}}{\frac{V_{ref}}{I_s R_1}}\right) \end{aligned}$$

$$\therefore \boxed{V_o = +V_t \ln\left(\frac{V_i}{V_{ref}}\right)} \rightarrow (3) \quad \text{where, } V_t = \frac{kT}{q}$$

Now o/p voltage of the ckt is,

Now o/p voltage of the ckt is,

$$V_{o\text{comp}} = \left(1 + \frac{R_f}{R}\right) V_i \quad (\text{by non-inverting amp})$$

$$\boxed{V_{o\text{comp}} = +\left(1 + \frac{R_2}{R_{TC}}\right) V_t \ln\left(\frac{V_i}{V_{ref}}\right)} \rightarrow (4)$$

$R_{TC} \rightarrow$  Temp. sensitive resistance  
When  $R_{TC}$  is chosen appropriate to  $V_t$ , the o/p voltage  
can be controlled stable.

- (b) Antilogarithmic amplifier
- The ckt shown is antilog amp for which i/p  $V_i$  is fed into temperature compensating voltage divider  $R_2$  &  $R_{TC}$  and then to base of  $\beta_2$ .
- o/p  $V_o$  is fed back to inverting i/p of  $A_1$  through  $R_1$


 


fig anti log amp

 

Apply KVL to  $\alpha_2$

$$V_B + V_{BE_2} = V_E_2 \rightarrow ①$$

Here,  $V_A = V_E_2$

$$① \Rightarrow V_B + V_{BE_2} = V_A \rightarrow ②$$

We have find these 3 voltages and they are as follows:

$$V_B = \frac{V_i R_{TC}}{R_2 + R_{TC}} \rightarrow ③$$

$$V_{BE_2} = -V_t \ln \frac{V_{ref}}{I_{SR}} \rightarrow ④$$

$$V_A = -V_t \ln \frac{V_o}{I_{SR}} \rightarrow ⑤$$

where  $V_t = \frac{kT}{q}$

Sub ③, ④ & ⑤ in ②

$$\frac{V_i R_{TC}}{R_2 + R_{TC}} + \left( -V_t \ln \frac{V_{ref}}{I_{SR}} \right) = -V_t \ln \frac{V_o}{I_{SR}}$$

$$\frac{V_i R_{TC}}{R_2 + R_{TC}} = V_t \ln \frac{V_{ref}}{I_{SR}} + V_t \ln \frac{V_o}{I_{SR}}$$

$$= -V_t \left[ -\ln \frac{V_{ref}}{I_{SR}} + \ln \frac{V_o}{I_{SR}} \right]$$

$$= -V_t \ln \frac{\frac{V_o}{I_{SR}}}{\frac{V_{ref}}{I_{SR}}}$$

$$= -V_t \ln \left( \frac{V_o}{V_{ref}} \right) \rightarrow ⑥$$

both sides by 0.4343, to change it to log

$$\Rightarrow 0.4343 \frac{V_i R_{TC}}{R_2 + R_{TC}} = -V_t \cdot 0.4343 \ln\left(\frac{V_o}{V_{ref}}\right)$$

$$\Rightarrow 0.4343 \frac{V_i R_{TC}}{R_2 + R_{TC}} = -V_t \log_{10}\left(\frac{V_o}{V_{ref}}\right)$$

$$\Rightarrow -\frac{1}{V_t} 0.4343 \frac{V_i R_{TC}}{R_2 + R_{TC}} = \log_{10}\left(\frac{V_o}{V_{ref}}\right) \rightarrow (7)$$

Substitute  $K' = \frac{1}{V_t} 0.4343 \frac{R_{TC}}{R_2 + R_{TC}}$  in (7)

$$\Rightarrow -K' V_i = \log_{10}\left(\frac{V_o}{V_{ref}}\right) \rightarrow (8)$$

Take antilog on both sides

$$\Rightarrow 10^{-K' V_i} = \frac{V_o}{V_{ref}}$$

$$\therefore \boxed{V_o = V_{ref} 10^{-K' V_i}} \rightarrow (9)$$

- . Therefore increase in i/p by 1V cause o/p to decrease by decade.

## 2.12 COMPARATORS:

- Comparator is a ckt which compares signal voltage of an op-amp with reference voltage at other i/p of op-amp
- It is open-loop op-amp with o/p  $\pm V_{sat} (= V_{cc})$

Two types:

- (a) Inverting comparator
- (b) non-inverting comparator

### (a) non-inverting comparator:

- $V_{ref}$  is applied to '-' terminal.
- $V_i$  is applied to '+' terminal
- o/p voltage  $V_o$  is at  $-V_{sat}$  for  $V_i < V_{ref}$

Take both sides by 0.4343, we change  $\ln \rightarrow \log$

$$\Rightarrow 0.4343 \frac{V_i R_{TC}}{R_2 + R_{TC}} = -V_t \cdot 0.4343 \ln \left( \frac{V_o}{V_{ref}} \right)$$

$$\Rightarrow 0.4343 \frac{V_i R_{TC}}{R_2 + R_{TC}} = -V_t \log_{10} \left( \frac{V_o}{V_{ref}} \right)$$

$$\Rightarrow -\frac{1}{V_t} 0.4343 \frac{V_i R_{TC}}{R_2 + R_{TC}} = \log_{10} \left( \frac{V_o}{V_{ref}} \right) \rightarrow (7)$$

Substitute  $K' = \frac{1}{V_t} 0.4343 \frac{R_{TC}}{R_2 + R_{TC}}$  in (7)

$$\Rightarrow -K' V_i = \log_{10} \left( \frac{V_o}{V_{ref}} \right) \rightarrow (8)$$

Take antilog on both sides

$$\Rightarrow 10^{-K' V_i} = \frac{V_o}{V_{ref}}$$

$\therefore \boxed{V_o = V_{ref} 10^{-K' V_i}} \rightarrow (9)$

- Therefore increase in i/p by 1V cause o/p to decrease by decade.

## 2.12 COMPARATORS:

- Comparator is a ckt which compares signal voltage of an op-amp with reference voltage at other i/p of op-amp
- It is open-loop op-amp with o/p  $\pm V_{sat}$  ( $= V_{cc}$ )

Two types:

- Inverting comparator
- non-Inverting comparator


### (a) non-inverting comparator:

- $V_{ref}$  is applied to '-' terminal.
- $V_i$  is applied to '+' terminal
- O/P voltage  $V_o$  is at  $-V_{sat}$  for  $V_i < V_{ref}$

- (1) Zero crossing detector (Sine to square wave generator)
- (2) Window detector
- (3) Time marker generator
- (4) Phase meter
 
### 2.13 SCHMITT TRIGGER:

- Also known as "Regenerative Comparator."
- If no feedback added to comparator, gain  $\rightarrow \infty$
- If loop gain  $-\beta A_{OL} = 1$ , gain with feedback  $A_{vf} = \infty$
- This results in abrupt (zero rise time) transition b/w  $V_o$ .
- The following fig. shows regenerative comparator.



Apply KCL at 'b'

$$I_1 = I_2 + I_3 \rightarrow \textcircled{1}$$

By ideal character of op-amp, input impedance  $= \infty \Rightarrow \frac{V_i}{I_f} = \frac{1}{0}$

$$\therefore I_2 = 0 \rightarrow \textcircled{2}$$

$$\text{Eqn } \textcircled{1} \Rightarrow I_1 = I_3 \rightarrow \textcircled{3}$$

$$\text{From ckt, } I_1 = \frac{V_b - V_o}{R_1}, \quad I_3 = \frac{V_{ref} - V_b}{R_2}$$

$$\therefore \frac{V_b - V_o}{R_1} = \frac{V_{ref} - V_b}{R_2}$$

$$\frac{V_b}{R_1} - \frac{V_o}{R_1} = \frac{V_{ref}}{R_2} - \frac{V_b}{R_2}$$

$$\frac{V_b}{R_1} + \frac{V_b}{R_2} = \frac{V_{ref}}{R_2} + \frac{V_o}{R_1}$$

$$\frac{V_b(R_2 + R_1)}{R_1 * R_2} = \frac{V_{ref} R_1 + V_o R_2}{R_1 * R_2}$$

$$\Rightarrow V_b(R_1 + R_2) = \frac{V_{ref} R_1 + V_o R_2}{R_1 + R_2}$$

$$\therefore V_b = \frac{V_{ref} R_1 + V_o R_2}{R_1 + R_2} \rightarrow (1)$$

As per ideal characteristics, op-amp should achieve perfect balance. i.e.  $V_d = 0 \Rightarrow \boxed{V_a = V_b} \rightarrow (2)$

From ckt,  $V_a = V_i \Rightarrow V_b = V_i \rightarrow (3)$

(6) in (4)  $\Rightarrow \boxed{V_i = \frac{V_{ref} R_1 + V_o R_2}{R_1 + R_2}} \rightarrow (7)$

- As i/p voltage is applied to (+) terminal & feedback voltage to (+) terminal,  $v_i$  triggers  $v_o$ , every time it exceeds certain voltage levels
- They are called as upper threshold & lower threshold voltage ( $V_{UT}$  &  $V_{LT}$ )
- Suppose  $V_o = +V_{sat}$ , then eqn (7) becomes


$$V_{UT} = \frac{V_{ref} R_1 + V_{sat} R_2}{R_1 + R_2} \rightarrow (8)$$

- For  $V_o = -V_{sat} \Rightarrow V_{LT} = \frac{V_{ref} R_1 - V_{sat} R_2}{R_1 + R_2} \rightarrow (9)$


- Now hysteresis voltage is

$$\boxed{V_H = V_{UT} - V_{LT}} \quad \text{problems}$$


$$= \frac{2 R_2 V_{sat}}{R_1 + R_2}$$

 

 Transfer characteristics  
(a) for  $V_i$  increasing



(b) for  $V_i$  decreasing

 

(c) composite i/p o/p curve

## 2.14: PRECISION RECTIFIER

- Major limitation of ordinary diode is that it can't rectify voltage.
- A ckt that acts like an ideal diode is designed by placing diode in feedback loop of an op-amp.
- When input voltage is higher than  $V_T$ , diode 'D' conducts, which is called as voltage follower, for i/p  $V_i > V_T/A_{OL}$  and  $V_o$  follows positive half cycle.
- When i/p voltage  $V_i$  is lesser, then Diode 'D' is off, this ckt is called as precision diode and some applications are
  - Half Wave rectifier
  - Full Wave rectifier
  - Peak-Value detector
  - clipper
  - clamper

Under precision rectifier, we will discuss half wave & full wave rectifier

### (a) Half Wave Rectifier (HWR)


 
 


fig (a) Ideal HWR


- I/P  $V_i \rightarrow +ve$ , diode  $D_1$  conducts, causing  $V_{on}$  to go negative side.  
∴  $D_2 \rightarrow$  reverse biased
- O/P voltage  $V_o$  is zero as i/p flows through  $D_1$ .
- For  $V_i < 0$ , diode  $D_2$  conducts and  $D_1$  is off, causing  $V_{on}$  to Positive side ∴  $D_2 \rightarrow$  forward biased.

- The i/p, o/p waveforms are shown in fig(b)
- The op-amp in the ckt must be a high speed op-amp since it alternates b/w open loop & closed loop operations.
- The limitation of this ckt is skew etc.
- The given ckt provides positive o/p if both diodes are reversed, then the input signal gets inverted and provide negative o/p.

### (b) Full Wave Rectifier (FWR)

 


fig(a) Precision FW

 


fig(b) Equivalent ckt for  $V_i > 0$

- For positive i/p i.e.  $V_i > 0$ , diode  $D_1$  is on,  $D_2$  is off. Both op-amp acts as inverter.  $\therefore [V_o = V_i]$

 - For negative i/p i.e.  $V_i < 0$ , diode  $D_1$  is off,  $D_2$  is on & its equivalent ckt is as follows.



fig(c) ckt for  $V_i < 0$

 

fig(d) equivalent ckt of fig(c)

Let o/p voltage  $v_o$  is  $v$   
Rkt at node  $V_A$

$$\frac{V_i}{R} + \frac{V}{2R} + \frac{v}{R} = 0$$



$$\frac{V_i}{R} + \frac{3v}{2R} = 0$$

$$\therefore v = -\frac{2}{3} V_i$$

$$\therefore \text{o/p voltage}, v_o = \left(1 + \frac{R}{2R}\right) \left(-\frac{2}{3} V_i\right) = -V_i$$


Hence for  $V_i < 0$ , o/p is negative positive.

  This ckt is also known as absolute value ckt. The i/p & o/p waveform are as follows:




fig(e) i/p & o/p waveform

## 2.15 PEAK DETECTOR:

 

(a) positive peak detector

 

(b) o/p  $v_o$  corresponding to arbitrary i/p  $v_i$ .


- The job of a peak detector is to compute the peak value of the input
- The ckt follows voltage peaks of a signal & stores highest value in a capacitor
- If a high peak signal value comes along, this new value is stored
- The highest peak value is stored until capacitor is discharged
- When  $v_i > v_c$ , voltage across capacitor ; diode 'D' is forward biased & ckt become voltage follower
- O/P  $v_o$  follows  $v_i$  as long as  $v_i$  exceeds  $v_c$
- When  $v_i < v_c$ , diode is in reverse biased & capacitor hold charge till  $v_i$  become greater than  $v_c$  ( $v_i > v_c$ )
- In the given ckt, it is noted that peak at time  $t'$  is missed
- Hence MOSFET reset switch is used to reset the ckt, across the capacitor
- Ckt can be modified to hold lowest voltage of a signal reversing the diode

Application:


- In test & measurement instrumentation
- Amplitude Modulation (AM) communication
 
## 2.16 CLIPPER:

- A precision diode may also be used to clip-off a certain portion of P/P signal to obtain desired O/P waveform




(a) positive clipper

 


(b) positive Vref

 (c) negative Vref


- clipping level is determined by  $V_{ref}$  and could be obtained from positive supply voltage  $V^+$
- it can be seen that portion of o/p voltage for  $V_o > V_{ref}$  are clipped off
- For i/p voltage,  $V_i \leq V_{ref}$ , diode  $D$  conducts
- op-amp works as voltage follower,  $V_o$  follows  $V_i$ , till  $V_i \leq V_{ref}$
- When  $V_i > V_{ref}$ ,  $V_{OA}$  is large and will drive ' $D$ ' into cut-off
- If  $V_{ref}$  is negative, then entire o/p waveform above  $V_{ref}$  will get clipped off as shown as follows: in fig a,b,c



fig(d) negative clipper

 


(e) negative  $V_{ref}$

 


(f) positive  $V_{ref}$

- positive clipper of fig(a) can be easily converted into a negative clipper by simply reversing diode ' $D$ ' and changing polarity of the reference voltage  $V_{ref}$
- negative clipper clips off negative parts of i/p signal below  $V_{ref}$
- ckt diagram of negative clipper & the expected waveform is shown in fig (d,e,f)

## 2.17 CLAMPER:

 


fig(a) peak clumper

 

 (b) waveform for  $-V_{ref}$

- clamper is also known as "inserter or restorer"
- ckt is used to add desired dc level to o/p voltage i.e. o/p voltage is clamped to desired dc level.
- If clamped dc level is positive, it is positive clamper
- If clamped dc level is negative, it is negative clamper
- Positive dc voltage applied at (+) terminal, which clamps peak of o/p waveform. o/p voltage is net result of ac/dc  $V_i$  at (-) & (+) terminals
- For positive  $V_{ref}$ ,  $V_i$  is positive, Diode 'D' is forward biased
- If signal  $V_i$  is applied at (-) terminal. During -ve half cycle Diode 'D' conducts, capacitor 'c' charge through diode 'D' to negative peak voltage  $V_{max}$ .
- During positive half cycle, 'D' is reverse biased & capacitor retains its previous voltage  $V_m$



(c) waveform for  $+V_{ref}$

- The negative peak clamping is obtained by reversing the diode 'D' and using negative reference voltage  $-V_{ref}$
- Resistor  $R$  is used for protecting op-amp against excessive discharge current from capacitor 'C' especially when dc voltage supply are switched off

## 2.18 ACTIVE FILTERS: ~~(\*)~~ ~~(\*)~~ ~~(\*)~~

Filters are used in ckt that pws require separation of signals according to their frequencies. They are widely used in communication & signal processing. The 3 configuration of active filters are



- ① Low pass filter (LPF)
- ② High pass filter (HPF)
- ③ Band pass filter (BPF)

### ① Low pass filter (LPF).

Active filters may be of different order and types. LPF can be classified as

- (a) First order low pass filter
- (b) Second order "
  
#### (a) First order LPF: ~~(\*)~~ ~~(\*)~~



fig(a) First ord LPF & its freq. response

As per given circuitry and given,

$$V_o(s) = \left(1 + \frac{R_f}{R_i}\right) V_i \rightarrow (1)$$

$$\text{to find } V_i(s) : V_i(s) = \frac{V_{sc}}{R + \frac{1}{sc}} \cdot V_o(s)$$

$$V_i(s) = \frac{1}{1 + sRC} V_o(s) \rightarrow (2)$$

(2) into (1)

$$V_o(s) = \left(1 + \frac{R_f}{R_i}\right) \frac{V_o(s)}{1 + sRC}$$

$$\frac{V_o(s)}{V_i(s)} = A_0 \frac{1}{1 + sRC} \rightarrow (3)$$

By Laplace transform,

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{A_0}{1 + sRC} \rightarrow (4)$$

$$\text{Let } \omega_h = \frac{1}{RC} \Rightarrow RC = \frac{1}{\omega_h}$$

$$\therefore H(s) = \frac{A_0}{1 + \frac{s}{\omega_h}} = \frac{A_0 \omega_h}{s + \omega_h} \rightarrow (5)$$

Put  $[s = j\omega]$  in (4)

$$H(j\omega) = \frac{A_0}{1 + j\omega RC} \rightarrow (6)$$

$$\text{Sub } [\omega = 2\pi f] \Rightarrow H(j\omega) = \frac{A_0}{1 + j2\pi f RC} \rightarrow (6)$$

$$\text{Here, } f_h = \frac{1}{2\pi RC}$$

$$H(j\omega) = \frac{A_0}{1 + j(f/f_h)} \rightarrow (7)$$

(i) At very low freq,  $f \ll f_h$  (passband)

$$|H(j\omega)| \approx A_0$$

(ii) At  $f = f_h$

$$|H(j\omega)| = \frac{A_0}{\sqrt{2}}$$

(greatest decreas)

(iii) At very high freq,  $f \gg f_h$

$$|H(j\omega)| \ll A_0 \approx 0$$

(stopband)

## (b) Second Order Active LPF (Scallen-key filter) (15)

- An improved filter response obtained using 2nd order active filter
- It consists of 2 pairs of RC combination and has a roll-off rate of 40 dB/decade

 


Fig. Scallen key filter

- A general 2nd order filter (Scallen-key) is shown in fig(a)
- It can be used for analysing LPF & HPF

The op-amp is connected as non-inverting amp, hence

$$v_o = \left(1 + \frac{R_f}{R_i}\right) v_B = A_o v_B \rightarrow ①$$

$$\rightarrow ② \quad (1)$$

$$\Rightarrow v_B = v_o / A_o$$

Node 'A' → apply KCL

$$(v_A - v_i) y_1 + (v_A - v_B) y_2 + (v_A - v_o) y_3 = 0$$

$$v_A y_1 - v_i y_1 + v_A y_2 - v_B y_2 + v_A y_3 - v_o y_3 = 0$$

$$v_A y_1 - v_i y_1 + v_A y_2 - v_B y_2 + v_A y_3 - v_o y_3 = 0$$

$$v_A (y_1 + y_2 + y_3) - v_i y_1 - v_B y_2 - v_o y_3 = v_i y_1 \rightarrow ③$$

$$v_A (y_1 + y_2 + y_3) - v_B y_2 - v_o y_3$$

$$\text{Sub } ② \text{ in } ③ \quad v_A (y_1 + y_2 + y_3) - \frac{v_o}{A_o} y_2 - v_o y_3 = v_i y_1 \rightarrow ④$$

$$v_A (y_1 + y_2 + y_3) - \frac{v_o}{A_o} y_2 - v_o y_3$$

$$= v_i y_1$$

$$\rightarrow ④$$

$$\text{KCL at 'B'} \quad (v_B - v_A) y_2 + (v_B - 0) y_4 = 0$$

$$(v_B - v_A) y_2 + v_B y_4 = 0$$

$$v_B y_2 - v_A y_2 + v_B y_4 = 0$$

$$v_B (y_2 + y_4) - v_A y_2 = 0$$

$$v_B (y_2 + y_4) = v_A y_2$$

$$\therefore v_A = \frac{v_B (y_2 + y_4)}{y_2}$$

$$\rightarrow ⑤$$

Sub ⑤ in ④


$$v_A = \frac{v_o (y_2 + y_4)}{A_o y_2} \rightarrow ⑥$$

Sub (6) in (7)

$$\begin{aligned}
 V_i Y_1 &= \frac{V_o}{A_o} \left( \frac{Y_2 + Y_4}{Y_2} \right) (Y_1 + Y_2 + Y_3) - \frac{V_o}{A_o} Y_2 - V_o Y_3 \\
 &= \frac{V_o (Y_2 + Y_4)}{A_o Y_2} (Y_1 + Y_2 + Y_3) - \frac{V_o Y_2^2}{A_o Y_2} - V_o A_o Y_3 Y_2 \\
 &= \frac{V_o}{A_o Y_2} [Y_1 Y_2 + Y_2^2 + Y_2 Y_3 + Y_1 Y_4 + Y_2 Y_4 + Y_3 Y_4 - Y_2^2 - A_o Y_3 Y_2] \\
 V_i Y_1 &= \frac{V_o}{A_o Y_2} [Y_1 Y_2 + Y_2 Y_3 (1 - A_o) + Y_4 (Y_1 + Y_2 + Y_3)] \\
 \frac{V_o}{V_i} &= \frac{A_o Y_1 Y_2}{Y_1 Y_2 + Y_2 Y_3 (1 - A_o) + Y_4 (Y_1 + Y_2 + Y_3)} \rightarrow (7)
 \end{aligned}$$

This gain formula for 2nd order active filter

Second order LPF :-

 

Sub  $Y_1 = Y_2 = \frac{1}{R}$ ;  $Y_3 = Y_4 = SC$  in (7)

$$\begin{aligned}
 \Rightarrow H(s) &= \frac{A_o \left( \frac{1}{R} \right) \left( \frac{1}{R} \right)}{\left( \frac{1}{R} \right) \left( \frac{1}{R} \right) + \left( \frac{1}{R} \right) (SC) (1 - A_o) + SC \left( \frac{1}{R} + \frac{1}{R} + SC \right)} \\
 &= \frac{A_o / R^2}{\frac{1}{R^2} + \frac{SC}{R} (1 - A_o) + SC \left( \frac{2}{R} + SC \right)}
 \end{aligned}$$

Taking LCM  $A_o / R^2$

$$H(s) = \frac{1}{\frac{1}{R^2} + \frac{SCR (1 - A_o)}{R^2} + SCR \left( \frac{2 + SRC}{R^2} \right)}$$

$$= \frac{A_o}{1 + SCR (1 - A_o) + SCR (2 + SRC)}$$

$$= \frac{A_o}{1 + SCR [1 - A_o + 2 + SRC]}$$

$$\Rightarrow H(s) = \frac{A_0}{1 + SRC(3 - A_0 + SRC)}$$

$$= \frac{A_0}{1 + SRC(3 - A_0) + (SRC)^2}$$

→ ⑧

If  $s = c \Rightarrow H(0) = A_0$

$s = \infty \Rightarrow H(\infty) = 0$

Let  $\omega_h = \frac{1}{RC}$  &  $\alpha = 3 \cdot A_0$

$$RC = \frac{1}{\omega_h}$$

$$H(s) = \frac{A_0}{1 + s(\frac{1}{\omega_h})\alpha + (\frac{s}{\omega_h})^2} \rightarrow ⑨$$

$$H(s) = \frac{A_0}{(\frac{s}{\omega_h})^2 + (\frac{s}{\omega_h})\alpha + 1} \rightarrow ⑩$$

Taking LCM

$$H(s) = \frac{A_0 \cdot \omega_h^2}{s^2 + s\omega_h\alpha + \omega_h^2}$$

Put  $[s = j\omega]$

$$H(j\omega) = \frac{A_0 \omega_h^2}{(j\omega)^2 + (j\omega)\omega_h\alpha + \omega_h^2}$$

$$= \frac{A_0}{\frac{(j\omega)^2}{\omega_h^2} + \frac{j\omega\omega_h\alpha}{\omega_h^2} + \frac{\omega_h^2}{\omega_h^2}}$$

$$= \frac{A_0}{\frac{-\omega^2}{\omega_h^2} + j \frac{\omega_h\alpha}{\omega_h} + 1}$$

Separating Real & imaginary terms,

$$H(j\omega) = \frac{A_0}{(1 - \frac{\omega^2}{\omega_h^2}) + j \frac{\omega_h\alpha}{\omega_h}} \quad \text{for } (a+ib) \propto e^{j\theta} \text{ if } b \neq 0$$

→ ⑪

$$\therefore |H(j\omega)| = \sqrt{1 + \left(\frac{\omega^2}{\omega_h^2}\right)^2 - \frac{2\omega^2}{\omega_h^2} + \frac{\omega^2\alpha^2}{\omega_h^2}}$$

Let  $S_n = \frac{\omega}{\omega_h}$  in eqn ⑨

$$H(S_n) = \frac{A_0}{1 + S_n\alpha + S_n^2}$$

→ damping coefficient  
 $\alpha \rightarrow \text{damping coefficient}$   
 $A_0 \rightarrow \text{gain}$   
 $\omega_h \rightarrow \text{upper cut off frequency}$   
 in radian/sec

 


Fig. 2<sup>nd</sup> order LPF response for different damping

Ans.

for Butterworth filters,  $\boxed{A = 1.414}$  from fig

Sub A in eqn (1)

$$|H(j\omega)| = \sqrt{1 + \left(\frac{\omega}{\omega_h}\right)^2 - \frac{2\omega^2}{\omega_h^2} + \frac{\omega^2}{\omega_h^2}(1.414)^2}$$

$$= \sqrt{1 + \left(\frac{\omega}{\omega_h}\right)^2 - \frac{2\omega^2}{\omega_h^2} + \frac{2\omega^2}{\omega_h^2}}$$


$$|H(j\omega)| = \frac{A_0}{\sqrt{1 + \left(\frac{\omega}{\omega_h}\right)^2}} \rightarrow (13)$$

For 2nd order eqn (3) can be expressed as

$$|H(j\omega)| = \frac{A_0}{\sqrt{1 + \left(\frac{\omega}{\omega_h}\right)^2 \times 2}} \rightarrow (14)$$

For n<sup>th</sup> order, it is expressed as

$$|H(j\omega)| = \frac{A_0}{\sqrt{1 + \left(\frac{\omega}{\omega_h}\right)^{2n}}} \rightarrow (15)$$

 

(\*) Design procedure for 2nd order Butterworth LPF (for problems)

① choose a value of higher cut off freq 'f<sub>h</sub>'

② Let  $R_2 = R_3 = R$  &  $C_2 = C_3 = C$

→ choose any value of C  $\leq 1\mu F$

→ Then find 'R' value using

$$f_h = \frac{1}{2\pi\sqrt{R_2 R_3 C_2 C_3}} = \frac{1}{2\pi R C}$$

$$\Rightarrow R = \frac{1}{2\pi f_h C}$$

③ calculate pass band gain required to achieve BW response

$$A_0 = 3 - \alpha$$

$$\alpha = (1.414)$$

$$\Rightarrow A_0 = 3 - 1.414 = 1.586$$

$$\text{WKT, gain } A_0 = 1 + \frac{R_f}{R_i} \Rightarrow$$

$$\begin{cases} 1 + \frac{R_f}{R_i} = 1.586 \\ \frac{R_f}{R_i} = 0.586 \end{cases}$$

$$\therefore \boxed{R_f = 0.586 R_i}$$

(A) choose value of  $k_1 \leq 100 k^2$   
Find  $R_f$  using ab vir eqn in 4<sup>th</sup> step

Select  $R_L = 12k\Omega$

(B) calculate gain magnitude (or) freq response from  $\left( \frac{V_o}{V_{in}} \right)$

## (2) High Pass Active Filter

- High pass is complement of LPF
- It is obtained by exchanging  $R$  and  $C$  in LPF circuit

 


fig 2<sup>nd</sup> order HPF

Put  $Y_1 = Y_2 = SC$  ;  $Y_3 = Y_4 = \frac{1}{R}$  in eqn (7)

$$H(s) = \frac{A_0 (SC)(SC)}{(SC)^2 + (SC)\left(\frac{1}{R}\right)(1-A_0) + \frac{1}{R}(SC + SC + \frac{1}{R})} \rightarrow (17)$$

After further simplification, the transfer function is

$$H(s) = \frac{A_0 s^2}{s^2 + (3 - A_0) \omega_1 s + \omega_1^2} \rightarrow (18)$$

where,  $\omega_1 = 1/Rc$


$$(or) H(s) = \frac{A_0}{1 + \frac{\omega_1}{s} (3 - A_0) + \left(\frac{\omega_1}{s}\right)^2 \left(\frac{\omega_1}{s}\right)^2} \rightarrow (19)$$

For  $\omega = 0 \Rightarrow H(s) = 0$

$\omega = \infty \Rightarrow H(s) = A_0$

The lower cut-off frequency is

$$f_L = f_{3dB} = \frac{1}{2\pi RC}$$

 

Putting value in (1) and  $\omega = \omega_0$  we get  
the voltage gain magnitude eqn of II order HPF is

$$|H(j\omega)| = \left| \frac{V_o}{V_i} \right| = \frac{A_0}{\sqrt{1 + (f_u/f)^4}} \rightarrow (20)$$

Hence,  $\left| \frac{H(j\omega)}{A_0} \right| = \frac{1}{\sqrt{1 + \left(\frac{f_u}{f}\right)^4}} \rightarrow (21)$

For 2nd order HPF, the expression can be written as

$$\boxed{\left| \frac{H(j\omega)}{A_0} \right| = \frac{1}{\sqrt{1 + (f_u/f)^{2 \times 2}}}} \rightarrow (22)$$

For n<sup>th</sup> order HPF, it is

$$\boxed{\left| \frac{H(j\omega)}{A_0} \right| = \frac{1}{\sqrt{1 + (f_u/f)^{2n}}}} \rightarrow (23)$$

### (3) Band pass filter:

There are 2 types of BPF as per quality factor  $Q$

(a) Narrow band pass filter ( $Q > 10$ )

(b) Wide " ( $Q < 10$ )

The following relationship is important

$$Q = f_0 / BW = f_0 / (f_h - f_l)$$

where  $f_0 = \sqrt{f_h f_l}$

$f_0 \rightarrow$  central freq

$f_h \rightarrow$  upper cut-off freq

$f_l \rightarrow$  lower cut-off freq

### (a) Narrow Band Pass filter:

Important parameters of BPF are

→ upper & lower cut off freq ( $f_h$  &  $f_l$ )


→ Band width (BW)

→ central freq ( $f_0$ )


→ Central freq. gain ( $A_0$ )

→ Selectivity ( $Q$ )

 • Circ has 2 feedback path & op-amp is in inverting mode



fig(b) 2nd order BPF

 

fig(a) Band-pass Configuration.

Apply KCL at node 'A' in fig(a)

$$(V_A - V_i)y_1 + (V_A - V_B)y_2 + (V_A - V_o)y_3 + V_A y_4 = 0$$

$$V_A y_1 - V_i y_1 + V_A y_2 - V_B y_2 + V_A y_3 - V_o y_3 + V_A y_4 = 0$$

$$V_A[y_1 + y_2 + y_3 + y_4] - V_i y_1 - V_o y_3 = 0 \quad (\because V_B = 0, \text{ the term } V_B y_2 = 0)$$

$$\therefore V_i y_1 + V_o y_3 = V_A(y_1 + y_2 + y_3 + y_4) \rightarrow (24)$$

KCL at node 'B'

$$(V_B - V_A)y_2 + (V_B - V_o)y_5 = 0$$

$$-V_A y_2 - V_o y_5 = 0 \quad (\because V_B = 0)$$

$$\Rightarrow V_B y_2 = -V_o y_5$$

$$\therefore \boxed{V_A = -V_o \frac{y_5}{y_2}} \rightarrow (25)$$

Sub (25) in (24)

$$V_i y_1 + V_o y_3 = -\frac{V_o y_5 (y_1 + y_2 + y_3 + y_4)}{y_2}$$

$$V_i y_1 = -\frac{V_o [y_1 y_5 + y_2 y_5 + y_3 y_5 + y_4 y_5]}{y_2} - V_o y_3$$

$$V_i y_1 = -\frac{V_o (y_1 y_5 + y_2 y_5 + y_3 y_5 + y_4 y_5)}{y_2} - V_o y_3 y_2$$

$$V_i y_1 = -\frac{V_o [y_1 y_5 + y_2 y_5 + y_3 y_5 + y_4 y_5 + y_2 y_3]}{y_2}$$

$$\Rightarrow \frac{V_o}{V_i} = -\frac{y_2 y_3}{y_1 y_5 + y_2 y_5 + y_3 y_5 + y_4 y_5 + y_2 y_3} \rightarrow (26)$$

For this cut to be BPI put  $V_1 = G_{11}V_1 + G_{12}V_2$ ,  $V_2 = G_{21}V_1 + G_{22}V_2$

The transfer function becomes

$$H(s) = \frac{V_o(s)}{V_i(s)} = -G_{11}C_1$$

$$V_i(s) = (G_{11} + G_{12}G_2 + G_{21}G_1 + G_{22})V_1 + G_{12}V_2$$

$$= G_{11}C_1$$

$$(G_{11} + G_{12}G_2 + G_{21}G_1 + G_{22})V_1 + G_{12}(V_1 + V_2)$$

$$= G_{11}C_1$$

$$G_{11}C_1 + G_{12}(C_1 + C_2) + G_{21}(C_1 + C_2) + G_{22}C_2$$

$$H(s) = \frac{-G_1}{G_{11} + G_{12}G_2 + G_{21}G_1 + G_{22}} \rightarrow (27)$$

The cut is gain equivalent of a parallel RLC cut of BPI driven by current source  $G_1V_1$  and with Bode plot characteristics as in fig (d).

The gain expression,  $\frac{V_o(s)}{V_i(s)} = -\frac{G_1}{4} = -\frac{G_1}{G_1 + G_2 + 1/sL} \rightarrow (28)$

 


Fig (c) Parallel RLC cut

 


Fig (d) Bode plot characteristics

Comparing gain expression in (27) & (28)

$$G_1 = G_1 \quad \rightarrow (29)$$


$$L = \frac{C_2}{G_2(G_1 + G_2)} \quad \rightarrow (30)$$

$$G_1 = \frac{G_2(G_1 + G_2)}{C_2} \quad \rightarrow (31)$$

$$1/C = C_2 \quad \rightarrow (32)$$

For instance, the cut fig (c) has unity power factor i.e. imaginary part is zero which gives resonant freq as
 
$$\omega_0^2 = \frac{1}{LC} = G_2 \frac{(G_1 + G_2)}{C_2} \quad \rightarrow (33)$$



for high pass section, the magnitude of gain is

$$|H_{HPF}| = \left| \left( 1 + \frac{R_F}{R_1} \right) \left( \frac{j 2\pi f R_2 C_2}{1 + j 2\pi f R_2 C_2} \right) \right| = \left| A_{01} \frac{j(f/f_J)}{1 + j(f/f_J)} \right| = \frac{A_{01} (f/f_J)}{\sqrt{1 + (f/f_J)^2}}$$

where,  $f_J = \frac{1}{2\pi R_2 C_2}$

Similarly for low pass section,

$$|H_{LPF}| = \frac{A_{02}}{\sqrt{1 + (f/f_h)^2}}$$

where,  $f_h = \frac{1}{2\pi R_1 C_1}$

The voltage gain magnitude of BPF is product of HPF  $\times$  LPF  
The freq response can be calculated from

$$\left| \frac{V_o}{V_i} \right| = \frac{A_{01} (f/f_J)}{\sqrt{[1 + (f/f_J)^2] [1 + (f/f_h)^2]}}$$

where total pass band gain  $A_o = A_{01} \times A_{02}$

To obtain  $-A_{02}$  dB/decade roll-off, II order LPF & HPF

Should be cascaded

The gain at resonance is

$$\left. \frac{V_o}{V_i} \right|_{\omega=\omega_0} = -\frac{G_1'}{G_1} - \frac{G_1}{G_1} = -\frac{(G_1/G_5)C_2}{C_2 + C_3}$$

$$= -\frac{(R_5/R_1)C_2}{C_2 + C_3}$$

The Q-factor is

$$Q_0 = \frac{\omega_0 L}{R} = \omega_0 R C = \frac{\omega_0 C}{G_1} = \frac{\omega_0 C_2 C_3}{(C_2 + C_3) G_5}$$

The bandwidth is given by

$$\text{BW} = f_h - f_l = \frac{f_0}{Q_0} = \frac{\omega_0}{2\pi Q_0} = \frac{\omega_0}{2\pi R C_0}$$

$$= \frac{1}{2\pi R C} = \frac{G_1}{2\pi C} = \frac{G_5(C_2 + C_3)}{2\pi C_2 C_3}$$

and  $f_0 = \sqrt{f_h f_l}$

For  $C_2 = C_3 = C$ , the gain from eqn 32 is

$$\left. \frac{V_o}{V_i} \right|_{\omega=\omega_0} = -\frac{R_5}{2R_1} = -A_0 \rightarrow 37$$

$$\omega_0 = \frac{\sqrt{G_5(G_1 + G_4)}}{C} \rightarrow 38$$

$$\text{BW} = \frac{G_5}{\pi C} = \frac{1}{\pi R_5 C} \rightarrow 39$$

Above 3 eqn are gain at resonance, resonance freq. & bandwidth

Using eqn 35, 37 is 38 in eqn 27, transfer fn becomes:

$$H(s) = \frac{-A_0(\omega_0/\omega)s + \omega_0^2}{s^2 + (\omega_0/\omega)s + \omega_0^2} \rightarrow 40$$

$$= \frac{-A_0 \alpha \omega_0 s}{s^2 + \alpha \omega_0 s + \omega_0^2} \rightarrow 41$$

For  $\omega \ll \omega_0$  and  $\omega \gg \omega_0 \Rightarrow \text{gain} = 0$

$\omega = \omega_0$ , gain =  $A_0$

### Analog multipliers: [Analog Multipliers]

It is most commonly used technique & integrated ckt component for performing non-linear operations on signals. Gilbert multiplier cell forms basis of a wide variety of ckt.  $V_o = KV_2 V_4$

Common terminologies associated with multiplier characters:


① Accuracy : derivation of actual o/p from ideal o/p

② Linearity : defines accuracy of multiplier

③ Squaring mode accuracy

④ Bandwidth

 1.1 Analog Multiplier Using Emitter Coupled Transistor pair



$$I_E = I_C [1 + e^{-V_E/V_T}]$$

fig. Emitter coupled transistor pair

The o/p currents  $I_{c1}$  and  $I_{c2}$  are related to  $V_1$  is given

$$I_{c1} = \frac{I_{EE}}{1 + e^{-V_1/V_T}} \rightarrow ①$$

$$I_{c2} = \frac{I_{EE}}{1 + e^{V_1/V_T}} \rightarrow ②$$

where  $V_T$  is thermal voltage.

$I_{B1}$  &  $I_{B2}$  are neglected

 


fig (b) Simple modulator using differential amp

From ① & ②


$$\Delta I_C = I_{C1} - I_{C2}$$

$$= \frac{I_{FE}}{1 + e^{-V_1/V_T}} - \frac{I_{FE}}{1 + e^{V_1/V_T}}$$

$$= I_{FE} \left[ \frac{1}{1 + e^{-V_1/V_T}} - \frac{1}{1 + e^{V_1/V_T}} \right]$$

$$\therefore \Delta I_C = I_{FE} \tanh \left( \frac{V_1}{2V_T} \right) \rightarrow ③$$

 The dc transfer characteristics of Emitter-coupled transistor pair is given



$$\text{When } V_1 \ll V_T, \quad I_{FE} \tanh \left( \frac{V_1}{2V_T} \right) = I_{FE} \frac{V_1}{2V_T} \rightarrow ④$$


$$\Delta I_C = I_{FE} \left( \frac{V_1}{2V_T} \right) \rightarrow ⑤$$

Thus eqn. ③ becomes,

$\rightarrow$  If  $I_{FE}$  is proportional to 2nd i/p. signal  $V_2$  then

$$I_{FE} \approx k_o [V_2 - V_{BE(on)}] \rightarrow ⑥$$
 
$$\text{Sub } ⑥ \text{ in } ⑤, \quad \Delta I_C = \frac{k_o V_1 [V_2 - V_{BE(on)}]}{2V_T} \rightarrow ⑦$$



There are 2 limitations in this:

①  $V_2$  is offset by  $V_{BE(on)}$     ②  $V_2$  must always be positive.

③  $\tanh(x)$  is approximated as 'x'.  
To overcome 1st & 2nd limitation Gilbert multiplier cell is used

### 12. Gilbert Multiplier cell

- It is modification of emitter coupled transistor cell and it allows four quadrant multiplication
- It is basis of integrated circuit balanced multipliers
- Two cross-coupled emitter-coupled pairs are in series connection with an emitter coupled pair forms Gilbert multiplier cell
- Collector currents of  $\alpha_3$  &  $\alpha_4$  are


$$I_{C3} = \frac{I_Q}{1 + e^{-V_1/V_T}} \rightarrow ①$$

$$I_{C4} = \frac{I_{C1}}{1 + e^{V_1/V_T}} \rightarrow ②$$

III<sup>14</sup> Collector current of Q<sub>5</sub> & Q<sub>6</sub> are given by

$$I_{C5} = \frac{I_{C2}}{1 + e^{V_1/V_T}} \rightarrow (3)$$
 
$$I_{C6} = \frac{I_{C2}}{1 + e^{-V_1/V_T}} \rightarrow (4)$$



The collector currents  $I_{C1}$  &  $I_{C2}$  of transistors Q<sub>1</sub> & Q<sub>2</sub> can be expressed as

$$I_{C1} = \frac{I_{EE}}{1 + e^{-V_2/V_T}} \rightarrow (5)$$

$$I_{C2} = \frac{I_{EE}}{1 + e^{V_2/V_T}} \rightarrow (6)$$

sub (5) in (1) & (2)

$$I_{C3} = \frac{I_{EE}}{(1 + e^{-V_1/V_T})(1 + e^{-V_2/V_T})} \rightarrow (7)$$

$$I_{C4} = \frac{I_{EE}}{(1 + e^{V_1/V_T})(1 + e^{V_2/V_T})} \rightarrow (8)$$



iii) Substitute ⑥ in ③ & ④

$$I_{C5} = \frac{I_{EE}}{(1 + e^{V_1/kT})(1 + e^{V_2/kT})} - ⑨$$

$$I_{C6} = \frac{I_{EE}}{(1 + e^{-V_1/kT})(1 + e^{V_2/kT})} - ⑩$$

The differential o/p current  $\Delta I$  is given by.

$$\Delta I = I_{L1} - I_{L2}$$

$$\Delta I = (I_{C3} + I_{C5}) - (I_{C4} + I_{C6})$$

$$\Delta I = (I_{C3} - I_{C6}) - (I_{C4} - I_{C5}) - ⑪$$

Substitute eq ① in ⑩ in ⑪ & employing exponential formulae for hyperbolic functions we get.

$$\Delta I = I_{EE} \left[ \tanh\left(\frac{V_1}{2kT}\right) \tanh\left(\frac{V_2}{2kT}\right) \right] - ⑫$$

The above equation shows that when  $V_1 \approx V_2$  are small, Gilbert cell shown in figure can be used as a four quadrant analog multiplier cell with use of current to voltage converters.

The dc transfer characteristics of such a multiplier circuit is the product of hyperbolic tangent of 2 ip voltages.

The o/p voltage  $V_o$  can be generated from  $\Delta I$ , by using 2 equal valued resistors connected to  $V_{CC}$  & by sending  $I_{L1}$  ( $= I_{C3} + I_{C5}$ ) thro' one resistor &  $I_{L2}$  ( $= I_{C4} + I_{C6}$ ) thro' another (2) resistor.

A modulator or a mixer is a circuit with 2 i/p namely. ⑦  
Carrier i/p & modulating i/p & one modulated o/p.

Linear response is required only for modulating i/p, since carrier is usually an ac signal.

Multiplexer can also be used as modulator., if one of the i/p's is very large & 2nd i/p is very small ( $\tanh(x) \approx x$ )

Then, transistor operated by large signal i/p act as switches multiplies small i/p signal by square wave.

Hence this mode of operation act as modulator. = Synchronous Modulator.  
[Gilbert multiplier with predistortion circuits]


### Gilbert Multiplier with Predistortion Circuits:

\* When magnitude of  $V_1$  &  $V_2$  are very small when impressed with  $V_T$ , the hyperbolic tan function is approximated as near, & circuit can be used as multiplier, for finding  $V_1 \times V_2$ .

But when larger  $V_1$  &  $V_2$  are to be multiplied, a non-linearity function can be used to predistort the i/p signal.

This compensates for the hyperbolic tangent function transfer characteristics of basic cell.

 Required non-linearity function is an "inverse hyperbolic tangent" characteristics.



generation of the inverse hyperbolic tangent function is shown above figure.

Assume that the circuit within the box generate a differential o/p current, & it linearly depends on i/p voltage  $V_i$ .


$$\text{Then, } I_{E1} = I_0 + k_1 V_i$$

$$I_{E2} = I_0 - k_1 V_i$$

$I_{O1}$  = dc current flowing in each o/p.

$\frac{\partial I}{\partial V}$  = transconductance of voltage to current converter.

$$\text{assume } V_i = 0.$$

 

An Inverse hyperbolic tangent circuit

The differential voltage  $\Delta V$  across diode connected transistor Q7 & Q8 is given by

$$\Delta V = V_T \ln \left( \frac{I_{O1} + k_1 V_i}{I_0} \right) \cdot V_T \ln \left( \frac{I_{O1} - k_1 V_i}{I_0} \right)$$

$$\Delta V = V_T \ln \left( \frac{I_{O1} + K_1 V_1}{I_{O1} - K_1 V_1} \right)$$

This can be transformed into

$$\Delta V = \alpha V_T \tanh^{-1} \left( \frac{K_1 V_1}{I_{O1}} \right)$$

using identity  $\tanh^{-1} = \frac{1}{2} \ln \left( \frac{1+x}{1-x} \right)$

if functional block is used, it compensates for the non-linearity of the  $V_p$ 's

Eq: (12) can be represented by

$$\Delta I \approx R_{EE} \left( \frac{K_1 V_1}{I_{O1}} \right) \left( \frac{K_2 V_2}{I_{O2}} \right) \quad - (13)$$

$I_{O1}, K_1, K_2$  = Parameters of the functional blocks following  $V_p$   $V_1$  &  $V_2$ .

complete four-quadrant analog multiplier:

[Complete Four-Quadrant Analog Multiplier]

\* The three boxes are voltage-to-current converters or current-to-voltage converters in effect.

\* The pre-distortion for the input signal is achieved by transistors  $Q_1$  &  $Q_8$ .

\* The current  $I_Q$  &  $I_D$  passing through the emitter of  $Q_7$  generate a voltage between the two emitter terminals, that is proportional to the inverse hyperbolic tangent of  $V_i$ .

\* This compensates for the hyperbolic tangent expression for eq. (8),  $I_{C4}$ .


analysis of the circuit:

A complete four quadrant analog multiplier using Gilbert cell is shown in below figure.

1 Complete Four-

Quadrant analog

Multiplication Using  
- Gilbert cell.

 

2 Current through base-emitter junctions of transistors  $Q_{10}$ ,  $Q_3$ ,  $Q_2$ , &  $Q_8$  connected in series can be expressed by.

$$I_9 I_{10} = I_A I_{10} \quad - (11)$$

By from the series connection of the transistor  $Q_7$ ,  $Q_6$ ,  $Q_5$  and  $Q_8$ , we get.

$$I_9 I_{10} = I_5 I_{10} \quad - (15)$$

From (11), we get

$$I_1 = I_3 + I_4 \quad - (16)$$

$$I_2 = I_5 + I_6 \quad - (17)$$

$$I_{L1} = I_3 + I_5 \quad - (18)$$

$$I_{L2} = I_4 + I_6 \quad - (19)$$

$$I_{xx} = I_9 + I_{10} \quad - (20)$$

The transfer characteristics of differential voltage to current converter is given by

$$I_9 - I_{10} = \frac{V_1}{K_1} \quad - (21) \quad \text{&} \quad \frac{I_1 - I_2}{K_2} = \frac{V_2}{K_2} \quad - (22)$$

1 The transfer characteristics of the differential - to - single feed current to Voltage converter is given by

$$V_0 = K_0 (I_{L2} - I_4) \quad - \quad (23)$$

(6)

where  $K_0, K_1, K_2$  = constants.

Substitute for  $I_4$  &  $I_{L2}$  from (18) & (19) in (23)

$$V_0 = K_0 [ (I_4 + I_6) - (I_3 + I_5) ]$$

Using eq, (14) & (15),

$$V_0 = K_0 \left[ \left( I_4 + I_5 \frac{I_{10}}{I_9} \right) - \left( I_4 \frac{I_{10}}{I_9} + I_5 \right) \right] - (24)$$

Simplifying the above eq.

$$V_0 = K_0 \left( \frac{I_9 - I_{10}}{I_9} \right) (I_4 - I_5) \quad - (25)$$

From (16) & (17)

$$I_1 - I_2 = (I_3 + I_4) - (I_5 + I_6)$$

$$= \left( I_4 \frac{I_{10}}{I_9} + I_4 \right) - \left( I_5 + I_5 \frac{I_{10}}{I_9} \right)$$

Solving for  $(I_4 - I_5)$  gives (26)

$$(I_4 - I_5) = \left( \frac{I_9}{I_9 + I_{10}} \right) (I_1 - I_2) \quad - (27)$$

Sub (27) in (25) & using (21) & (23), we get

$$\begin{aligned} V_0 &= K_0 \left( \frac{I_9 - I_{10}}{I_9 + I_{10}} \right) (I_1 - I_2) \\ &= \frac{K_0 V_1 V_2}{I_{xx} K_1 K_2} = K_m V_1 V_2 \quad - (28) \end{aligned}$$

$$\text{where } K_m = \frac{K_0}{I_{xx} K_1 K_2}$$

(28) employs no approximations. Hence the ip s/b amplitudes have no constraints.

Practical

Total Implementation of 4-Quadrant analog Multiplier

It can be observed that

$$I_1 - I_2 = \frac{2 V_2}{R_{ip}} \rightarrow (29)$$

 


Fig. 9.12 Practical four-quadrant analog multiplier circuit

$$I_9 - I_{10} = \frac{2V_1}{R_x} - \quad (30)$$

further it is assumed that the drop across base-emitter of Q<sub>9</sub> - Q<sub>10</sub> & Q<sub>1</sub> - Q<sub>2</sub> pairs are small in comparison with the drop across R<sub>x</sub> & R<sub>y</sub>.

sub (29) in (30) is (28)

$$\begin{aligned} V_0 &= \frac{4 K_0 R_c V_1 V_2}{T_{xx} R_x R_y} \\ &= K_m V_1 V_2 \quad \text{where } R \gg R_c. \end{aligned}$$

This circuit is capable of performing precise multiplication of continuously varying analog signal by another signal.

problem:

- Need to be able to turn the errors due to offset & mismatch in the integrated circuit implementation.

## Variable Transconductance Techniques:

### Variable Transconductance Technique:

Variable transconductance technique makes use of the dependence characteristics of the transistor transconductance parameter on the emitter current bias applied.

Simple differential circuit arrangement depicting the principle is shown in below figure.

The relationship between  $V_o$  &  $V_x$  is given by

$$V_o = g_m R_L V_x \rightarrow (30)$$

$g_m = \frac{\partial E_E}{\partial V_T} = \text{transconductance of the stage.}$

Application of 2nd ip  $V_y$  to reference current source of the differential amplifier is very  $g_m$ .

Thus, if  $R_E I_{EE} \gg V_{BE}$ , the bias voltage is related to  $I_{EE}$  by the relation  $V_y = I_{EE} R_E$ .

Thus the overall voltage transfer expression is given by

$$\begin{aligned} V_o &= g_m R_L V_x = \left( \frac{V_y}{V_T R_E} \right) V_x R_L \\ &= V_x V_y \frac{R_L}{V_T R_E} \end{aligned}$$

### Operation of Logarithmic Bias

#### Input for Differential stage:

It is assumed that  $|V_x| \ll V_y \Rightarrow$  there is no emitter generation.

Ref. by (A), collector current  $I_1$  &  $I_2$  are related to the applied voltage  $V_x$  by the relation

$$\frac{I_1}{I_2} = e^{(V_x/V_y)} \rightarrow (31)$$

 


Fig: Differential stage of Transconductance Multiplier

Linearity can be achieved by reducing the exponential current-voltage characteristics to a linear one as shown in 38:

The transistor  $Q_1$  &  $Q_2$  are biased through the diode connected  $Q_A$  &  $Q_B$ , which are driven by controlled current source  $I_A$  &  $I_B$  respectively.

Then the net bias voltage  $V_x$  is represented by.

$$V_x = V_T \ln \left( \frac{I_B}{I_A} \right) \quad - \textcircled{32}$$

Sub \textcircled{31} in \textcircled{31}


$$\frac{I_1}{I_g} = \frac{I_B}{I_A}$$

by

$$\frac{I_A}{I_A + I_B} = \frac{I_2}{I_1 + I_2} = \frac{1}{1 + e^{V_x/V_T}} \quad - \textcircled{33}$$


$$\frac{I_B}{I_A + I_B} = \frac{I_1}{I_1 + I_2} = \frac{e^{V_x/V_T}}{1 + e^{V_x/V_T}} \quad - \textcircled{34}$$

 The above equation are valid over a wide range of the device characteristics are well matched &  $V_{BE}$  obey basic diode equation.


 
## Four Quadrant Variable Transconductance Multiplier

A typical four-quadrant multiplier circuit is shown below.



FOUR QUADRANT MONOLITHIC MULTIPLIER

The four quadrant operation indicates that the o/p voltage is directly proportional to the product of the 2 i/p voltage regardless of the polarity of the i/p's and such multipliers can be operated in all the four quadrants of operation.

The 1<sup>st</sup> part of circuit generates an intermediate voltage  $V_1$  across the transistor  $Q_A$  &  $Q_B$  in response to i/p signal  $V_x$ .

The non-linear response to i/p  $V_x$  in generating  $V_1$  is compensated by the inverse non-linearity associated with the base-emitter junctions of the quad-transistor  $Q_5 - Q_6$  &  $Q_7 - Q_8$ .

Thus the o/p voltage  $V_o$  is maintained proportional to the linear product of the 2 i/p voltages.

The emitter degeneration resistors  $R_x$  &  $R_y$  provide linear conversion of the i/p voltages to the differential currents  $I_x$  &  $I_y$ .

$$\text{Thus } I_x = \frac{V_x}{R_x} \quad \& \quad I_y = \frac{V_y}{R_y}$$

The value of  $R_x$  &  $R_y$  are chosen such that  $R_x \gg V_T/I_1$ ,  
 $\& R_y \gg V_T/I_2$ .

of voltage  $V_o$  can be written as

$$V_o = R_L ((I_6 + I_7) - (I_5 + I_8)) \quad - \textcircled{35}$$

apply  $\textcircled{33}$  &  $\textcircled{34}$  to the circuit,

$$\frac{I_b}{I_x + I_y} = \frac{I_5}{I_x - I_y} = \frac{I_1 + I_x}{2I_1} \quad - \textcircled{36}$$

$$\frac{I_8}{I_x + I_y} = \frac{I_7}{I_x - I_y} = \frac{I_1 - I_x}{2I_1} \quad - \textcircled{37}$$

sub  $\textcircled{36}$  &  $\textcircled{37}$  in  $\textcircled{35}$ .

$$V_o = \frac{2R_L}{I_1} (I_x I_y) \quad - \textcircled{38}$$

Since  $I_x$  &  $I_y$  are linearly related to  $V_x$  &  $V_y$ ,

$$V_o = K V_x V_y \quad - \textcircled{39}$$

$$K = \text{Scaling factor} = \frac{2R_L}{I_1 R_x R_y} = 0.1$$

# Applications of Multiplier IC's

Sinha, R.

PRINCE

16

## APPLICATIONS OF MULTIPLIER IC's

- Voltage Squarer
- Frequency Doubler
- Voltage divider
- Square Rooter
- Phase angle detector
- Rectifier

### Voltage Squarer :-

 


Fig shows. Multiplier IC connected to a squaring ckt. The i/p's can be positive or negative, represented by any corresponding voltage level between 0 & 10V.

I/p voltage  $V_i$  is squared simply by connecting both the terminal

$$V_x = V_y = V_i \text{ & o/p is } V_o = KV_i^2$$

The circuit thus perform the squaring operation. This application can be extended for frequency doubling w/ applications also as explained.


### Frequency Doubler :-

\* Squaring circuit connected for frequency doubling operation.


A sine wave signal  $v_i$  has a peak amplitude of  $A_v$  & frequency of 3 Hz

% Voltage of doubler ckt is
 
$$\begin{aligned}
 V_o &= \frac{A_v \sin 2\pi ft \times A_v \sin 2\pi ft}{10} = \frac{A_v^2}{10} \sin^2(2\pi ft) \\
 &= \frac{A_v^2}{20} [1 - \cos 4\pi ft]
 \end{aligned}$$



2391  
890198

 

fig(a) circuit diagram  
fig(b) I/P & O/P waveform

Assume peak amplitude  $A_v = 5V$  &  $f_i = 10\text{kHz}$ ,  $V_o = 1.25 - 1.25 \cos 2\pi(2000)t$

1st term  $\rightarrow$  dc term of 1.25V peak amplitude

O/P waveform ripples with twice the i/p frequency in the rectified O/P of the i/p signal.

This forms principle of application of analog multiplier as rectifier of ac s/s

Dc component is removed by connecting 1μF coupling capacitor between O/P terminal & load resistor.

### Voltage Divider:

Voltage divider constructed using multiplier & op-amp.


Circuit produces the ratio of 2 i/p s/s's.

Division is achieved by connecting the multiplier in the feedback loop of an op-amp.

Two i/p voltages =  $V_{den}$  &  $V_{num}$ .

$V_{den} =$  i/p of multiplier & o/p of op-amp  $V_{OA}$  as another i/p to multiplier.

 O/P  $V_{num}$  of multiplier is connected back to inverting i/p of op-amp in feedback loop.



Characteristic op-amp operation of multiplier gives  $V_{om} = KV_{OA} V_{den}$

As shown in dia, no i/p sig current can flow into the inverting i/p terminal of op-amp, which is at virtual ground.

i.e. at 'a',  $i_1 + i_2 = 0$

$V_{om} = KV_{OA} V_{den}$

$$i_1 = \frac{V_{num}}{R}, R = \text{i/p resistance}$$

$$i_2 = \frac{V_{om}}{R}$$

With Virtual Ground, at 'a'

$$i_1 + i_2 = \frac{V_{num}}{R} + \frac{V_{om}}{R} = 0$$

$$V_{om} = -V_{num}$$

Sub.  $V_{om}$  in above eqn.  $\Rightarrow KV_{OA} V_{den} = -V_{num}$

$$V_{OA} = \frac{-V_{num}}{KV_{den}}$$

where,

$V_{num}$  &  $V_{den}$  are numerator & denominator voltages.  $\therefore$  Voltage division operation is done.

$V_{num}$  = 've or '-'ve &  $V_{den}$  = only '+'ve value to ensure

$V_{den}$  is changed; Gain  $\propto \frac{V_{num}}{V_{den}}$  changes, "ve" feedback.

Automatic Gain Control (AGC) circuits. this feature is used in

### Square Rooter:-

Divider circuit can be used to find square root of a signal by connecting both i/p's of multiplier to o/p of op-amp.

O/p voltage of multiplier  $V_{om}$  is equal in magnitude but opposite in polarity w.r.t (and) to  $V_i$ .

w.r.t

$$V_{om} = (\gamma_{10})^{\text{scale factor}} \text{ of } V_o \times V_o \text{ on.}$$

$$-V_i = V_{om} = V_o^2 / \gamma_{10}$$

Solving for  $V_o$  & eliminating  $V_i$  yields

$$V_o = \sqrt{10} |V_i|$$

- \*  $V_o$  = square root of 10 times the absolute magnitude of  $V_i$ .
- \*  $V_i$  = must be negative <sup>else</sup> op-amp saturates.
- \* Range of  $V_i$  is between  $-1$  &  $-10V$ , voltage less than  $-1V$  will cause inaccuracies.
- \* Diode prevents negative saturation for positive polarity  $V_i$   $\frac{1}{2}$ .  
For +ve value of  $V_i$ , diode connections are reversed.

### Phase Angle Detector :-

Multiplexer is configured as phase angle detection measurement.  
Then 2 sine-waves of the same frequency are applied to the r/p of the multiplier, o/p  $V_o$  has a dc component & an ac component

Trigonometric identity

$$\sin A \sin B = \frac{1}{2} (\cos(A-B) - \cos(A+B))$$

When 2 frequencies are equal, but with different phase angles, e.g.  
 $A = 2\pi f t + \theta$  for signal  $v_x$  &  $B = 2\pi f t$  for signal  $v_y$ .

$$[\sin(2\pi f t + \theta)] [\sin(2\pi f t)] = \frac{1}{2} [\cos \theta - \cos(4\pi f t + \theta)]$$

$\therefore$  if 2 ip s/a  $v_x$  &  $v_y$  are applied to multiplier  $V_o$  (dc)




$$V_o(\text{dc}) = \frac{V_{xp} V_{yp}}{2} \cos \theta$$

$V_{xp}$  &  $V_{yp}$  = peak voltage amplitudes of s/a  $v_x$  &  $v_y$ .

$\Rightarrow V_o(\text{dc})$  depends on  $\cos \theta$ .

Dc voltmeter can be calibrated as phase angle meter when  $V_{xp} * V_{yp}$  is equal to 20.
   
$$V_o(\text{dc}) = \cos \theta \quad ; \text{ when } V_{xyp} V_{yp} = 20 \quad \text{or} \quad V_{xyp} V_{yp} = 1.41V$$




## PHASE-LOCKED Loop

69

- APPLICATION:**
- Radar synchronization & communication Applications.
  - Satellite communication + electronic frequency control.
  - Air borne Navigation S/m.
  - FH communication S/m, computers etc.

### BASIC PRINCIPLES & OPERATION OF THE BASIC PLL

Block diagram of basic PLL is.

 

Main elements :-

- Phase Detector / Comparator
- LPF
- Bal. Amplifier
- $V_{CO} \Rightarrow$  Voltage Controlled Oscillator.

**Phase Detector:** It is a multiplier which generates sum & difference of 2 i/p signals.

Free running frequency  $f_0$  of the VCO is determined by externally connected resistor & a timing capacitor.

When loop is locked, frequency  $f_0 \propto$  to externally applied voltage  $V_C$  called dc control voltage.

Input periodic signal  $V_i$  of frequency  $f_i$  & VCO output signal  $V_0$  of frequency  $f_0$  are applied to PLL, Phase detector produce a d.c or low frequency signal  $V_e$  which is proportional to phase difference between  $V_i$  &  $V_0$ .

$$\text{difference in phase} \\ \therefore V_e \propto (V_i - V_0)$$

frequency sum components is filtered out.

Low frequency difference signal is passed out the filter & then amplified by error Amplifier (A).

This amplified signal is applied as input to VCO as control voltage  $V_C$ , which changes VCO frequency  $f_O$  in such a way difference between  $f_O$  &  $f_i$  is reduced.

When these two frequency is brought identical by this feedback action then circuit is said to be locked.

Once "locked",  $f_O = f_i$ , with infinite phase difference  $\phi$ .

~~Access~~  
process of capture :-

[Process of capture]

Important aspect of PLL, by which loop achieves condition of being in-lock with signal from a free-running and unlocked condition.

In unlocked condition of PLL, VCO operate at  $f_c$  called "centre frequency or free running frequency". Corresponds to applied voltage of 0V dc at its control input. Capture process is non-linear.

Assume, feedback loop of PLL is initially open between loop-filter & VCO control input.

Input signal frequency  $f_i$  assumed to be closer to VCO centre frequency  $f_c$  is applied to the input of the phase detector.

Phase detector is usually phase detector analog multiplier that multiplies two sinusoidal together & produce sum & difference of 2 S/H as its O/P.

High frequency sum components is filtered out, by LPF & O/P of LPF is difference between VCO centre frequency  $f_c$  & incoming signal frequency  $f_i$ .

Consider that loop is closed, difference frequency is applied to VCO input as the control voltage  $V_c$ . This will make VCO frequency  $f_o$ , a sinusoidal function of time.


$\therefore$  It alternately moves "closer & farther" away from  $f_i$ :

O/P of phase detector  $\Rightarrow f_o - f_i$ ; moves higher frequency when  $f_o$  moves away from  $f_i$ ; & moves to lower frequency when  $f_o$  moves closer to  $f_i$ .

O/P of phase detector has asymmetrical wave shape during capture process. This produce dc component in phase detector O/P.

Dc component shifts the VCO frequency  $f_o$  towards  $f_i$  & thus frequency difference  $V_o$  gradually diminishes.

 O/P of phase detector during capture process.



when loop is locked; frequency difference becomes zero. & dc voltage remain at the loop filter O/P.

LPF filter  $f_o - f_i$  resulting from interfering signal, which are far away from  $f_o$ . It also acts as memory for loop., when lock is momentarily lost due to large interfering transient signal.

$\therefore$  Capture Range & Pull-in Time are dependent on amount of Gain in the loop. & Bandwidth of the filter.

It will be out of capture range when beat frequency is too high due to VCO frequency which is far away from centre frequency.

Once locked achieved, VCO track signal well beyond capture range.

~~Procedure~~ Reduce B.W of filter  $\rightarrow$  improve selectivity of out of band sp &  $\downarrow$  capture range  $\Rightarrow$  pull-in time  $\uparrow$  & loop phase margin (less)

**Capture Range**: Capture Range of PLL is defined as one range of input frequency around centre frequency within which the loop get locked from an unlocked condition.


**Pull-In-Time**: Pull-in Time is the total time required for the loop to get captured with input signal.

**Important Feature**: Ability to suppress the noise such as those super-imposed on the input signal & noise generated by VCO.

Free running stage  
capture range  
Lock Range  
pull in time

closed

### LOOP ANALYSIS OF PLL

 

Assume PLL is initially in locked condition. Also assume, gain of the Phase detector is  $K_d$  volt/rad of phase difference, Transfer characteristic of loop filter is  $F(s)$  & Gain of forward loop is  $A$ .

$$\text{i/p sinusoidal s.t. } V_i \text{ is } V_i = V_p \sin(\omega t + \theta_i) \quad \text{--- (1)}$$

If phase shift of the signal at the VCO o/p is  $\theta_{osc}$ , the average value of the o/p of phase detector is

$$V_o = K_d (\theta_i - \theta_{osc}) \quad \text{--- (2)}$$

$\theta_i$  &  $\theta_{osc}$  = phase shift w.r.t an arbitrarily assumed reference.

Phase of the signal at the o/p of VCO as a function of time is equal to integral of the VCO o/p frequency.

$$\omega_{osc}(t) = \frac{d \theta_{osc}(t)}{dt}$$

$$\theta_{osc}(t) = \int_0^t \omega_{osc}(t) dt + \theta_{osc}|_{t=0}$$

∴ integral component is represented as  $\frac{1}{2} \theta$  inside the VCO block.

Oscillator frequency  $\omega_{osc}$  & dc control voltage  $V_c$  is related

$$\omega_{osc} = \omega_c + k_o V_c \quad - (3)$$

$\omega_c$  = centre or free-running angular frequency

when  $V_c = 0$  &  $k_o$  is VCO Gain in rad/s per volt.

Closed-loop transfer function of the PLL becomes.

$$\begin{aligned} \frac{V_c(s)}{\theta_i(s)} &= \frac{k_d F(s) A}{1 + k_d A F(s) \frac{k_o}{s}} \\ &= \frac{s k_d F(s) A}{s + k_d k_o A F(s)} \quad - (4) \end{aligned}$$

Response of the loop to frequency variation at the i/p rather than phase,

$$\frac{V_c(s)}{w_i(s)} = \frac{V_c(s)}{s \theta_i(s)} = \frac{k_d F(s) \cdot A}{s + k_d k_o A F(s)} \quad - (5)$$

$$w_i = d\theta_i/dt, w_i(s) = s \theta_i(s)$$

consider  $F(s) = 1$ ; 1st order LPF.

$$\frac{V_c(s)}{w_i(s)} = \frac{k_v}{s + k_v} \times \frac{1}{k_o} \quad - (6)$$

$$k_v = \text{loop bandwidth}, k_v = k_o k_d \cdot A$$

$k_v$  = effective bandwidth & loop & capture range depend on  $k_v$ . If

$k_v$  decrease, capture time rises & capture-range reduces. ∴ property of interference rejection improves.

Second-order PLL :-

1st order PLL has several limitation.


- Both sum & difference frequency component are fed to the o/p from Phase detector.
- All out of band interfering signals from the i/p will appear shifted in frequency at the o/p

Loop-filter is highly desirable in application where interfering S/I are present.

Common configuration of monolithic PLL is 2nd order loop with loop filter  $F(s)$  of simple single-pole, low pass filter realized with R-C

$$F(s) = \frac{1}{1+s/\omega} = \frac{1}{1+sT} - \textcircled{7}$$

$$\omega = 1/Rc = Y_T$$

 

Block Diagram of Second-order PLL using single pole loop filter.


Loop lock-range & Capture Range :-

Loop lock-range is represented as the range of frequencies about  $\omega_0$  for which the PLL maintains the relationship  $\omega_i = \omega_{osc}$ .

If phase detector can determine the phase difference between  $\theta_i$  &  $\theta_{osc}$  over a  $\pm \pi/2$  range;

lock-range is,
 
$$\begin{aligned} \omega_L &= \pm \Delta\omega_{osc} \\ &= K_d A K_o (\pm \pi/2) \\ &= \pm k_v (\pi/2) - \textcircled{8} \end{aligned}$$



Capture Range is range of i/p frequencies within which an initially unlocked loop will get locked with an i/p s/o.

$F(s) = 1$ ; capture range = lock-range.

If  $F(s) = \frac{1}{(1+s/\omega_i)}$   $\Rightarrow$  capture range  $\subset$  lock range.


## VOLTAGE CONTROLLED OSCILLATOR: ✓ [VCO]

\* VCO is an oscillator whose oscillating frequency varies in response to control voltage  $V_c$ .  $\Rightarrow f_0 = kV_c$ ,  $\therefore V_c > 0 \Rightarrow k$  is defined as sensitivity of VCO in rad/Volt.



### Properties:-

- Linearity in voltage to frequency conversion.
- Frequency stability against temperature changes, & drift characteristics.
- High operating frequency & wide tracking range of frequencies.
- High Modulation sensitivity to & ease of tuning.


### IC 566 VCO :- [NE/SE 566]

 

Pin diagram.

  

O/p wave form

 

Basic Block Diagram.

The frequency of oscillation is determined by an externally connected resistor  $R_1$  & capacitor  $C_1$ .

Control voltage or modulating input  $V_C$  is applied at control terminal (pin 5).

Triangular voltage obtained at pin 4 is applied. It is generated by alternately charging capacitor  $C_1$  by one current source & discharging it linearly through another current source.

Amount of charge & discharge voltage swing is determined by Schmitt trigger. It provide square-wave o/p at pin 3 through power amplifier  $A_2$  & triangular-wave o/p at pin 4 through buffer amplifier  $A_1$ .

Operation of VCO:-

O/p voltage during of the Schmitt trigger is set to, level  $V_{CC} - 0.5V_{CC}$  if  $R_a = R_b$  in positive feedback path. Voltage at non-inverting terminal of  $A_2$  swings from  $0.5V_{CC}$  to  $0.25V_{CC}$ .

During charging of  $C_1$ , voltage across  $C_1$  just exceed  $0.5V_{CC}$ , Schmitt trigger switches to low ( $0.5V_{CC}$ ) & capacitor starts discharging.

When voltage across  $C_1$  reduces to  $0.25V_{CC}$  the Schmitt trigger switches to HIGH ( $V_C$ )

Maintain source current & sink current equal to obtain equal +ve & -ve slope. at pin 4.

Square-wave o/p of Schmitt trigger, inverted & buffered at pin 3.

Calculation of free running frequency  $f_0$  of VCO :-

Voltage change across capacitor  $C_1$  is  $\Delta V = 0.25V_{CC}$ . Since constant current source are used, rate of change of voltage across the capacitor is given by

$$\frac{\Delta V}{\Delta t} = i/C_1$$

$$\frac{0.25V_{cc}}{\Delta t} = \frac{i}{C_1}$$

$$\Delta t = \frac{0.25V_{cc}C_1}{i} \rightarrow ①$$

Time period  $T$  of the triangular waveform is  $2\Delta t$ .

$\therefore$  frequency of oscillation  $f_0$  is

$$f_0 = \frac{1}{T} = \frac{1}{2\Delta t} = \frac{i}{0.5V_{cc}C_1} \rightarrow ②$$

$$i = \frac{V_{cc} - V_c}{R_1}; V_c = \text{voltage at pin 5.} \rightarrow ③$$

$$f_0 = \frac{2(V_{cc} - V_c)}{C_1 R_1 V_{cc}} \rightarrow ④$$

$\therefore$  O/p frequency of VCO varied by

- External resistor  $R_1$ ,
- External capacitor  $C_1$ ,
- Control voltage  $V_c$  applied at pin 5.

Voltage  $V_c$  at pin 5 is set by voltage divider circuit consisting of  $R_2$  &  $R_3$ . If  $V_c$  is initially set to  $\frac{1}{8}V_{cc}$ , then.

$$f_0 = \frac{2(V_{cc} - (1/8)V_{cc})}{C_1 R_1 V_{cc}} = \frac{1}{4R_1 C_1} = \frac{0.25}{R_1 C_1} \rightarrow ⑤$$

Voltage - to - frequency conversion factor:

The voltage - to - frequency conversion factor is determined by  $K_V = \frac{\Delta f_0}{\Delta V_c}$

$\Delta V_c$  = change in modulating signal required to produce a corresponding shift  $\Delta f_0$  in frequency. Assuming centre frequency is  $f_0$  & new frequency  $f_1$ ,

$$\Delta f = f_1 - f_0.$$

$$= \frac{2(V_{cc} - V_c + \Delta V_c) - 2(V_{cc} - V_c)}{C_1 R_1 V_{cc}} = \frac{2\Delta V_c}{C_1 R_1 V_{cc}}$$

$$\Delta f = \frac{2 \Delta V_c}{C_{IRIVCC}}$$

$$\frac{\Delta f}{\Delta V_c} = k_V = \frac{2}{C_{IRIVCC}}$$

$$f_0 = \frac{1}{2R_1 C_1}$$

$$k_V = \frac{2f_0}{V_C}$$

## MONOLITHIC PHASE-LOCKED LOOP

PRINCIPLE

### MONOLITHIC PHASE LOCKED LOOP

\* Monolithic PLLs are SE/NE 56B series from Signetics.

LM 560 series from National Semiconductor Corp.

\* PLL circuit consists of a Gilbert type Phase detector, temperature-compensated VCO & facility for connecting an external RC circuit to perform the loop-filter function.

### NE 565 PLL :

The analog phase detector circuit of PLL comprises of Q<sub>1</sub>-Q<sub>2</sub>, Q<sub>3</sub>-Q<sub>4</sub> & Q<sub>5</sub>-Q<sub>6</sub> differential amplifier pairs.

Q<sub>3</sub> & R<sub>3</sub> serve as current-sink bias source.

R<sub>1</sub> & R<sub>2</sub> serve as loads for the phase detector. The diode connected transistors Q<sub>7</sub> & Q<sub>3</sub> reduce the voltage swings to  $\pm 0.7V$  & conversion ratio of PLL becomes

$$K_d = \frac{0.7 - (-0.7)}{\pi} = \frac{1.4}{\pi} \quad - (1)$$


Balanced O/P from the phase detector is supplied to the differential transistor pair Q<sub>10</sub>-Q<sub>11</sub> biased by Q<sub>39</sub> which acts as the current sink. This stage works for a gain of 1.4 & a single ended O/P from this stage taken across R<sub>12</sub>.

Resistor R<sub>12</sub> in combination with the external capacitor connected between pin 7 & ground form the loop-filter.

Transistors Q<sub>12</sub> through Q<sub>23</sub> form the Voltage controlled current source for the VCO. Equal charging & discharging currents are supplied to the external capacitor C<sub>1</sub> connected to pin 9. Resistor R<sub>1</sub> is connected between pin 8 & +V<sub>cc</sub>.


Schmitt trigger formed by Q<sub>25</sub> through Q<sub>36</sub> with differential amplifier. O/P circuit consisting of Q<sub>33</sub> & Q<sub>34</sub> from part of VCO. Charging & Discharging cycles through the current source are determined by switching the transistors Q<sub>23</sub> & Q<sub>37</sub> ON or OFF.

 Transistor Q<sub>14</sub>, Q<sub>26</sub>, Q<sub>30</sub> & Q<sub>35</sub> connected as diodes generate the desired level shifting.



-V <sub>CC</sub>	14	NC
I/P 2	13	NC
I/P 3	12	NC
VCO 4	11	NC
O/P	10	+V <sub>CC</sub>
Phase	9	C <sub>EXT</sub> or VCO
comparator	8	R <sub>EXT</sub> VCO
%P		
Reference		
o/p		
Demodulated		
O/P.		

14-PIN DIAGRAM

 

BLOCK DIAGRAM OF IC 565

IC 565 is available in 14 pin DIP package. A 10-pin Metal Can Package.

O/p of phase detector is applied to a differential amplifier.

Single ended o/p dropped across R is connected internally to VCO. It is also demodulated o/p at pin 7 of PLL.

R is part of LPF. Capacitor C between pin 7 & 10 along with the internal resistor R of 3.6k $\Omega$  from the LPF, Capacitor C should be large enough to eliminate variation in demodulated o/p voltage at pin 7.

Dual power supply  $\pm 6V$  to  $\pm 12V$ , If single supply  $+12V$  &  $+24V$ .  
 Rating characteristics :- Voltage =  $\pm 6V$  & TA =  $+25^\circ C$

$0.001\mu F$  C is connected between pin 7 & 8. to avoid oscillations due to parasitic effect.

Free running or centre frequency of VCO is

$$\omega_0 = \frac{1.2}{4R_1C_1} \quad - (2)$$

$R_1$  &  $C_1$  = External Resistor & capacitor. connected to pin 8 & 9.

$R_1 \Rightarrow 2k\Omega$  to  $20k\Omega$

Device can achieve lock with an ip signal over  $\pm 60\%$  of B.W w.r.t  $\omega_0$ .

Pin 2 & 3 two ip terminal of IC565. The ip s/e can also be direct coupled without any dc voltage difference between the pins, dc resistance does from pin 2 & 3 being equal.

Derivation of Lock-in-Range :-

\* Assume  $\phi$  radians is the phase difference between ip s/e & VCO voltage. Op of phase detector  $V_e$  is

$$V_e = K_d (\phi - \pi/2) \quad - (3)$$

$K_d$  = Phase angle-to-voltage transfer coefficient of phase detector.

control voltage at VCO is  $V_c = AK_d (\phi - \pi/2) \quad - (4)$

A = Voltage gain of Amplifier.

VCO shifts free running frequency  $\omega_0$  to frequency  $\omega$  is

$$\omega = \omega_0 + K_0 V_c \quad - (5)$$

$K_0$  = Voltage to frequency transfer coefficient of VCO.

PLC achieve lock with signal frequency  $\omega_i$

$$\omega = \omega_i = \omega_0 + K_0 V_c \quad - (6)$$

From (4) & (6)

$$V_c = \frac{\omega_i - \omega_0}{K_0} = A K_d (\phi - \pi/2) \quad - (7)$$

$$\phi = \pi/2 + (\omega_i - \omega_0) / K_0 K_d A \quad - (8)$$

maximum o/p voltage magnitude available from the phase detector  
occurs for  $\phi = \pi$  & 0 radian.

$$V_{c(\max)} = \pm K_d \frac{\pi}{2}$$

∴ Maximum control voltage to drive VCO is

$$V_{c(\max)} = \pm \left(\frac{\pi}{2}\right) K_d \cdot A \quad - (9)$$

Maximum VCO swings in frequency that can be achieved is

$$(f - f_0)_{\max} = K_o V_{c(\max)} = K_d K_o A \left(\frac{\pi}{2}\right) \quad - (10)$$

∴ Maximum range of signal frequencies over which PLL can remain locked

$$\begin{aligned} \delta_i &= \delta_0 \pm (f - f_0)_{\max} \\ &= \delta_0 \pm K_d K_o A \left(\frac{\pi}{2}\right) = \delta_0 \pm \Delta \delta_L \end{aligned} \quad - (11)$$

Lock-in frequency range is  $2\Delta \delta_L \pm \delta_{\text{lim}}$  (11) it is given by

$$\text{lock-in range} = 2\Delta \delta_L = K_d K_o A \pi = K_v \pi \quad - (12)$$

where  $K_v = K_o K_d A$ . loop bandwidth.

$$\text{or } \Delta \delta_L = K_d K_o A \left(\frac{\pi}{2}\right) = K_v \left(\frac{\pi}{2}\right) \quad - (13)$$

lock-in range is symmetrically located with respect to free running frequency  $f_0$  of VCO. ICL PLL 565,

$$K_v = \frac{8 \delta_0}{V}$$

$$V = \pm V_{cc} - (-V_{cc})$$

$$K_d = \frac{1.4}{\pi}$$

$$A = 1.4$$

$$\Delta \delta_L = \pm 7.8 \frac{\delta_0}{V} \quad - (14)$$

## Derivation of capture range:

When PLL is not initially locked to the signal, the frequency of the VCO will be its free running frequency  $\omega_0$ .

Phase angle difference between the i/p signal & VCO output voltage will be.

$$\begin{aligned}\phi &= (\omega_i t + \phi_i) - (\omega_0 t + \phi_0) \\ &= (\omega_i - \omega_0) t + \Delta\phi\end{aligned} \quad - (15)$$

Thus phase difference is not constant change with time.

$$\frac{d\phi}{dt} = \omega_i - \omega_0 \quad - (16)$$

Phase detector output voltage will therefore not have a dc component but will produce ac voltage with a triangular waveform of peak amplitude  $K_d (\pi/2)$  & fundamental frequency  $(\omega_i - \omega_0) = A_f$ .

$$\text{LPF is simple RC network; T.F} \Rightarrow T(f) = \frac{1}{1+j(\omega/\omega_1)} \quad - (17)$$

i/p to LPF:

$$\Delta f = \omega_i - \omega_0 ,$$

$\Delta f > \omega_1$ , LPF T.F. will be

$$T(\Delta f) = \frac{\omega_1}{\Delta f} = \frac{\omega_1}{\omega_i - \omega_0} \quad - (18)$$

voltage  $V_c$  to drive VCO

$$V_c = V_o \times T(f) \times A$$

$$V_{c(\max)} = V_{o(\max)} \times T(f) \times A \quad - (19)$$

w.k.t

$$V_{c(\max)} = \pm K_d (\pi/2) A (\omega_i / \Delta f)$$

Corresponding value of maximum VCO frequency shift is

$$\begin{aligned}(\omega - \omega_0)_{\max} &= K_d V_{c(\max)} \\ &= K_d K_o (\pi/2) \cdot A \cdot (\omega_i / \Delta f)\end{aligned} \quad - (20)$$

Let  $\omega_i = \omega$ , for acquisition of signal frequency, maximum signal frequency range that can be acquired by PLL is

$$(\omega_i - \omega_0)_{\max} = \pm K_d K_o (\pi/2) A (\omega_i / \Delta f_c) \quad - (21)$$

$$\Delta f_c = (f_p - f_o)_{\max}$$

$$(\Delta \theta_c)^2 = K_d K_o (\frac{\pi}{2}) A \theta_1$$

since  $\Delta \theta_L = \pm K_d K_o (\frac{\pi}{2}) A \theta_1$ ; we get

$$\Delta \theta_c = \pm \sqrt{\theta_1 \Delta \theta_L}$$

∴ (22)

Total capture range is

$$2\Delta \theta_c \approx 2\sqrt{\theta_1} \Delta \theta_L$$

here lock-in range =  $2\Delta \theta_L = K_d K_o A \pi = K \sqrt{\pi}$ .

IC 565,  $R = 3.6 \times 10^3$

$$\therefore \Delta \theta_c = \pm \left[ \frac{\Delta \theta_L}{(2\pi)(3.6 \times 10^3) C} \right]^{1/2} \quad \text{∴ (23)}$$

$C = \text{Ferrads}$ .


Capture Range is symmetrically located w.r.t to  $f_{VCO}$ .

PLL cannot obtain lock outside capture range.

Once captured, it will hold on until the signal frequency goes beyond the lock-in range.

To increase lock-in range, larger capture range is required

 If capture range is increased, PLL susceptible to noise. LPF bandwidth is reduced to minimize interference.



1) For PLL 565, given the free-running freq as 100 kHz,  
 the demodulation capacitor of  $2\mu F$  and supply voltage is  $\pm 6V$   
 determine the lock & capture freq. & identify the  
 component values.

Soln:  $f_0 = 100\text{kHz}$ ,  $C = 2\mu F$ ,  $V_{cc} = \pm 6V$

$$\therefore \Delta f_L = \pm \frac{7.8 f_0}{V} = \pm \frac{7.8 \times 100 \times 10^3}{6 - (-6)} = \pm 65\text{kHz}$$

$$\therefore 2\Delta f_L = 2 \times 65\text{kHz} = 130\text{kHz}$$

$$\Delta f_C = \pm \sqrt{\frac{\Delta f_L}{2\pi \times 3.6 \times 10^3 \times C}} = \pm \sqrt{\frac{65 \times 10^3}{2\pi \times 3.6 \times 10^3 \times 2 \times 10^{-6}}} = \pm 1.199\text{kHz}$$

$$f_0 = \frac{1.2}{4R_1C_1}$$

assume,  $R_1 = 12\text{k}\Omega$ . a standard value,

$$100 \times 10^3 = \frac{1.2}{4 \times 12 \times 10^3 \times C_1}$$

$$\therefore C_1 = \frac{1.2}{4 \times 12 \times 10^3 \times 100 \times 10^3} = 25 \times 10^{-10}\text{F}$$

2) Determine the output freq.  $f_0$ , lock range  $\Delta f_L$  and  
 capture range  $\Delta f_C$  of IC 565. Assume  $R_1 = 15\text{k}\Omega$ ,  $C_1 = 0.01\mu F$   
 $C = 1\mu F$  &  $V_{cc} = +12V$ .

Soln:

$$R_1 = 15\text{k}\Omega, C_1 = 0.01\mu F \quad \& \quad C = 1\mu F$$

$$\therefore \text{Free running freq. } f_0 \approx \frac{1.2}{4R_1C_1}$$

$$= \frac{1.2}{4 \times 15 \times 10^3 \times 0.01 \times 10^{-6}} = 2\text{kHz}$$

$$\text{Lock range} = \Delta f_L = \pm \frac{1.8 \text{ Hz}}{\sqrt{V}}$$

$$= \pm 1.8 \times \frac{2000}{12} = \pm 103 \text{ kHz}$$

Capture range.

$$\Delta f_C = \pm \left[ \frac{\Delta f_L}{2\pi (3.6 \times 10^3) \times C} \right]^{1/2}$$

$$= \pm \left[ \frac{1.3 \times 10^{-3}}{2\pi \times 3.6 \times 10^3 \times 1 \times 10^{-6}} \right]^{1/2}$$

$$= 239.73 \text{ Hz.}$$

UNIT - 18


## AM Detection:

- \* PLL can be used as an AM detector for demodulating the amplitude-modulated signals. Assume AM signal is given by

$$V_m(t) = V_p [1 + m(t)] \sin w_c t = V_p + V_p(m(t)) \sin w_c t$$

- : Signal  $V_m(t)$  can be demodulated by multiplying the signal with a local oscillator signal of the same carrier frequency  $\omega_c$ .

Then multiplier o/p is

 


Simple AM detector.

$$\begin{aligned} V_o(t) &= A V_p [(1 + m(t)) \sin w_c t \sin(w_c t + \theta)] \\ &= A V_p [1 + m(t)] \frac{\cos \theta - \cos(2w_c t + \theta)}{2} \end{aligned}$$

- \* High-frequency 2nd term can be removed by LPF and hence filter o/p becomes

$$V_o(t) = V [1 + m(t) \cos \theta]$$

$$V = A V_p$$

 


AM detector Using PLL

- \* Local oscillator s/o generated in PLL is phase-locked with V\_p s/o.
- \* PLL is locked to carrier frequency of amplitude-modulated signal.
- \* VCO o/p of PLL, which has same frequency values as the carrier, but unmodulated, is applied as one i/p to the multiplier.
- \* In unlock condition, VCO o/p signal of PLL is 90° out of phase with the V\_p signal.
- \* AM i/p signal is phase-shifted by 90° before being applied to the multiplier.
- \* Two signals applied to multiplier, AM s/o & carrier s/o generated in PLL are now in phase.
- \* O/p of multiplier is then passed through LPF for removal of high frequency components.

## APPLICATIONS OF IC 565 PLL

- Frequency Multiplication / Division
- AM Detection
- FM Detection
- FSK Modulation / Demodulation
- Frequency Synthesizing
 
### Frequency Multiplication / Division:-



A Divide-by- $N$ -network (frequency divider) is inserted between VCO and phase detector.

when PLL is in locked condition, O/P of frequency divider network is same as I/P frequency  $\delta_i$ .

VCO actually provides multiple of I/P frequency. This multiplication factor is achieved by inserting suitable divide-by- $N$  network,  $N$  is integer.

In locked condition,  $\delta_o = N\delta_i$ . Eg.: Divide-by-5 Now shown.

Frequency Multiplication can also be obtained by operating PLL in harmonic locking mode for I/P signals, which is rich in harmonic such as square-wave.

Then VCO can get directly locked on the  $n^{\text{th}}$  harmonic of I/P signal without use of frequency divider. Value of  $n$  is limited to 10.


## $V_o$ & Amplitude of $V_p$ s/k

- \* This AM detector exhibits a high degree of selectivity due to the fact that PLL responds selectively to the carrier frequencies, which are very close to VCO o/p. Due to coherent detection, high degree of noise immunity.

## FH Detection:

- \* PLL is set locked with the i/p FM signal. Then the VCO frequency will be equal to the instantaneous frequency of FM signal  $f_i(t)$

$$f_i(t) = f_c + k_o V_c$$

 

- \* VCO control voltage  $V_c$  is demodulated FM o/p  $\therefore V_c = f_i(t) - f_c$   
Error voltage controls the VCO to maintain lock with  $\frac{V_c}{k_o}$ .  
the i/p signal.

- \* The instantaneous frequency of the FM signal is given by

$$f_i(t) = f_c + \Delta f_c \sin \omega_m t$$

$f_c$  = carrier frequency,  $\Delta f_c$  = peak frequency deviation,  
 $\omega_m$  = angular frequency of the modulating s/k.

AC Component of  $V_c(t)$  after the capacitor  $C_C$  is

$$V_c(t) = \frac{f_i(t) - f_c}{k_o} = \frac{f_c + \Delta f_c \sin \omega_m t - f_c}{k_o} = \frac{\Delta f_c \sin \omega_m t}{k_o}$$

$$V_c(t) = \Delta f_c \sin \omega_m t / k_o$$

This gives the modulating signal voltage applied to FM carrier at the transmitter

- \* Control voltage of VCO is a linear function of the instantaneous frequency deviation
- \* FM signal is demodulated, almost without any distortion.  
 $\therefore$  PLL can be employed for detection of wideband or narrowband FM s/k


with higher degree of linearity, which cannot be achieved by any other detection methods.

- \* Centre frequency  $f_0$  should be set as close as possible to FM carrier frequency  $f_c$  to achieve maximum symmetrical lock-range.
 
### FSK Modulation / Demodulation:

FSK is type of frequency modulation, in which binary data or code is transmitted by means of a carrier frequency that is shifted between two fixed frequency values,  $f_1$  = logic 0,  $f_2$  = logic 1.

- \* Frequencies corresponding to logic 1 & logic 0  $\Rightarrow$  mark & space.



- \* PLL is designed to remain in-lock with the FSK signal for both the frequencies  $f_1$  &  $f_2$ . Then VCO control voltage fed to the comparator is given by

$$V_{f_1} = \frac{f_1 - f_0}{k_0} \quad V_{f_2} = \frac{f_2 - f_0}{k_0}$$

$$\Delta V_f = \frac{f_2 - f_1}{k_0}$$

- $V_{f_1}$  &  $V_{f_2}$  applied to comparator, one i/p pass through LPF-2.
- filter designed for time constant which is longer than FSK pulse duration to obtain a dc voltage.
- This dc voltage will have value midway between  $V_{f_1}$  &  $V_{f_2}$ .
- FSK s/e  $V_i$  is applied to i/p, loop gets locked to i/p frequency & tracks it in between 2 frequencies  $f_1$  &  $f_2$ .

$$f_1 = \frac{1.45}{(R_A + R_B)C}$$

$$= 1270 \text{ Hz}$$


$$f_2 = \frac{1.45}{(R_A + 2R_B)C} = 1070 \text{ Hz}$$

## Frequency Synthesizing:-

- \* It produces a large number of precise frequencies which are derived from single reference source of frequency, such as stable crystal controlled oscillator.
- \* A Temperature controlled crystal oscillator provides stable reference frequency  $\delta_R$  & i/p signal to phase detector is provided by o/p of VCO.
- \* A  $\div$  by N counter is used in loop.  $\therefore \delta_D = \delta_0/N$ ,  $\delta_0 = \text{o/p frequency of VCO}$ .
- \* In locked condition,  $\delta_R = \delta_D$ .  

$$\therefore \delta_0 = N\delta_R$$
- \* Divide by N counter is realized by programmable divider,  $\therefore$  it is possible to achieve multiples of reference frequency.
- \* Frequency Synthesizing can also be obtained by harmonic locking in which locking is achieved with harmonic of reference signal.
- \* VCO frequency is set to multiple of i/p reference frequency. The VCO锁 with desired harmonic of i/p frequency.

 
Drawback:- lock-in range reduces when successively higher & weaker harmonics are used for locking.



UNIT-IV : ANALOG TO DIGITAL AND DIGITAL TO ANALOG CONVERTERS

ANALOGY AND DIGITAL DATA CONVERSIONS:

 DIGITAL TO ANALOG CONVERTER [D/A CONVERTER (or DAC)]



The input is an  $n$ -bit binary word  $D$  and is combined with a reference voltage  $V_R$  to give an analog output signal.

The output of a DAC can be either a Voltage or Current.

For a voltage output DAC, the D/A converter is mathematically described as,

$$V_o = k V_{FS} \left[ d_1 2^{-1} + d_2 2^{-2} + \dots + d_n 2^{-n} \right]$$

$V_o \rightarrow$  o/p voltage,  $V_{FS} \rightarrow$  full scale o/p vrg.

$k \rightarrow$  scaling factor

$d_1, d_2, \dots, d_n \rightarrow n$ -bit binary Fractional word

$d_1 \rightarrow$  MSB

$d_n \rightarrow$  LSB

## TYPES OF DIGITAL TO ANALOG CONVERTERS [DAC]

- i) Weighted resistor DAC
- ii) R-2R Ladder
- iii) Inverted R-2R Ladder

## WEIGHTED RESISTOR TYPE D/A CONVERTER;

- \* In the weighted resistor type DAC each digital level is converted into an equivalent analog voltage or current.
- \* In a 4-bit DAC which accept data from 0000 to 1111 there are 15 discrete levels of input & hence it is convenient to divide the output analog signal into 15 levels.
- \* The LSB of the digital data causes a change in the analog output that is equal to  $\frac{V_R}{15}$  of full-scale analog output voltage ( $V_R$ )
  - ∴ the weighted resistor network is designed in such a way that a 1 in LSB ( $2^0$ ) position results in  $V_R \times \frac{1}{15}$  of o/p.
  - A '1' in the  $2^1$  bit position must cause a change in the analog o/p voltage that is equal to  $\frac{2}{15} \text{ th}$  of  $V_R$  (i.e., twice the size of LSB).
- \* By
  - 1 in  $2^2 \Rightarrow V_R \times \frac{4}{15} V$
  - 1 in  $2^3 \Rightarrow V_R \times \frac{8}{15} V$
- \* Sum of the weights assigned to various bit position of a 4-bit DAC must be equal to 1 i.e.,  $(\frac{1}{15} + \frac{2}{15} + \frac{4}{15} + \frac{8}{15})V_R = V_{FS}$
- \* In general, the weight assigned to the LSB is  $\frac{1}{(2^n - 1)}$ , where  $n$  = no. of bits in the digital input.

 


Fig: 4-bit weighted Resistor DAC

- The  $2^0$  bit is changed to  $\frac{1}{15}$ th of  $V_R$ ,  $2^1$  bit to  $\frac{2}{15}$ th of  $V_R$ ,  $2^2$  bit to  $\frac{4}{15}$ th of  $V_R$  &  $2^3$  bit to  $\frac{8}{15}$ th of  $V_R$ .
  - These 4 voltages are added together to form the analog output voltage using an op-amp summer circuit.
- The resistor  $R_0, R_1, R_2$  &  $R_3$  from the voltage divider network connected with the opamp and  $R_L$  is the load resistor which should be large enough so as to not to load the divider network.
  - LSB connected with highest i/p resistance  $R_0$  while  $2^1$  bit is connected with a resistance of half the value of LSB resistor i.e.,  $R_0/2$ .  
 $\therefore$  its current contribution at the summing junction of op-amp will be twice that of LSB.  
 why  $2^2$  bit connected to  $\frac{1}{4}$ th of LSB resistance =  $R_0/4$   
 $2^3$  bit " "  $\frac{1}{8}$ th of " " =  $R_0/8$ .
  - O/p is the sum of these 4 attenuated voltages.

### Operating Principle:

I Illustration: The equivalent circuit, when applied with the digital data of 0001 is shown below.

 


Fig: Equivalent circuit of a 4bit weighted resistor DAC for Input 0001

- The analog o/p voltage  $V_0$  can be calculated using ~~Milman's~~ theorem, which states that the voltage at any node in a resistive network is equal to the sum of current entering the node

divided by the sum of the conductance connected at the node.

Then O/p voltage is

$$V_o = \frac{\frac{V_R}{R_1} + \frac{V_R}{R_2} + \frac{V_R}{R_3} + \frac{V_R}{R_4}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} - \textcircled{1}$$

\* for the weighted resistor network, assuming  $R_1 = R$ ,  $R_2 = R/2$ ,  $R_3 = R/4$ ,  $R_4 = R/8$  & apply Millman's theorem to the circuit, we get.

$$V_o = \frac{\frac{V_R}{R} + \frac{V_R}{R/2} + \frac{V_R}{R/4} + \frac{V_R}{R/8}}{\frac{1}{R} + \frac{1}{R/2} + \frac{1}{R/4} + \frac{1}{R/8}} - \textcircled{2}$$

 


Fig: n-Bit weighted Resistor DAC.

for 0 = 111  
MSB      LSB

\* The above diagram is an n-bit DAC using opamp as a summing amplifier.

\* It employs a binary weighted resistor network to generate the term  $b_i 2^{-i}$  where  $i = 1, 2, \dots, n$ .

\* The circuit also uses n-electronic switches controlled by the binary input word  $b_1, b_2, \dots, b_n$  and reference voltage  $V_R$ .

\* Switches are of single pole double throw (SPDT) type.

\* If binary ip is 1, then switch connects to resistance to the reference voltage  $-V_R$ ; if 0  $\rightarrow$  to Ground.

Considering an ideal opamp A, o/p current  $I_o$  is

$$I_o = I_1 + I_2 + \dots + I_n.$$

$$= \frac{V_R}{2^1 R} b_1 + \frac{V_R}{2^2 R} b_2 + \dots + \frac{V_R}{2^n R} b_n.$$

$$= \frac{V_R}{R} [b_1 \bar{2}^1 + b_2 \bar{2}^2 + \dots + b_n \bar{2}^n]$$


Then o/p voltage  $V_o = I_o R_f$ .

$$= \frac{V_R R_f}{R} [b_1 \bar{2}^{-1} + b_2 \bar{2}^{-2} + \dots + b_n \bar{2}^{-n}] \quad \text{--- (3)}$$

Using Eq:  $V_o = KV_{FS} (b_1 \bar{2}^1 + b_2 \bar{2}^2 + \dots + b_n \bar{2}^n)$  --- (3).

it is seen that  $R_f = R$ , then  $K = 1$ ,  $V_{FS} = V_R$ .

 - \* The n-bit DAC ckt, uses a negative reference voltage, thus producing a positive staircase voltage.
- \* The analog o/p voltage waveform for 3-bit weighted resistor DAC is shown.



\* It can be noted that.

- ↳ DAC o/p is result of multiplying the analog signal  $V_R$  by digital data. ∴  $V_R$  is made variable, then DAC is called multiplying DAC [MDAC].
- ↳ Higher the value of  $n$ , finer is the resolution of conversion, & closer is the staircase to a continuous ramp waveform.
- ↳ DAC available for 6 bit to 8 bits.
- ↳ Op-amp can be connected to non-inverting mode also.
- ↳ Op-amp is operated as current to voltage converter.
- ↳ Polarity of  $V_R$  is chosen depending on switches to be operated
- ↳ Accuracy & stability of DAC based on accuracy of resistors & their temperature dependence & also to handle varying current based on bit values.

When I/P is DDI  
MSB 130  
DDI

$$b_1 = 0, b_2 = 0; b_3 = 1$$

$$V_D = k V_{FS} \left[ b_1^{-1} + b_2^{-2} + b_3^{-3} \right]$$
$$V_D = 1 (V_{FS}) \left[ 0 (2^{-1}) + 0 (2^{-2}) + 1 (2^{-3}) \right]$$

$$k=1 \quad \& \quad V_{FS} = 8V = V_R$$

$$V_D = V_R \left[ 2^{-3} \right]$$

$$V_D = \frac{V_R}{2^3} = \frac{V_R}{8}$$

$$V_D = \frac{8}{8} = 1V$$

- (3)
- Disadvantage:
- ↳ Requirement of wide range of resistor values.
  - ↳ As the length of binary word is increased, the range of resistor values needed also increases.
  - ↳ Fabrication of such large value of resistors of order of  $M\Omega$  is not practically possible.
  - ↳ Voltage drop variation affects accuracy.

### R-2R Ladder DAC

- \* A wide range of resistor value is required in the design of binary weighted resistor DAC.
- \* In R-2R ladder DAC resistors of only 2 values i.e.,  $R$  &  $2R$  are used. hence suitable for integrated circuit fabrication.
- \* Typical value of  $R$  vary from  $2.5k\Omega$  to  $10k\Omega$ .
- \* The principle of operation of a ladder type n/w for 4 bit DAC is shown with binary i/p  $b_1, b_2, b_3, b_4$  & analog o/p  $V_o$
- ↳ One terminating resistor.
- \* In this ladder circuit, the o/p voltage is a weighted sum of digital input.

Ex: 4 bit binary i/p

$$b_1 b_2 b_3 b_4 = 1000 \text{ i.e.,}$$

$$\text{MSB} = 1, \text{ other i/p} = 0.$$

Modified circuit is shown.

- \* The terminating resistor ( $2R$ ) and resistor connected to  $b_4$  i/p ( $2R$ ) are combined at node  $N_1$  to form an equivalent resistor  $R$  as shown in 1st stage.

 


Fig: 4bit R-2R ladder type DAC


 


Fig: Equivalent Ckt for binary  
 $b_1 b_2 b_3 b_4 = 1000$

 \* Then node  $N_2$ , the resistor connected with  $b_3$  i/p ( $2R$ ) can be combined with resistor ( $R+R=2R$ ) to form the 2nd stage of equivalent circuit is shown.



Why at  $N_3$ , the equivalent circuit of 2nd stage., where equivalent resistor  $R$  is obtained.


Then, the analog o/p voltage  $V_o$  is.

$$V_o = \frac{V_R \times 2R}{R+R+2R} = \frac{V_R}{2} \quad - (4)$$

Thus for digital i/p  $b_1 b_2 b_3 b_4 = 1000$

$$V_o = V_R/2.$$

 Why for  $b_1 b_2 b_3 b_4 = 0100 \Rightarrow V_o = V_R/4$   
 $b_1 b_2 b_3 b_4 = 0010 \Rightarrow V_o = V_R/8$   
 $b_1 b_2 b_3 b_4 = 0001 \Rightarrow V_o = V_R/16$




Since the resistive ladder is a linear network, the principle of superposition can be used to find the total analog o/p voltage for a particular digital i/p by adding the o/p voltages caused by individual digital i/p's.

$$n\text{-bit DAC is. } V_o = \frac{V_R}{2^1} + \frac{V_R}{2^2} + \dots + \frac{V_R}{2^n} \quad - (5)$$

$n$  = total of bits at the i/p.

- \* The practical arrangement of 1 bit DAC using op-amp is shown.
- \* The inverting i/p terminal of the op amp act as summing junction for the ladder inputs.
 
$$\text{Using eq (5)} \quad V_o = -V_R \frac{R_2}{R} \left( \frac{b_1}{2^1} + \frac{b_2}{2^2} + \frac{b_3}{2^3} + \frac{b_4}{2^4} \right) \quad - (6)$$



$$V_o = -V_R \frac{R_f}{R_{x24}} [b_1 2^3 + b_2 2^2 + b_3 2^1 + b_4 2^0]$$

Q1 Generally for an n-bit i/p signal.

$$V_o = -\frac{V_R}{2^n} (b_1 2^{n-1} + b_2 2^{n-2} + \dots + b_n 2^0)$$

The resolution of  $R/2R$  ladder type DAC, with current o/p is


$$\text{Resolution } I = \frac{1}{2^n} \times \frac{V_R}{R}$$

The resolution of the  $R/2R$  ladder type DAC with voltage o/p is

$$\text{Resolution } V = \frac{1}{2^n} \times \frac{V_R}{R} \times R_f$$

$R_f$  = feedback resistance.

Fig: Four Bit  
 $R/2R$  Ladder  
DAC

 

Voltage Mode R-2R Ladder

 


Fig: Voltage-mode R-2R ladder  
DAC

- \* Shows the alternate circuit arrangement of the R-2R ladder type called voltage-mode R-2R ladder D/A converter.
- \* The 2R resistors are switched between the two voltage levels  $V_L$  and  $V_H$  as determined by the bit values  $b_1, b_2 \dots b_n$ .
- \* The output from ladder is obtained at the left most ladder node, buffered at the op of op-amp.
- \* The two voltages  $V_L$  and  $V_H$  can be any 2 voltage levels.
- \* As the  $Y_p$  binary word changes from 0...0 (all 0 bits) to 1...1 (all 1 bits), the voltage of node S changes correspondingly in step of  $2^{-n} (V_H - V_L)$  from the minimum voltage of  $V_O = V_L$  to the maximum of  $V_O = V_H - 2^{-n} (V_H - V_L)$ .

Advantages of R-2R type DAC are:

- i) more accurate selection and design of resistor R and 2R are possible and
- vii) the binary word length can be increased by adding required number of R-2R sections.

### Inverted or Current-mode R-2R Ladder DAC

 


Fig: Inverted or Current-mode R-2R Ladder DAC

- \* In weighted resistor and R-2R ladder type of DAC the current flowing through the resistors changes as the input data changes.

- \* Power dissipation causes heating, and non-linearity of D/A converter arises due to varying power dissipation values corresponding to bit patterns.
- \* This becomes a serious limitation as the word length increases. This is eliminated in the inverted R-2R ladder type of D/A converter.
- \* The bit position of each of the subsequent MSBs and LSBs are interchanged.
- \* Each binary i/p is connected through the switch to either ground or to inverting i/p terminal of op amp, which is at virtual ground.
- \* Since both the positions of switch bi are at ground potential i.e., the actual or virtual ground, the current flow through any resistor is constant and it is independent of the i/p binary bit value.

These currents can be represented as,

$$I_1 = \frac{V_R}{2R} \quad - \textcircled{7}$$

$$I_2 = \frac{(V_R/2)}{2R} = \frac{V_R}{4R} = \frac{I_1}{2} \quad - \textcircled{8}$$

$$I_3 = \frac{(V_R/4)}{2R} = \frac{V_R}{8R} = \frac{I_1}{4} \quad - \textcircled{9}$$

$$\vdots I_n = \frac{(V_R/2^{n-1})}{2R} = \frac{I_1}{2^{n-1}} \quad - \textcircled{10}$$

Output voltage  $V_O$  is

$$V_O = -I_0 \times R_f.$$

$$= -R_f (I_1 + I_2 + I_3 + \dots + I_n)$$

$$= -\frac{V_R R_f}{R} (b_1 2^{-1} + b_2 2^{-2} + \dots + b_n 2^{-n})$$

$$\text{When } R_f = R; \quad V_O = -V_R (b_1 2^{-1} + b_2 2^{-2} + \dots + b_n 2^{-n})$$


- \* The circuit operation on the principle of summation of the currents. Hence it is called R- $\Delta$ R ladder current mode type of DAC.
- \* The current divides equally in successive nodes. The current flow in individual arms of the network remains the same irrespective of binary bit pattern.
- ∴ currents are maintained constant in all the branches and the ladder node voltages also remain constant at  $V_R/2^n$ ,  $V_R/2^{n-1}$ ,  $V_R/2^{n-2}$  ...  $V_R/2^1$ .
- \* Op-amp is used as a I-V converter & total current  $I_0$  is determined by binary word.

Advantage:

- Stray capacitances do not affect the speed of response of the circuit due to the constant ladder node voltages.
- Hence speed performance is improved.
- Capability of using any 2 voltage level for the bit switching, neither of which needs necessarily be zero.
 
### High Speed Sample and Hold Circuit

- \* The basic principle of sample and hold circuit is dealt with is shown below fig, shows a sample and hold circuit for high speed of operation.




## High Speed Sample and Hold circuit

\* The basic principle of sample and hold circuit is dealt with is shown below fig , shows a sample and hold circuit for

high speed of operation.

Sample - and  
Hold Circuit

 

changes.

- \* The MOS transistor M shown is an analog switch capable of switching by logic levels, such as that from TTL.
- \* It alternately connects and disconnects the capacitor  $C_1$  to the o/p of op-amp  $A_1$ .
- \* Diode  $D_1$  &  $D_2$  are inverse-parallel connected. They prevent op-amp  $A_1$  from getting into saturation when the transistor M is OFF.
- \* This makes the operation of the circuit faster. Hence, the o/p of op-amp  $A_1$  will be  $V_o'(t) = V_i(t) - 0.7V$  when  $V_i(t) < V_o(t)$  and  $V_o'(t) \approx V_i(t) + 0.7V$  when  $V_i(t) > V_o(t)$ .
- \* When transistor M is ON, op-amps  $A_1$  &  $A_2$  act as voltage follower.
- \* The waveform is shown in below figure, it illustrate the operation of the circuit.
- \* The transistor M is alternately switched ON and OFF by the control voltage  $V_S$  at the gate terminal.
- \* Note that the voltage  $V_S$  is to be higher than the threshold voltage of FET.
- \* When the transistor switch M is ON for a short interval of time, the capacitor  $C_1$  quickly charges or discharges to the value of the analog signal at that instant.
- \* When input  $V_i$  is larger than capacitor voltage  $V_C$  and the transistor M is OFF, it rapidly charges to the level of  $V_i$  the instant M switches ON.  
Why if  $V_C$  is initially greater than  $V_i$  then  $C_1$  rapidly discharges to the level of  $V_i$  when M becomes ON.
- \* When M is OFF, only the input bias current of opamp  $A_2$  & the gate-source reverse leakage current of FET are effective in discharging the capacitor.

- \* Hence, the damped voltage is held constant by  $C_1$  until the next sampling instant or acquisition time.
- \* The below fig shows the sampling or acquisition time  $t_1$  and holding time  $t_2$ .
- \* During the sampling time  $t_1$ ,  $C_1$  is charged through the FET channel resistance  $R_{DS(on)}$ , and the charging time  $t_1 = 5 R_{DS(on)} C_1$ . When the capacitor charges to 0.993 of input voltage.
- \* During the hold time  $t_2$ , the capacitor partially discharges.


 
 


Fig : Capacitor Voltage waveform

Fig : Signal voltage, control voltage & output voltage waveforms.

- \* This is called hold-mode droop. To avoid this, Op amp  $A_2$  must have very low i/p bias current, the capacitor should have a low leakage dielectric and  $M$  must have very low reverse leakage current between its gate and source terminals.
- \* The low channel resistance  $R_{DS(on)}$  is desirable for the FET to achieve faster charging & discharging of  $C_1$ .
 
## ANALOGY TO DIGITAL CONVERTER: [A/D CONVERTER]



Schematic of ADC

The input is an analog signal and output is digital word.

The output digital word is generated with respect to reference voltage  $V_R$  and i/p s/d.

The functional value of D is.

$$D = d_1 \cdot 2^{-1} + d_2 \cdot 2^{-2} + d_3 \cdot 2^{-3} + \dots + d_n \cdot 2^{-n}$$

$d_1 \rightarrow \text{MSB}$  &  $d_n \rightarrow \text{LSB}$

Types:

- (i) Direct Type ADC [directly converts A to D]
- (ii) Indirect type ADC. [Initially converts A to (an Integrating Type ADC time & frequency and then converts to D)]
- (iii) Direct Type ADC
  - 1. Flash Type [comparator type] converter
  - 2. Counter Type converter
  - 3. Tracking (or) servo converter
  - 4. Successive Approximation type converter
- (iv) Integrating Type ADC:
  - 1. charge Balancing ADC
  - 2. Dual slope ADC.

## SIMULTANEOUS TYPE (FLASH TYPE) A/D CONVERTER

- \* The simultaneous type ADC is based on comparing an unknown analog i/p voltage with a set of reference voltages.
- \* To convert an analog signal into a digital signal of  $n$  output bits,  $(2^n - 1)$  number of comparators are required.
- \* For e.g.: 2 bit ADC requires 3 or  $(2^2 - 1)$  comparators, while 3 bit require 7 or  $(2^3 - 1)$  comparators.

- \* Block Diagram of a  $n$  bit simultaneous type ADC is shown.

 


Table: Comparator & Digital o/p for a 2 bit simultaneous type ADC

Analog I/p voltage ( $V_i$ )	Comparator o/p			Digital o/p	
	$C_1$	$C_2$	$C_3$	$b_2$	$b_1$
$0 \leq V_i \leq V/4$	0	0	0	0	0
$V/4 \leq V_i \leq V/2$	1	0	0	0	1
$V/2 \leq V_i \leq 3V/4$	1	1	0	1	0
$3V/4 \leq V_i \leq V$	1	1	1	1	1

- \* As shown in fig, the 3 opamps are used as comparators.
- \* The non-inverting inputs of all the three comparators are connected to the analog input voltages.
- \* The inverting input terminal of the opamps are connected to a set of reference voltages  $V_A$ ,  $2V_A$  &  $3V_A$  respectively, which are obtained using a resistive divider network & power supply  $+V$ .
- \* The output of a comparator is in positive saturation state when the voltage at the non-inverting i/p terminals is more than the voltage at the inverting terminal and it is in negative saturation state otherwise.
- \* When the analog i/p voltage is less than  $V_A$ , the voltage at the non-inverting terminals of the 3 comparators is less than their respective inverting input terminal voltages. Hence, the comparator o/p are  $c_1 c_2 c_3 = 000$ .
- \* When analog i/p is between  $V_A$  &  $V_B$ , the comparator o/p's are  $c_1 c_2 c_3 = 100$ .
- \* Since there are 4 ranges of analog i/p voltages, this can be coded using 2 bit digital o/p ( $b_2 b_1$ ).
- \* The coding circuit for encoding the 3 comparator o/p into 2 digit o/p's is shown inside the dotted square. Using the simplified expressions for  $b_1$  &  $b_2$ .
- \* The logic expressions for  $b_2$  &  $b_1$  can be written as
 
$$b_2 = c_1 c_2 \bar{c}_3 + c_1 \bar{c}_2 c_3 = c_1 c_2 (\bar{c}_3 + c_3) = c_1 c_2$$

$$b_1 = c_1 \bar{c}_2 \bar{c}_3 + \bar{c}_1 c_2 c_3 = c_1 (c_2 \oplus c_3)$$
- \* Now, 3 bit ADC can be constructed using seven ( $2^3 - 1$ ) comparators.
- \* The comparators & digital o/p for 8 different ranges of analog i/p voltage are given below.

 


Fig. Block diagram of  
3 bit simultaneous type  
ADC.

Analog Input voltage $V_i$	Comparator o/p							Digital o/p		
	$C_1$	$C_2$	$C_3$	$C_4$	$C_5$	$C_6$	$C_7$	$b_3$	$b_2$	$b_1$
$0 \leq V_i \leq V/8$	0	0	0	0	0	0	0	0	0	0
$V/8 \leq V_i \leq 2V/8$	1	0	0	0	0	0	0	0	0	1
$2V/8 \leq V_i \leq 3V/8$	1	1	0	0	0	0	0	0	1	0
$3V/8 \leq V_i \leq 4V/8$	1	1	1	0	0	0	0	1	1	1
$4V/8 \leq V_i \leq 5V/8$	1	1	1	1	0	0	0	1	0	0
$5V/8 \leq V_i \leq 6V/8$	1	1	1	1	1	0	0	1	0	1
$6V/8 \leq V_i \leq 7V/8$	1	1	1	1	1	1	0	1	1	0
$7V/8 \leq V_i \leq V$	1	1	1	1	1	1	1	1	1	1

\* It is clear that the logic expression for ( $b_3$ ,  $b_2$ , and  $b_1$ ) are complex due to their dependence on seven input variables ( $C_1$ ,  $C_2$ , ...,  $C_7$ )

\* Hence, the coding circuit is implemented using a priority encoder.

\* IC74148 is an 8 to 3 priority encoder with active LOW i/p 20/p's

\* Since the temperature o/p's are active HIGH, they are connected to the i/p's of encoder through inverters and the o/p's of encoder are inverted once again to get active HIGH digital o/p's  $b_3$ ,  $b_2$  and  $b_1$ .

### Advantages:

\* Simultaneous type ADC is the fastest because ADC is performed simultaneously through a set of comparators. Hence, it is also called Flash type ADC.

(Typical) conversion time is 100ns or less

\* Construction is simple and easier to design.

### Disadvantages:

\* The simultaneous type ADC is not suitable for ADC with more than 3 or 4 digital o/p bits.

\* Total ( $2^n - 1$ ) comparators are required for an n-bit ADC and number of comparators required doubles for each added bit.

 


Fig: Logic Diagram of 3-bit Simultaneous type ADC

## SUCCESSIVE APPROXIMATION TYPE ADC

QUESTION NO. 7

- \* Conversion time is maintained constant in an successive approximation type ADC and it is proportional to the number of bits in the digital O/P, unlike the counter and continuous type ADC.
- \* The basic principle of this ADC is that the unknown analog i/p voltage is approximated against an n-bit digital value by taking one bit at a time, beginning with the HSB.
- \* The principle of successive approximation process for a 4bit conversion is shown below.

 


Fig: Principle  
of  
4 bit  
digital  
O/P.

- \* This type of ADC operates by successively dividing the voltage range by half, as explained in the following steps.
- ↳ The HSB is initially set to 1 with remaining 3 bits set to 0. The digital equivalent is compared with the unknown analog i/p voltage.
- ↳ If the analog i/p voltage is higher than the digital equivalent, the HSB is retained as 1 and the second HSB is set to 1. Otherwise, the HSB is reset to 0 and second HSB is set to 1.
- ↳ Comparison is made as given in step 1 to decide whether to retain or reset the 2nd HSB. The 3rd HSB is set to 1 and the operation is repeated down to LSB and by this time, the converted digital value is available in the SAR.
- \* From above figure., it can be seen that the conversion time is constant (i.e. 4 cycle for 4 bit ADC) for various digital O/P's

- \* This method uses a very efficient search strategy to complete an n-bit conversion in just n-clock periods.
- \* ∴ for an 8-bit successive approximation type ADC, the conversion requires only 8 cycles, irrespective of the amplitude of analog i/p voltage.
- \* The functional block diagram of successive approximation type ADC is shown below.

 



Fig: Functional Block Diagram of Successive Approximation Type ADC

- \* The circuit employs a successive approximation register (SAR) which finds the required value of each successive bit by trial & error method.
- \* The o/p of SAR is fed to an n-bit DAC.
- \* The analog o/p equivalent to digital to analog converter is applied to the non-inverting i/p of the comparator, while the other i/p of the comparator is connected with an unknown analog i/p voltage  $V_i$  under conversion.
- \* The comparator o/p is used to activate the successive approximation logic of SAR.
- \* When the START command is applied, SAR sets the MSB ( $b_1$ ) of the digital signal, while the other bit made zero, so that the trial code becomes 10000000.
- \* The o/p of SAR is converted into analog equivalent  $V_r$  and gets compared with the i/p signal  $V_i$ .

- \* If  $V_i$  is greater than DAC o/p, then the trial code is less than the correct digital value.
- \* the MSB is retained as 1 and the next significant bit is made 1 and the testing is repeated.
- \* If the analog i/p  $V_i$  is now less than DAC o/p, then the value 11000000 is greater than the exact digital equivalent.
- \* Therefore, the comparator resets the second MSB to 0 and proceeds to the next most significant bit.
- \* This process is repeated for all the remaining lower bits in sequence until all the bit position are tested.
- \* The EOC signal is sent out when all the bits are scanned and the value of DAC o/p just crosses  $V_i$
- \* Table below shows the flow of conversion sequence and Fig shows the o/p response with the associated waveforms.

Correct Digital Representation	Successive Approximation Register (SAR) o/p $V_i$ at different stages in the conversion	Comparator o/p.
11010100	1000 0000	1 (Initial o/p)
	1100 0000	1
	1110 0000	0
	1101 0000	1
	11011 000	0
	11010 100	1
	11010110	0
	11010101	0
	11010100	0

 - \* It can be observed that the DAC o/p voltage gets successively closer to the analog i/p voltage  $v_i$ .
- \* For 8-bit ADC, it requires 8 pulses to compute the o/p irrespective of the value of the analog i/p.
- \* AD1582  $\rightarrow$  12 bit ADC  $\rightarrow$  successive approximation technique used a 28-pin DIP CMOS package.




## Single Slope Type ADC

11

- \* If short conversion time is not important, one can consider single or dual slope type A/D converter.
- \* These converter techniques are based on comparing the unknown analog i/p voltage with a reference voltage that begins at 0V & increases linearly with time.
- \* The time required for the reference voltage to reach the value of unknown analog i/p voltage is proportional to the amplitude of unknown analog i/p voltage.
- \* This time period can be measured using digital counter.
- \* The block diagram of single slope type ADC is shown.

Fig: Block Diagram of Single Slope ADC.

 

- \* The main circuit of this converter is a ramp generator, which on receiving a RESET from the control circuit increases linearly with time from 0V to a maximum voltage  $V_m$ .
- \* For eg: if  $V_m = 10V$  and it takes 1ms to move from 0V to 10V, then the slope is  $10V/ms$ .
- \* Such a ramp generator can be either an opamp based integrator circuit or DAC driven by a sequence binary counter, whose o/p waveform

is a staircase increasing linearly. The operation of this converter is explained

- \* Assume that a positive analog i/p voltage  $V_i$  is applied at the non-inverting input of the comparator.
- \* Now, when a RESET signal is applied to the control logic, the 4 digit decade counter reset to 0 and the ramp voltage begins to increase.
- \* Since  $V_i$  is positive, the comparator o/p is in HIGH state.
- \* This allows the CLK pulse to pass to the i/p of the 4 digit counter through the AND gate and the counter is incremented.
- \* This process continues until the analog i/p voltage is greater than the ramp generator voltage.
- \* When the ramp generator voltage is equal to the analog i/p voltage, the comparator o/p becomes negatively saturated or logic 0 and the clock is prevented from passing through the gate, casing the counter operation.
- \* Then the control circuit generates a STROBE signal, which latches the counter value in the 4 digit latch, which is displayed on 7-segment displays.
- \* The displayed value is then equivalent to the amplitude of analog i/p voltage.

For e.g. Clock value  $C_{CK} = 1\text{MHz}$ , Slope of the ramp generator is  $1V/\mu\text{s}$ , A digit decade counter reaches its full scale value i.e. 9999 in  $9999\mu\text{s} \Rightarrow 9.999\text{ms}$ , ramp generator voltage reaches  $9.999\text{V}$ .

- \* So this single slope type ADC can display any analog i/p value from 0V to 9.999V.
- \* If  $V_i = 5.62V$ , counter require 5620 clock pulse to advance from 0000 to 5620., ramp voltage raise to 5.62V.  
 $\therefore$  Display 5620.  $\Rightarrow 5.62V$ .

### Disadvantage:

- $\rightarrow$  Due to component value error and clock errors.
- $\rightarrow$  Integrated o/p voltage is a function of the product of R & C.  
 $\therefore$  Changes in the value of capacitance & Resistance due to temperature affect the integrated o/p & introduce error.
- $\rightarrow$  Drift in clock frequency cause error.

### Dual slope Type ADC

- \* In dual slope type ADC, the integrator generates two different ramps, one with the unknown analog i/p voltage  $V_i$  as the i/p and another with a known reference voltage  $-V_R$  as the i/p.
- \* Hence it is called dual slope type ADC.
- \* The operation of dual slope type ADC is explained as follows.
- \* Assume that the 4-digit decade counter is initially reset to 0000, the ramp o/p  $V_R$  is reset to 0V, analog i/p voltage is positive, and the i/p to the ramp generator or integrator is switched to the unknown analog i/p voltage.
- \* Since the positive analog i/p voltage is connected to the inverting i/p of the integrator, the integrator o/p  $V_S$  is a negative ramp while the comparator o/p  $V_g$  is positive and CLK passed through the AND gate

- \* This results in counting-up of the 4-digit decade counter.
- \* The negative stamp will proceed for a fixed time period  $T_1$ , which is determined by a count detector for the time period  $T_1$ .
- \* At the end of fixed time period  $T_1$ , the ramp voltage is given by

$$-V_g = \frac{V_i}{Rc} \times T_1$$

$Rc$  = Time constant of the stamp generation circuit.

 


Fig: Dual Ramp Output Waveform

- \* when the counter reaches the fixed count at time period  $T_1$ , the count detector gives a signal to the control circuit which in turn resets the counter to 0 and switches the integrator i/p to a negative reference voltage ( $-V_R$ ).
- \* Now, the ramp generator begins at  $-V_S$  and increase upward until it reaches 0V.
- \* During this time, the counter gets advanced
- \* When  $V_S$  reaches 0V, the comparator o/p will become 0 and the CLK is inhibited from passing through the AND gate.
- \* Now, the conversion cycle is said to be completed and the positive ramp voltage is given by

$$V_S = -\left(\frac{-V_R}{R_C} \times T_2\right)$$

$V_R$  &  $R_C$  are constant & time period  $T_2$  is variable.

- \* Since the ramp generator voltage starts at 0V, decreasing down to  $-V_S$  and then increasing up to 0V, the amplitude of negative and positive ramp voltages can be equated as follows,

$$-\frac{V_i}{R_C} \times T_1 = \frac{V_R}{R_C} \times T_2$$

$$-V_i = V_R \times \frac{T_2}{T_1}$$

- \* From the above equation, it is clear that the unknown analog i/p voltage is proportional to the time period  $T_2$ , because  $V_R$  is known reference voltage and  $T_1$  is the predetermined time period.


- \* Also the contents of the 4-digit decade counter at the end of conversion reflect the variable time period  $T_2$ .

## ANALOG TO DIGITAL CONVERTER USING VOLTAGE TO TIME CONVERSION

- \* An analog signal can be converted into digital signal by counting the pulses from a variable frequency source whose frequency is dependent on the analog i/p signal value.
- \* The counting is done for a fixed period of time.
- \* Alternatively, the pulses from a fixed frequency source can be counted for a variable period of time, and the time period is then dependent on the analog signal under conversion.


Fig. Functional Block

Diagram

 

- \* The above figure shows such an ADC. It employs an integrator, a sample & hold (S/H) circuit, a voltage comparator and high speed counter.
- \* A negative reference voltage  $V_R$  is applied to the integrator, which integrates the voltage  $V_R$  and provides a positive polarity o/p.

Fig. Input & output Waveform

 

- \* The analog signal  $i_p$  under conversion  $V_i(t)$  is sampled at a rate fixed by the control voltage  $V_c$ , and the sampled signal at any instant  $V_i$  is applied as  $i_p$  to the non-inverting terminal of comparator.
- \* The integrator o/p  $V_s$  is connected to the inverting i/p of comparator.
- \* When the integrated voltage  $V_s$  is less than the analog voltage sample  $V_i$  as shown, the comparator o/p is at positive saturation or at  $V_i$  as shown. ( $V_s < V_i$ ) =  $V_{sat}$  or 1 logic 1.
- \* A fixed frequency clock  $V_{cr}$  is applied to the high speed counter through the AND Gate  $G_1$ .
- \* The AND gate is enabled for the duration from  $t=0$  when  $V_i=0$  to the time  $t=T$  when  $V_g=V_i$ .
- \* W.K.T  $V_g = \frac{V_R t}{\tau}$  where time constant is given by  $\tau = R C$  for integrator.

∴ at time  $t=T$  when  $V_g=V_i$ , we can infer

$$T = \frac{\tau V_i}{V_R}$$

Assuming  $f_c$  is the clock frequency, the count o/p  $N$  obtained during the time interval 0 to  $T$  is given by

$$N = F_c T = \frac{T F_c V_i}{V_R}$$

Hence, the count value  $N$  is proportional to  $V_i$ .

- \* The Sample & Hold circuit samples the +ve i/p voltage  $V_i(t)$  for every  $T_A$ .
- \* Then the sampled voltage  $V_i$  is held for a time duration indicated by  $T_H$ .
- \* During the period  $T_H$ , switch  $S$  is held open, and the integrator operates with its o/p following a ramp voltage waveform  $V_s$ .
- \* When  $V_s < V_i$ , the comparator o/p  $V_g = 1$ , Gate G1 is enabled, with  $V_C = 0$  state.
- \* This continues for a time interval  $T$  and during this time, the clock pulse are passed by the gate G1 to the high speed counter.
- \* Thus the digital o/p of the counter is directly proportional to  $T$ .
- \* During this time interval  $T_A$ , the gate is disabled, and the digital o/p is read from the counter.
- \* The switch  $S$  is closed during  $T_A$ , the capacitor discharges, resetting  $V_s$  to 0V thus starting a new conversion.


## Oversampling A/D converter

- \* Analog circuitry forms the most important part of a data converter.
- \* The resolution and speed of the data conversion are limited by the component mismatch and non-linearity of the components, drift, ageing, noise, dynamic limitation and parasitic.
- \* Hence, over-sampling converters employing more complex digital circuitries are used.
- \* They sample the analog signal at a rate much higher than the sampling rate normally required with Nyquist converters.
 
## DELTA MODULATION (DM)

- \* DM developed in 1940's is a differential pulse-code modulation (DPCM) technique, in which the derivation of the signal is quantized.
- \* When signal variations between the subsequent samples periods are very small, the word length of the quantizer can be reduced.
- \* With very high over-sampling rate, the changes between sample periods are made very small, and the quantizer can be reduced to low-bit.
- \* A 1-bit DPCM coder is known as a delta modulator (DM).
- \* DM codes the difference in the signal amplitude instead of the signal amplitude itself.
- \* The delta modulator A/D converter has the following processes:
  - ↳ The analog signal is approximated with a series of segments.




- ↳ Each segment of the approximated signal is compared with the original analog wave to determine the increase or decrease in relative amplitude.
- ↳ The decision process of establishing the state of successive bit is determined by this comparison.
- ↳ Only the state related to change of information is sent, and a no-change condition causes the modulated signal to remain at the same on state of the previous sample.
- ↳ Examples of delta Modulation technique are.
  - Continuously Variable Slope delta modulation.
  - Sigma delta Modulation
  - Differential Modulation.
- \* Delta modulation (DM) may be viewed as a simplified form of DPCM in which a 2 level (1 bit) quantizer is used in conjunction with a fixed first-order predictor.
- \* A DM encoder is shown below. It is known as a single integration modulator.
- \* The i/p signal is compared with the integrated o/p pulses and the delta (difference) signal is applied to the quantizer.
- \* The quantizer generates a positive pulse when the difference signal is negative and it generate a negative pulse when the difference signal is positive.
- \* The positive signal moves the integrator step by step closer to the present value of i/p, tracking the derivative of the o/p signal.



Delta Modulation Encoder

The DM is based on quantizing the change in the signal from sample to sample rather than the absolute value of the signal at each sample.

- \* Since the o/p of the integrator in the feedback loop of figure tries to predict the i/p  $x(t)$ , the integrator works as a predictor.
- \* The prediction error term  $x(t) - \bar{x}(t)$  in the current prediction is quantized and it is used to make the next prediction.
- \* The quantized prediction error which is the delta modulation o/p is integrated in the receiver just as it is in the feedback loop.
- \* i.e., the receiver predicts the i/p signals as shown.
- \* The predicted signal is smoothed with a low pass filter.

   

- \* The delta modulators exhibit slope overload for rapidly rising i/p signals, and their performance is thus dependent on the frequency of the i/p signal.
- \* In theory, the spectrum of quantization noise of the prediction error is flat and the noise level is set by the 1-bit comparator.

### Slope Overload Distortion:

The slope overload distortion is introduced due to the use of a step size delta that is too small to follow some portions of the waveform with a steep slope. It can be reduced by increasing the step size.

## Granular Noise :

The Granular noise results from using a step size that is too large in parts of the waveforms having a small slope. The granular noise can be reduced by decreasing the step size.

- \* An alternative solution is to employ a variable step size that adapts itself to the short - term characteristics of the source signal. Here, the step size is increased relatively small slope. This strategy is called Adaptive Delta Modulation (ADM).

## Sigma-Delta ( $\Sigma-\Delta$ ) Modulator

- \* DTM requires two integrators for modulation and demodulation processes as shown.
- \* Since integration is a linear operation, the second integrator can be moved ~~from~~ before the modulator without altering the overall  $y_p$ - $y_p$  characteristics.
- \* Furthermore, the 2 integrators in fig., can be combined into a single integrator by the linear operation properly as shown.
- \* The arrangement shown is called a Sigma-Delta ( $\Sigma-\Delta$ ) modulator and its S-domain equivalent.
- \* This structure can be considered as being a smoothed version of a 1-bit delta modulator.
- \* The name sigma-delta modulator comes from the principle of placing the integrator (sigma) before the delta modulator.
- \* Sometimes, the ( $\Sigma-\Delta$ ) modulator is referred to as an interpolative coder.
- \* The quantization noise characteristic or the noise performance of such a Coder is frequency dependent in contrast to the delta modulation.

# LIC - UNIT - V → WAVEFORM GENERATORS.

R. Sma

## Introduction :-

### SPECIAL FUNCTION IC's


- \* The op-amps are widely used in circuits for generating various waveforms.
- \* Analog and digital equipments require one (or) more periodic waveforms for timing, control and other functions.
- \* The commonly used sinusoidal, square, triangular waveform generators are other forms of evolution in the design of operational amplifiers.
- \* It is capable of generating repetitive waveforms of fixed frequency and amplitude without the need of any other signal.

## SINE-WAVE GENERATORS:-

- \* The sine-wave is one of the most fundamental waveforms.
- \* The sine-wave oscillator using opamp the required phase shift of  $180^\circ$  in the feed back loop.
- \* It is a LC or RC combination.
 
## CONDITIONS FOR OSCILLATIONS:-

- \* oscillator is also called feedback amplifier.
- \* The part of output is fed back to the input with the use of a feedback circuit is called oscillator.



$$V_d = V_f + V_i$$

$$V_o = A_v V_d = A_v (V_f + V_i)$$

$$V_f = \beta V_o = \beta A_v (V_f + V_i)$$

$$V_o = A_v (\beta V_o + V_i); \quad V_o = A_v \beta V_o + A_v V_i;$$

$$V_o [1 - A_v \beta] = A_v V_i$$

$$\therefore \frac{V_o}{V_i} = \frac{AV}{1 - AVB}$$

$V_i = 0, V_o \neq 0$

$$|AVB| \geq 1$$


$$/ AVB = 0^\circ \text{ or } 360^\circ$$

Two basic requirements for sustained oscillations:

- The magnitude of the loop gain,  $AVB$ , must be unity
- The total phase-shift of the loop gain,  $AVB$ , must be equal to  $0^\circ$  or  $360^\circ$

Lc oscillators:-

 In Lc oscillator op-amp is considered.  $R_o \neq 0$



$$B = -\frac{V_f}{AV'f} \rightarrow ①$$

By voltage divide rule

$$V_f = \frac{Z_1}{Z_1 + Z_3} V_o \rightarrow ②$$

Also,

$$V_o = \frac{\pi}{\pi + R_o} V_f' A$$

$$\frac{1}{V_f' A} = \frac{\pi}{\pi + R_o} \frac{1}{V_o}$$

$$B = \frac{-V_f}{AVF'}$$

$$\begin{aligned} B &= \frac{Z_1}{Z_1 + Z_3} V_o \cdot \frac{\pi}{\pi + R_o} \frac{1}{V_o} \\ &= \frac{\pi_1 \pi}{(\pi_1 + \pi_3)(\pi + R_o)} \end{aligned}$$

→ When LC ckt is applied on Integrals

(2)

$$\beta \rightarrow j$$

$$\pi \rightarrow x$$

$$\beta = \frac{x_1 x_2}{j(R_0(\pi_1 + \pi_2 + \pi_3) + \pi_2(\pi_1 + \pi_3))}$$

$$\beta = \frac{x_1 x_2}{jR_0(x_1 + x_2 + x_3) + x_2(x_1 + x_3)}$$

When  $\beta'$  is calculated by  $\omega_0$

$$\beta = \frac{x_1}{x_2} \rightarrow ④$$

$$\beta(\omega_0) = \frac{x_1}{x_1 + x_3} \rightarrow ⑤$$

\*  $\beta(\omega_0)$  must be positive.

\*  $x_1$  &  $x_2$  have same sign.

\*  $x_1$  &  $x_2$  are capacitors &  $x_3$  are inductor

### HARTLEY OSCILLATOR:


→ The op amp is connected to operate in inverting mode.

Inductive

→  $x_1$  &  $x_2$  are capacitive reactance

→  $x_3$  is feedback network.

 → The phase shift through feedback network is  $180^\circ$ .



$$x_1 = j\omega L_1$$

$$x_2 = j\omega L_2$$

$$x_3 = \frac{1}{j\omega C}$$

$$x_3 = -j/\omega C$$

Angular frequency of oscillation


$$\omega_0 = \sqrt{\frac{1}{C(L_1 + L_2)}} \text{ and } \beta(\omega_0) = \frac{L_1}{L_2}.$$

$$\text{Frequency of oscillation } f_0 = \frac{1}{2\pi\sqrt{C L_T}}.$$

$$\text{where } L_T = L_1 + L_2. \text{ (or) } L_T = L_1 + L_2 + 2M$$

$M$  is the mutual inductance of coils  $L_1$  and  $L_2$ .  
Colpitts oscillator:

 - The feedback is connected to (-) terminal.
- The op-amp work as an Inverting Amplifier
- $X_1$  &  $X_2$  are capacitive reactance
- $X_3$  is Inductive element
- 180° phase shift.



$$X_1 = \frac{1}{j\omega C_1} = -j/\omega C_1$$

$$X_2 = \frac{1}{j\omega C_2} = -j/\omega C_2.$$

$$X_3 = j\omega L$$

Angular frequency of oscillation  $\omega_0$

$$\omega_0 = \sqrt{\frac{1}{L \left( \frac{C_1 C_2}{C_1 + C_2} \right)}}$$

$$\beta(\omega_0) = \frac{C_2}{C_1}$$

## Frequency of oscillation

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$CT = \frac{C_1 C_2}{C_1 + C_2}$$

(3)

The feedback factor  $\beta$  at the oscillation frequency is -1

## Rc OSCILLATORS:-


\* It operate well at high frequencies.

\* At low frequencies inductor and capacitors required for the timing circuit would be very bulky

(i) Rc phase shift oscillator

(ii) Wein bridge oscillator

## Rc phase shift oscillator:-

 

RC PHASE SHIFT OSCILLATOR.

\* op-amp is used in Inverting configuration.


\* It produces  $180^\circ$  phase-shift at the output.

\* The total phase shift around the loop is  $360^\circ$  or  $0^\circ$

\* gain of the amplifier is large and in series

Rc Network is exactly  $180^\circ$

# Derivation of frequency of oscillator:

 

$$V_o = V_f = I_3 R$$

Apply KVL in loop 1:

$$\frac{1}{j\omega C} I_1 + R [I_1 - I_2] = V_i$$

$$\left[ R + \frac{1}{j\omega C} \right] I_1 - I_2 R = V_i \rightarrow ①$$

Apply KVL in Loop 2:

$$\frac{1}{j\omega C} I_2 + R [I_2 - I_1] + R [I_2 - I_3] = 0$$

$$\frac{1}{j\omega C} I_2 + I_2 R - I_1 R + I_2 R - I_3 R = 0$$

$$-I_1 R + I_2 \left[ \frac{1}{j\omega C} + 2R \right] - I_3 R = 0 \rightarrow ②$$

Apply KVL in Loop 3:

$$\frac{1}{j\omega C} I_3 + R [I_3 - I_2] + R I_3 = 0$$

$$\frac{1}{j\omega C} I_3 + I_3 R - I_2 R + I_3 R = 0$$

$$-I_2 R + I_3 \left\{ \frac{1}{j\omega C} + 2R \right\} = 0 \rightarrow ③$$

Replace  $s = j\omega$  in eq ①, ② & ③

$$\left\{ R + \frac{1}{sc} \right\} I_1 - I_2 R = V_i \rightarrow ④$$

$$-I_1 R + I_2 \left\{ \frac{1}{sc} + 2R \right\} - I_3 R = 0 \rightarrow ⑤$$

$$-I_2 R + I_3 \left\{ \frac{1}{sc} + 2R \right\} = 0 \rightarrow ⑥$$

Matrix

$$\begin{bmatrix} R + \frac{1}{sc} & -R & 0 \\ -R & \frac{1}{sc} + 2R & -R \\ 0 & -R & \frac{1}{sc} + 2R \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_i \\ 0 \\ 0 \end{bmatrix}$$

$$\text{Output Voltage : } V_o = V_f = I_3 R$$

$$I_3 = \frac{A_3}{\Delta}$$

By Cramer's Rule,

$$\Delta = \begin{bmatrix} R + \frac{1}{sc} & -R & 0 \\ -R & \frac{1}{sc} + 2R & -R \\ 0 & -R & \frac{1}{sc} + 2R \end{bmatrix}$$

$$= \begin{bmatrix} \frac{1+SRC}{sc} & -R & 0 \\ -R & \frac{1+2SRC}{sc} & -R \\ 0 & -R & \frac{1+2SRC}{sc} \end{bmatrix}$$

$$\Delta = \frac{1+RSC}{SC} \left\{ \left( \frac{1+2SRC}{SC} \right)^2 - R^2 \right\} + R \left\{ (R) \left( \frac{1+2SRC}{SC} \right) - \right.$$

$$+ D \left\{ R^2 - D \right\}$$

$$= \frac{(1+SRC)(1+2SRC)^2}{(SC)^3} - R^2 \left( \frac{1+SRC}{SC} \right) - R^2 \left( \frac{1+2SRC}{SC} \right)$$

$$= \frac{(1+SRC)(1+2SRC)^2 - R^2(1+SRC)^2 - R^2(1+2SRC)(SC)^2}{(SC)^3}$$

$$= \frac{(1+SRC)(1+4S^2R^2C^2+4SRC) - R^2(SC)^2(1+SRC) - R^2(SC)^2(1+2SRC)}{(SC)^3}$$

$$= \frac{\cancel{(1+4S^2R^2C^2+4SRC+SRC+4S^3R^3C^3+4S^2R^2C^2-R^2S^2C^2)}}{\cancel{-R^3S^3C^3-R^2S^2C^2-2S^3R^3C^3}} \cdot S^3 C^3$$

$$\Delta = \frac{1+5SRC+6S^2R^2C^2+S^3R^3C^3}{S^3C^3} \rightarrow \textcircled{7}$$

$$\Delta_3 = \begin{bmatrix} \frac{1+SRC}{SC} & -R & V_i \\ -R & \frac{1+2SRC}{SC} & 0 \\ 0 & -R & 0 \end{bmatrix}$$

$$= \left( \frac{1+SRC}{SC} \right) \{0-0\} + R \{0-0\} + V_i \{R^2 - 0\}$$

$$\Delta_3 = 0 + 0 + V_i R^2$$

$$\Delta_3 = V_i R^2 \longrightarrow \textcircled{8}$$

The current flow in loop 3;

$$I_3 = \frac{\Delta_3}{\Delta}$$

$$I_3 = \frac{V_i R^2}{1 + 5SRC + bS^2R^2C^2 + S^3R^3C^3}$$

$$I_3 = \frac{V_i R^2 S^3 C^3}{1 + 5SRC + bS^2R^2C^2 + S^3R^3C^3} \longrightarrow \textcircled{9}$$

Output voltage  $V_o$ ,

$$V_o = V_f = I_3 R$$

$$\text{Sub } \textcircled{9} \quad V_o = \frac{V_i R^3 S^3 C^3}{1 + 5SRC + bS^2R^2C^2 + S^3R^3C^3}$$

$$\beta = \frac{V_o}{V_i} = \frac{S^3 R^3 C^3}{1 + 5SRC + bS^2R^2C^2 + S^3R^3C^3}$$

Replace  $S = j\omega$ ,

$$\beta = \frac{(j\omega)^3 R^3 C^3}{1 + 5(j\omega)RC + b(j\omega)^2 R^2 C^2 + (j\omega)^3 R^3 C^3}$$

$$\beta = \frac{-j\omega^3 R^3 C^2}{1 + 5j\omega RC - b\omega^2 R^2 C^2 - j\omega^3 R^3 C^3}$$

divide by  $-j\omega^3 R^3 C^3$  in Nr & Dr

$$\beta = \frac{1}{-\frac{1}{j\omega^3 R^3 C^3} + \frac{5j\omega RC}{-j\omega^3 R^3 C^3} - \frac{b\omega^2 R^2 C^2}{-j\omega^3 R^3 C^3} - \frac{j\omega^3 R^3 C^2}{-j\omega^3 R^3 C^3}}$$

$$= \frac{1}{-\frac{1}{j\omega^3 R^3 C^3} - \frac{5}{\omega^2 R^2 C^2} + \frac{b}{j\omega RC} + 1}$$

Assume,  $\alpha = \frac{1}{\omega RC}$

$$\beta = \frac{1}{+j\alpha^3 - 5\alpha^2 - jb\alpha + 1}$$

$$\beta = \frac{1}{(1-5\alpha^2) - j\alpha(b-\alpha^2)}$$

Imaginary part = 0

$$-j\alpha(b-\alpha^2) = 0$$

$$b-\alpha^2 = 0$$

$$\alpha^2 = b$$

$$\alpha = \sqrt{b}$$

$$\frac{1}{\omega RC} = \sqrt{b}$$

$$\frac{1}{2\pi FRC} = \sqrt{b}$$

$$f = \frac{1}{2\pi \sqrt{b} RC}$$

Real Part,

$$\beta = \frac{1}{1-5\alpha^2} = \frac{1}{1-5(\sqrt{b})^2}$$

$$\beta = \frac{1}{1-30} = \frac{1}{-29}$$

$$|\beta| = \frac{1}{29}$$

## Condition of oscillator

$$|AB| \geq 1$$

$$|A||B| \geq 1$$

$$|A| \left| \frac{1}{2^9} \right| \geq 1$$

$$|A| \geq 2^9$$

To make  $|A| \geq 2^9$ ,  $R_f = 2^9$  times of  $R$ .

### Advantages:

- \* circuit is simple to design.
- \* It produces sinusoidal o/p waveform.
- \* It is fixed frequency oscillator.

### Disadvantages:



- \* Frequency stability is poor.

# TIMER IC 555 and its modes of multivibrator

- \* 555 timer is a highly stable device for generating accurate time delay or oscillation.
- \* A single 555 timer can provide time delay ranging from microseconds to hours whereas counter timer can have a maximum timing range of days.
- \* It is designed to perform signal generation and specific timing.
- \* Voltage range: +5V to +18V
- \* Drive load: 200mA
- \* It is compatible with both TTL and CMOS logic circuits and op-amp based circuits.

## APPLICATIONS:

  1. oscillator
2. pulse generator
3. Ramp and square wave generator
4. Monoshot multivibrator
5. Burglar alarm
6. Traffic light control
7. Voltage monitor



PIN DIAGRAM  
OF IC 555

- \* The positive d.c. power supply terminal is connected to pins (V<sub>cc</sub>) and negative terminal is connected to pin 1 (GND).
- \* A control voltage input terminal accepts a modulation control input voltage applied externally.
- \* The (+) input terminal of the upper comparator is called threshold terminal.
- \* The (-) input terminal of the lower comparator is called trigger terminal.

### OPERATION:


- \* In Standby mode, the output Q of the control FF is HIGH. This makes the output low because of power amplifier which is basically an inverter.
- \* When a negative going trigger pulse is applied to pin 2 and should have its dc level greater than the threshold level of the lower comparator.
- \* At the negative going edge of the trigger, as the trigger passes through the output of the lower comparator goes HIGH and sets the control FF.

### MONOSTABLE MULTIVIBRATOR USING IC 555:

\* The Monostable multi vibrator has one stable state and one quasi-stable state.

\* It is also known as monostable (or) one-shot multivibrator.

\* It remains in its stable state until an impulse pulse triggers it into its quasi-stable state.

 

 


Fig.4.4 Timer in mono-stable operation with functional diagram

\* In the standby mode, control FF holds transistor Q<sub>1</sub> ON, thus clamping the external timing capacitor C to ground.

### ANALYSIS:

Voltage across the capacitor as given below:

$$V_C = V_{CC} \left(1 - e^{-t/RC}\right)$$

$$\text{At } t = T, \quad V_C = \frac{2}{3} V_{CC}$$

$$\frac{2}{3} V_{CC} = V_{CC} \left(1 - e^{-T/RC}\right)$$

$$\frac{2}{3} = 1 - e^{-T/RC}$$

$$\frac{2}{3} - 1 = -e^{-T/RC}$$

$$-\frac{1}{3} = -e^{-T/RC}$$

Taking natural log on both sides

$$\ln\left(\frac{1}{3}\right) = -\frac{T}{RC}$$


$$-T = RC \ln\left(\frac{1}{3}\right)$$

$$\boxed{T = 1.1 RC}$$


### APPLICATIONS MULTIVIBRATOR USING 555:

- (a) Pulse missing Detector
- (b) Frequency divider
- (c) PWM application


## MONOSTABLE USING IC 555:

 

## ASTABLE USING IC555:

 

## Astable using OP-Amp:

 

## ASTABLE MULTIVIBRATOR USING IC 555:

\* Comparing with monostable operation, the timing resistor is now split into two sections  $R_A$  and  $R_B$ .

\* The discharge (pin 7) terminal is connected to the junction of  $R_A$  and  $R_B$ .

\* Threshold (pin 6) and trigger (pin 2) terminals are connected to the  $V_C$  terminal and control (pin 5) terminal is bypassed to ground through  $0.01\mu F$  capacitor.

 


Fig.4.12 Astable multivibrator

 


Fig.4.13 Functional diagram of astable multivibrator using 555 timer

\* When the capacitor voltage reaches and rises above  $\frac{2}{3}V_{cc}$  the upper comparators triggers and reset the control flip flop so that  $\bar{Q}=1$ .

\*  $Q_1$  transistor  $\rightarrow$  ON

\* Capacitor starts discharging towards ground through  $R_B$  and transistor  $Q_1$  with the time constant  $R_B C$ .

\* During the discharge of timing capacitor as it reaches  $\frac{1}{3}V_{cc}$ , the lower comparators  $P_S$  triggered and this stage  $S=1, R=0$  which turns  $\bar{Q}=0$ .

\* The capacitor is charged and discharged between  $\frac{2}{3}V_{cc}$  and  $\frac{1}{3}V_{cc}$  respectively.

### ANALYSIS:

$$V_C = V_{cc} (1 - e^{-t/RC})$$

$$t = t_1, \quad V_C = \frac{2}{3} V_{cc}$$

$$\frac{2}{3} V_{cc} = V_{cc} (1 - e^{-t_1/RC})$$

$$\frac{2}{3} = 1 - e^{-t_1/RC}$$

$$\frac{2}{3} - 1 = -e^{-t_1/RC}$$

$$-\frac{1}{3} = -e^{-t_1/RC}$$

Taking natural log on both sides

$$\ln\left(\frac{1}{3}\right) = \frac{-t_1}{RC}$$

$$-t_1 = RC \ln\left(\frac{1}{3}\right)$$

$$t_1 = \boxed{1.1RC}$$

$$\text{At } t = t_2, V_C = \frac{1}{3} V_{CC}$$

$$\frac{1}{3} V_{CC} = V_C (1 - e^{-t_2/RC})$$

$$\frac{1}{3} - 1 = -e^{-t_2/RC}$$

$$\frac{-2}{3} = -e^{-t_2/RC}$$

Taking natural log on both sides

$$\ln\left(\frac{2}{3}\right) = -\frac{t_2}{RC}$$

$$-t_2 = RC \ln\left(\frac{2}{3}\right)$$

$$t_2 = 0.405 RC$$

$$t_{HIGH} = t_1 - t_2$$

$$= 1.1RC - 0.405RC$$

$$= RC(1.1 - 0.405)$$

$$t_{HIGH} = 0.69 RC$$

So for the given circuit

$$t_{HIGH} = 0.69 (R_A + R_B) C$$

$$t_{LOW} = 0.69 R_B C$$

$$T = t_{HIGH} + t_{LOW}$$

$$= 0.69 (R_A + R_B) C + 0.69 R_B C$$

$$= 0.69 R_A C + 0.69 R_B C + 0.69 R_B C$$

$$T = 0.69 (R_A + 2R_B) C$$

$$f = \frac{1}{T} = \frac{1.45}{(R_A + 2R_B)C}$$

The duty cycle D of the circuit is defined as the ratio of ON time to the total time period.

$$T = (t_{ON} + t_{OFF})$$

\* In this circuit, when the transistor Q<sub>1</sub> is on the output goes low.

$$D\% = \frac{t_{low}}{T} \times 100$$

$$D\% = \frac{R_B}{R_A + 2R_B} \times 100$$

### APPLICATIONS IN ASTABLE MODE:

- \* FSK Generator
- \* Timer as a Schmitt trigger.

## SQUARE WAVE GENERATORS:

\* Besides generating sine waves, the op-amp generates square wave form and pulses, an active device generate a square waveform is also called as multivibrator.


### (i) Astable multivibrator

\* It is also called as free running oscillator, the principle of generation of square wave output is to force an op-amp to operate in the saturation region.

$$\beta = \frac{R_2}{R_1 + R_2}$$

\* The output is also fed back to inverting terminal input after integrating by lowpass RC combination.

 \* Whenever the input at (-) input just exceeds  $V_{ref}$  switching takes place to  $+V_{sat}$  to  $-V_{sat}$ .



$$V_c(t) = V_f + (V_r - V_f) e^{-t/RC}$$

$$V_f = +V_{sat}$$

$$V_f = -\beta V_{sat}$$

Considering

$$V_c(t) = V_{sat} + (-\beta V_{sat} - V_{sat}) e^{-t/RC}$$

at  $t = T_1$

$$V_d(t) = -\beta V_{sat}$$

$$\beta V_{sat} = V_{sat} - (\beta V_{sat} + V_{sat}) e^{-T_1/RC}$$

$$\beta V_{sat} - V_{sat} = -V_{sat} (1 + \beta) e^{-T_1/RC}$$

$$V_{sat}(\beta - 1) = -V_{sat} (1 + \beta) e^{-T_1/RC}$$

$$V_{sat}(1 - \beta) = V_{sat} (1 + \beta) e^{-T_1/RC}$$

$$e^{-T_1/RC} = \frac{1 - \beta}{1 + \beta}$$

Taking log on both sides

$$\ln\left(\frac{-T_1}{RC}\right) = \ln\left(\frac{1 - \beta}{1 + \beta}\right)$$

Considering  $\beta = 0.5$


$$\frac{-T_1}{RC} = \ln\left(\frac{1 - 0.5}{1 + 0.5}\right)$$

$$\frac{-T_1}{RC} = \ln\left(\frac{0.5}{1.5}\right)$$

$$\frac{-T_1}{RC} = \ln\left(\frac{1}{3}\right)$$

$$\boxed{T_1 = 1'1 RC}$$

## (ii) MONOSTABLE MULTIVIBRATOR:

 

\* It has one stable state and one quasi-stable state.

\* This circuit is useful for generating single output pulse of adjustable time duration in response to a triggering signal.

\* The width of output signal depends only on external components connected to the op-amp.

\* Diode D1 clamps the capacitor voltage to  $0.7V$  when output  $V_o = V_{sat}$ .

\* A negative going pulse signal of magnitude  $V_t$ , passing through differentiator  $R_4 C_4$  and diode  $D_2$  produces going triggering impulse and  $V_o$  applied to the (+) input terminal.

$$V_o = V_f + (V_i - V_f) e^{-t/RC}$$

$$V_f = -V_{sat}$$

$$V_i = V_D$$

$$V_o = -V_{sat} + (V_D + V_{sat}) e^{-t/RC}$$

$$\text{At } t = T, V_o = -\beta V_{sat}$$

$$-\beta V_{sat} = -V_{sat}(V_D + V_{sat}) e^{-T/RC}$$

$$-\beta V_{sat} + V_{sat} = (V_D + V_{sat}) e^{-T/RC}$$

$$\frac{V_{sat}(1-\beta)}{V_D + V_{sat}} = e^{-T/RC}$$

$$\frac{V_{sat}(1-\beta)}{V_{sat}\left(1+\frac{V_D}{V_{sat}}\right)} = e^{-T/RC}$$

$$-\frac{T}{RC} = \ln \left( \frac{1 + \frac{V_D}{V_{sat}}}{1 - \beta} \right)$$

$$T = RC \ln (1 - \beta)$$

$$V_{sat} \gg V_D$$

$$R_1 = R_2$$


$$\beta = 0.5$$

$$T = 0.69 RC$$

\* Monostable multivibrator circuits are also referred as time delay circuit as it generates a fast transition at a predetermined time  $T$  after the application of input trigger.
 
## TRIANGULAR WAVE GENERATOR:

- \* Generally triangular wave generator may be derived from other sources through the use of comparators.
- \* Linear wave forms such as triangle and ramp may be derived from the charge/discharge action of a capacitor.



\* It basically consists of two level comparator followed by integrator circuit. The output of A<sub>1</sub> is a square wave of amplitude  $\pm V_{sat}$  and is applied to the (-) I/P of the integrator producing a triangular wave.

$$P = V_f + (V_i - V_f) \beta$$

$$V_f = -V_{ramp}$$

$$V_i = +V_{sat}$$

$$\beta = \frac{R_2}{R_2 + R_3}$$

$$P = -V_{ramp} + (V_{sat} + V_{ramp}) \frac{R_2}{R_2 + R_3}$$

At  $t = t_1$ , Voltage at P becomes equal to zero

$$-V_{ramp} = -\frac{R_2}{R_3} (+V_{sat}) \quad \text{--- (1)}$$

at  $t = t_2$ , when output of  $A_1$  switches from  $-V_{sat}$  to  $+V_{sat}$

$$V_{ramp} = -\frac{R_2}{R_3} (-V_{sat}) \quad \text{--- (2)}$$

peak to peak value of output is

$$V_o(PP) = +V_{ramp} - (-V_{ramp})$$

$$V_o(PP) = 2 \frac{R_2}{R_3} V_{sat} \quad \text{--- (3)}$$

The output from  $-V_{ramp}$  to  $+V_{ramp}$  in half the time period  $T/2$

$$V_o = \frac{1}{RC} \int_{t_1}^{t_2} V_i dt$$

$$V_o(PP) = \frac{1}{R_1 C_1} \int_0^{T/2} (-V_{sat}) dt$$

$$\Rightarrow \frac{V_{sat}}{R_1 C_1} \left( \frac{T}{2} \right)$$

$$T = 2 R_1 C_1 \frac{V_o(PP)}{V_{sat}} \quad \text{--- (4)}$$

Putting  $V_o(PP)$  value


$$T = 2 R_1 C_1 \frac{2 \frac{R_2}{R_3} V_{sat}}{V_{sat}}$$

$$= \frac{4 R_1 C_1 R_2}{R_3}$$

$$f_o = \frac{1}{T} = \frac{R_3}{4 R_1 C_1 R_2}$$
 
## ICL 8038 FUNCTION GENERATOR:

- \* Function generators are designed to provide the basic waveforms such as Square Wave, triangular wave and Sine wave.
- \* They are also called as waveform generators.
- \* The operation of ICL 8038 is based on charging and discharging of a grounded capacitor  $C$ , whose charging and discharging rates are controlled by programmable current generators  $I_A$  and  $I_B$  respectively.
- \* When switch is at position A, the capacitor charges at a rate determined by current source  $I_A$ .
- \* Once the capacitor voltage reaches the threshold value  $V_{LT}$  switch position to change from position A to B.



BLOCK DIAGRAM OF ICL 8038  
FUNCTION GENERATOR

## FREQUENCY OF OUTPUT WAVEFORM:

$$f_{out} = \frac{1}{T}$$

$$T = T_C + T_D$$

$$T_C = \Delta V_C \times \frac{1}{\text{Charging current}} \times C$$

$$T = \frac{V}{R}$$

$$T_C = \frac{V_{CC}}{3} \times \frac{R_A}{V_I} \times C$$

$$T_C = \frac{R_A C V_{CC}}{3 V_I}$$

The discharging time  $T_D$  can be given as

$$T_D = \Delta V \times \frac{1}{\text{discharging current}} \times C$$

$$= \frac{V_{CC}}{3} \times \frac{1}{\left( \frac{2V_I - V_i}{R_B} - \frac{V_i}{R_A} \right)} \times C$$

$$= \frac{V_{CC}}{3} \times \frac{1}{\frac{2V_i R_A - V_i R_B}{R_A R_B}} \times C$$

$$= \frac{V_{CC} \times R_A R_B \times C}{3 (2V_i R_A - V_i R_B)}$$

$$= \frac{V_{CC} \times R_A R_B \times C}{3 V_i (2R_A - R_B)}$$

$$\tau_d = \frac{C R_A V_{CC}}{3V_i} \left( \frac{R_B}{2R_A - R_B} \right)$$

$$T = T_c + \tau_d$$

$$= \frac{C R_A V_{CE}}{3V_i} + \frac{C R_A V_{CE}}{3V_i} \left( \frac{R_B}{2R_A - R_B} \right)$$

$$= \frac{C R_A V_{CC}}{3V_i} \left[ 1 + \frac{R_B}{2R_A - R_B} \right]$$

$$= \frac{C R_A V_{CC}}{3V_i} \left[ \frac{2R_A - R_B + R_B}{2R_A - R_B} \right]$$

$$T = \frac{R_A C V_{CC}}{3V_i} \left[ \frac{2R_A}{2R_A - R_B} \right]$$

$$f_{out} = \frac{1}{T}$$

$$= \frac{3V_i}{R_A C V_{CC}} \left( \frac{2R_A - R_B}{2R_A} \right)$$

Duty cycle is given as

$$\% d = \frac{T_c}{T_c + \tau_d} \times 100$$

$$= \frac{\frac{C R_A V_{CC}}{3V_I}}{\frac{C R_A V_{CC}}{3V_I} + \frac{C R_A V_{CC}}{3V_I} \left( \frac{R_B}{2R_A - R_B} \right)} \times 100$$

$$= \frac{\frac{C R_A V_{CC}}{3V_I}}{\frac{C R_A V_{CC}}{3V_I} \left( 1 + \frac{R_B}{2R_A - R_B} \right)}$$

$$= \frac{1}{\frac{2R_A - R_B + R_D}{2R_A - R_B}}$$

$$= \frac{2R_A - R_B}{2R_A} \times 100$$

$$\eta_{o, d} = \left( 1 - \frac{R_B}{2R_A} \right) \times 100$$

### Specifications:

Supply Voltage:  $\pm 18V$  or  $36V$

Power dissipation:  $750\text{ mW}$

Input Voltage: max of supply voltage level

Input Current:  $25\text{ mA}$

Output sink current:  $25\text{ mA}$



Storage temperature range:  $65^\circ C$  to  $125^\circ C$

Distortion:  $1\%$

Linenarity:  $0.1\%$

1	NC
13	NC
12	Sine adjust
11	VEE or GND
10	TPM <sup>ing</sup> capacitor
9	Squareout
8	AFMSweep out

## Saw-Tooth Wave Generator:

  

**Fig. 5.13 Saw-Tooth Wave Generator Circuit Diagram and output waveform**

The saw tooth wave oscillator which used the operational amplifier. The composition of this circuit is the same as the triangular wave oscillator basically and is using two operational amplifiers.

At the circuit diagram above, IC(1/2) is the Schmitt circuit and IC(2/2) is the Integration circuit. The difference with the triangular wave oscillator is to be changing the time of the charging and the discharging of the capacitor. When the

output of IC (1/2) is positive voltage, it charges rapidly by the small resistance (R1) value.

(When the integration output voltage falls) When the output of IC(1/2) is negative voltage, it is made to charge gradually at the big resistance(R2) value. The output waveform of the integration circuit becomes a form like the tooth of the saw. Such voltage is used for the control of the electron beam (the scanning line) of the television,

When picturing a picture at the cathode-ray tube, an electron beam is moved comparative slow. (When the electron beam moves from the left to the right on the screen). When turning back, it is rapidly moved.(When moving from the right to the left).

Like the triangular wave oscillator, the line voltage needs both of the positive power supply and the negative power supply. Also, to work in the oscillation, the condition of  $R_3 > R_4$  is necessary. However, when making the value of  $R_4$  small compared with  $R_3$ , the output voltage becomes small. The near value is good for  $R_3$  and  $R_4$

The oscillation frequency can be calculated by the following formula.

$$f = \frac{1}{2C(R_1+R_2)} \left( \frac{R_3}{R_4} \right)$$

With the circuit diagram,the oscillation frequency is as follows.

$$\begin{aligned} f &= (1/2C(R_1+R_2))*(R_3/R_4) \\ &= (1/(2 \times 0.1 \times 10^{-6} \times (5.6 \times 10^3 + 100 \times 10^3))) \times (120 \times 10^3 / 100 \times 10^3) \\ &= (1/(21.12 \times 10^{-3})) \times 1.2 \\ &= \textcolor{red}{56.8 \text{ Hz}} \end{aligned}$$

## IC 723 GENERAL PURPOSE REGULATOR:



\* In three terminal fixed Voltage regulators have the following limitations.

1. No short circuit protection
2. output voltage is fixed

\* The limitation have been overcome in the 723 general purpose regulators.

\* The zener diode, a constant current source and reference amplifier produce a fixed voltage of about 7 Volts at the terminal  $V_{ref}$ .

  \* The constant current source forces the zener to operate at a fixed point so that the zener outputs a fixed voltage.




- \* The power transistor  $Q_1$  is in series with unregulated power supply  $V_{in}$  and regulated output voltage  $V_o$ .  
\* so it must absorb the difference between these two voltages whenever any fluctuation in output voltage  $V_o$  occurs.

- \* The transistor Q<sub>1</sub> is also connected as an emitter follower and therefore provides sufficient current gain to drive the load.
- \* The output voltage is sampled by R<sub>1</sub>-R<sub>2</sub> divider and fed back to the (-) input terminal of the op-amp error amplifier.
- \* This sampled voltage is compared with the V<sub>ref</sub>. The output V<sub>o</sub> of the error amplifier drives the series transistor Q<sub>1</sub>.
- \* If output voltage increases (i.e. due to variation in load current), the sampled voltage β V<sub>o</sub> also increases.

$$\beta = \frac{R_2}{R_1 + R_2}$$

 - \* In turn reduces output voltage V<sub>o</sub> of diff-ential amplifier due to 180° phase difference provided by op-amp. V<sub>o</sub> is applied to base of Q<sub>1</sub> which is used as an emitter follower.



#### PIN DETAIL OF IC723

A Voltage regulator is an electronic circuit that provides a dc voltage independent of load current, temperature and ac line voltage.

The circuit consist of 4 parts

1. Reference voltage circuit
2. Error amplifier
3. Series pass transistor
4. Feedback network


 


FIG: SERIES REGULATOR

### MODES OF IC 723 REGULATOR

 

LOW POWER REGULATOR USING IC723

\* A simple positive low voltage regulator (2V to 7V).

\* The Voltage at NI terminal of the error amplifier - after due to  $R_1, R_2$  divider is

$$V_{NI} = V_{ref} = \frac{R_2}{R_1 + R_2}$$


\* The difference between  $V_{NI}$  and output Voltage  $V_o$  which is directly fed back to the INV terminal is amplified by the error amplifier

$$V_o = V_{ref} \frac{R_2}{R_1 + R_2}$$

The reference voltage is typically 7.15 V. So the output voltage  $V_o$  is

$$V_o = 7.15 \times \frac{R_2}{R_1 + R_2}$$

### HIGH VOLTAGE REGULATOR USING IC 723

 

\* The circuit produce regulator output voltage greater than 7V. The NI terminal connects directly to  $V_{ref}$  through  $R_3$ .

$$Av = 1 + \frac{R_1}{R_2}$$

$$V_o = V_{ref} \left( 1 + \frac{R_1}{R_2} \right)$$

$$V_o = 7.15 \left( 1 + \frac{R_1}{R_2} \right)$$

## AUDIO POWER AMPLIFIER:-

\* The amplifier receives an input from a signal source or from a transducer and gives out an amplified signal to the output device.

\* Small signal amplifiers are generally voltage amplifiers.

Features of an Audio power Amplifier:-

(i) Low power audio amplifier - 0 to 50 mW

(ii) Medium power audio amplifier - 50 mW to 500 mW

(iii) High power audio power amplifier - More than 500 MW

The design of heat sink for the IC determines the amount of power deliverable by an amplifier.

The power conversion Efficiency of the amplifier is defined as  $\eta = \frac{P_{ac}}{P_{dc}}$  where  $P_{ac}$  is the ac output power at the load and  $P_{dc}$  is the dc input supplied to the Amplifier by the dc input supply.

Classification and operation of power Amplifiers:-

The operating point of the transistor circuit is fixed by selecting proper biasing

Based on the position of the Q-point on the load line, some classifications of the power amplifiers are,

- (i) Class A power Amplifier
- (ii) Class B Power Amplifier
- (iii) Class AB power Amplifier

### LM380 Audio power Amplifier:

#### Features:-

- 1) It operates with low quiescent power drain
- 2) It has low distortion
- 3) It can operate at temperature of 0°C to 70°C
- 4) It can deliver high peak current of 1.3 A

Maximum.

- 5) Voltage gain of 34dB can be achieved.

#### CIRCUIT DESCRIPTION OF LM380:-

It consists of four stages, namely

- (i) PNP Emitter follower
- (ii) Differential amplifier
- (iii) Common emitter Amplifier and
- (iv) Quasi-complementary emitter follower

\* The Transistor Q<sub>1</sub> and Q<sub>2</sub> is PNP emitter follower input stage.


\* Its output drives the Q<sub>3</sub>-Q<sub>4</sub> pnp differential pair.

\* The Q<sub>5</sub> and Q<sub>6</sub> act as collector loads for Q<sub>3</sub>-Q<sub>4</sub>.

\* Q<sub>7</sub> and Q<sub>8</sub> establishes the collector current of Q<sub>9</sub>.

\* Q<sub>9</sub> forms the common-emitter amplifier stage.

 \* D<sub>1</sub>, D<sub>2</sub> & Q<sub>8</sub> act as an active current source load.



The capacitor  $C$  is connected to  $Q_9$  to provide Internal compensation.

This enables upper cut off frequency of 100 KHz at 2W for 8 loads.

The output stage is a Quasi-complementary pair emitter follower stage.

A dc feedback is introduced to the emitter of  $Q_4$  through Resistor  $R_5$ .

This stabilises the output.

$$I_3 = \frac{V - V_{EB1} - V_{EB3} - V_{EB1}}{R_3} \approx \frac{V - 3V_{EB}}{R_3}$$

(11)

$I_4$  of Transistor Q<sub>1</sub>

$$I_4 = \frac{V_o - V_{EB4} - V_{EB2}}{R_5} \approx \frac{V_o - 2V_{EB}}{R_5}$$

Equate  $I_3$  &  $I_4$  and Assume  $R_3 = 2R_5$ .

$$V_o = \frac{1}{2}V + \frac{1}{2}V_{EB}$$

$$\frac{V_i}{R_4} + \frac{V_o}{R_5} + \frac{V_i}{R_4} = 0$$

$$\therefore \frac{V_o}{V_i} = 2 \frac{R_5}{R_4} = -2 \frac{25 \times 10^3}{1 \times 10^3} = -50$$

Thus the overall <sup>Internal</sup> gain of the amplifier is 50.

Applications:-

- 1) Audio power Amplifier
- 2) High gain audio amplifier
- 3) Intercom connections
- 4) Bridge amplifier

### VIDEO AMPLIFIER:-

\* The video or wideband amplifiers are designed to provide a relatively flat gain versus frequency response characteristics for the range of frequencies required to transmit Video Information.


\* The frequency Range upto several MHz.

\* The TV required Bandwidth of 4 to 6 MHz

\* The op-amp is normally operated in a closed loop configuration.


### TYPE 733 VIDEO AMPLIFIER

It is a two - stage, differential Input,

 

\*  $Q_{10}$  &  $Q_{11}$  act as current sink bias for the emitter followers.

 \* The Resistors  $R_{11}$  &  $R_{12}$  provide negative feedback from the output terminals to balance i/p Terminals.




The use of Internal series-shunt feedback gives wide bandwidth with low phase distortion and high gain stability.

 (13)

Features:-


- \* It has a wide bandwidth of 180 MHz
- \* It offers an input resistance of  $250\text{ k}\Omega$
- \* Gain of 10, 100 and 400 are selectable
- \* External frequency compensation is not required
- \* It provides high common mode rejection ratio at high frequencies.



Internal circuit diagram and operation:-


- \* The internal circuit diagram of Type T33 monolithic video amplifier.
- \* It consists of two cascaded BJT differential amplifiers and a balanced emitter follower stage.
- \* The input stage consists of  $\alpha_1, \alpha_2$  and load resistance  $R_L$  and  $R_o$ .
- \* Resistor  $R_3$  through  $R_6$  provide the negative feedback path within the first stage.
- \* Resistor  $R_9$  &  $R_{10}$  act as load resistors.

# TYPE 3040 Video Amplifier:

 

The monolithic video amplifier IC 3040 from RCA uses a differential cascode configuration in the input stage. The input stage is formed by CC/CE compound connection of transistors Q<sub>1</sub>, Q<sub>2</sub> and Q<sub>3</sub> operated in CE, CC and CB configuration respectively. Q<sub>4</sub>, Q<sub>5</sub>, Q<sub>6</sub> are connected to a symmetrical configuration. Q<sub>7</sub>, Q<sub>8</sub> provide a low impedance differential output from the circuit. Q<sub>9</sub> provide current sink biasing for the differential circuit. R<sub>3</sub> and R<sub>4</sub> act as load resistors. The R<sub>5</sub> and R<sub>6</sub> bias the emitter followers transistor Q<sub>7</sub> and Q<sub>8</sub>. The diodes D<sub>1</sub> and D<sub>2</sub> with the resistor R<sub>10</sub> provide a dc bias voltage for the transistors Q<sub>2</sub>, Q<sub>3</sub>, Q<sub>5</sub> and Q<sub>6</sub>. The Q<sub>9</sub> is applied by the voltage divider using the resistor R<sub>1</sub> and R<sub>8</sub>.

## OPTO COUPLERS:

 

(D)

An opto coupler is a solid state component in which light emitter, the light path and the light detector are all enclosed within the component.

As the opto-coupler provides electrical isolation between two circuits, it is also called an opto-isolator.

An opto-isolator allows signal transfer without the use of coupling wires, capacitors or transformers.

It can couple digital or analog circuits to signals.

Opto coupler also called opto-electronic coupler.

It consists of Infrared LED and photo detector.

The opto isolator Transduce or Light Intensity

by using LEDs.


GaAs used to Spectral matching with the Silicon sensors.

It varies with temperature 25 to 45°C.

The switching time of opto-isolator decreases with increased current.

The light emitted from LED depends on the signal V.

It is proportional to input voltage.

 

16

Characteristics of opto-couplers :-

Collector-emitter voltage :-

Maximum voltage that can be applied across collector and emitter receiving phototransistors before it may break down.

Creepage distance :-

It is physical Measure. If the packages contaminate on it solder flux, or dampness will be created for noise signal to travel along the surface.

Forward current :-

This is the current passing through the transmitting LED.

Forward voltage :-

Voltage that is drop across LED when it is turn ON by the input signal  $V_i$ .

Collector dark current :-

current that can flow through the output photo Transistor when it is turned OFF.

Collector-Emitter saturation voltage :-

Voltage available between the collector and emitter when transistor in O/p is turn ON

Isolation Resistance :-

This is the Resistance from a pin on the Input side to the output side.

Response time:-

The rise and fall times duration that the o/p voltage requires to rise from zero to maximum and to fall from maximum to zero respectively

Cut off frequency:-

This is effectively the highest frequency of square-wave that can be applied to the opto-isolator.

Current Transfer Ratio:-

The input current is the forward current of LED that generates the emission of light, which is detected by photo diode, photo Darlington or photo SCR to produce the output current.

The ratio of output current  $I_o$  to the input current  $I_i$  is called the current Transfer Ratio.

OPTO-coupler ICs:-

The opto-coupler ICs are available in a variety of packages.

It is six-pin mini DIP.

OPTO coupler:-

The Type TLP112 from Toshiba is a mini-flat Coupler, suitable for surface mount assembly.

It consists of

- (i) GaAlAs light emitting diode
- (ii) high speed detector
- (iii) single chip photodiode - Transistor.

## Features:-

- (i) An isolation voltage of 2500 V rms can be achieved.
- (ii) switching speeds of  $t_{PHL} = 0.8 \mu s$ ,  $t_{PDL} = 2 \mu s$  (max) is possible.
- (iii) It is TTL compatible.

## MOC3009 - MDC3012 series opto-couplers :-

- \* It consists of Gallium Arsenide - Diode Infrared source.
- \* optically coupled silicon Triac driver.

## APPLICATIONS:-

- \* Solenoid / valve controls
- \* Lamp ballasts
- \* Interfacing microprocessors
- \* Motor controls
- \* Incandescent lamp dimmers.

## TLPI41G1 opto-coupler:-

- It is suitable for surface mount assembly.
- It consists of photo-Thyristor

## Features :-

- (i) peak off-state voltage : 400 V (min)
- (ii) Trigger LED current : 10 mA (Max)
- (iii) on-state current : 150 mA (max) and
- (iv) Isolation voltage : 2500 Vrms (min).

## Applications:-

- \* Programmable controllers
- \* Output Module
- \* Solid state relay

- a) They are compact and portable.
- b) Easy Interfacing With logic devices is possible
- c) They are more efficient than Isolation Transformers and relays
- d) The problems such as noise, transients and contact bounce etc.. are completely eliminated.

### ISOLATION AMPLIFIER:

The isolation amplifier is an amplifier in which there is no physical contact between the input and output sections. These amplifiers are used in applications requiring large common mode voltage difference between the input and the output sections. Several thousands volts can exists between the two sections.

They used in medical instrumentation applications where the patients must be isolated and protected from the leakage currents. They are hybrid ICs and consists of an input amplifiers, a GaAs light emitting diode (LED), a silicon photo diode and an output amplifier.

It is linearity of input-output characteristics. Typical isolation amplifier chips are 180100, 3450 - 3455 series from Burr Brown and AD293 and AD294 from Analog devices.

## IC 180100 ISOLATION AMPLIFIER:

The IC 180100 is an optically coupled isolation amplifier. It offers high accuracy, linearity and good stability against time and temperature. It needs careful directional matching of optical components.

The main features of the isolation amplifier 180100 are, as follows:

Supply voltage:  $\pm 18V$

Isolation voltage: ac peak or dc  $750V$

Input current:  $\pm 1mA$

Storage temperature range:  $-40^{\circ}C$  to  $100^{\circ}C$


Soldering lead temperature:  $+300^{\circ}C$

Output short circuit duration: continuous to ground

Leakage:  $0.3\mu A$  (max) at  $240V / 60Hz$

Bandwidth: 60 KHz

18 pin DIP package.

 

The 180100 has several modes of operations namely  
 Unipolar or bipolar, voltage or current input and inverting or  
 non inverting. It can be considered as high unity gain current  
 amplifier. Its output flows into a current to voltage converter.  
 The isolation barrier exists between the input and output.  
 The current at input device is replicated as  $I_{out}$  at  
 output side of the device. The  $I_{out}$  is forced to flow through  
 RF. The non-inverting input of the IC 180100 to the inverting  
 input of op-amp A<sub>1</sub>.

The transfer function of the IC 180100 is given by

$$\frac{V_{out}}{V_{in}} = \frac{RF}{1+AGE} \text{ where } AGE \text{ is the gain error.}$$

It is defined as the deviation of the ratio,  $\frac{I_{in}}{I_{out}}$  from  
 unity. It can thus be considered as the coupling error.

It consists of a matched pair of photo diodes and LED. The diode D<sub>1</sub> forms negative feedback path in LED. The diode D<sub>2</sub> receives the optical signal across the isolation barrier. The two matched current sources I<sub>REF1</sub> and I<sub>REF2</sub> are used for this purpose. connecting the current sources I<sub>REF1</sub> on the input side of the couplers and an equal current source I<sub>REF2</sub> on the output side.

The dc Error model used to represent 180100. The element I<sub>OS</sub> is called offset current. It is defined as the input current required for making the output voltage zero.

(22)

In Unipolar operation,  $I_{os}$  are mismatch. In bipolar operation the mismatch between  $I_{REF_1}$  and  $I_{REF_2}$ .  $I_{os}$  is sensitive to temperature, supply voltage, common mode voltage and iso mode voltage.  $I_{D_1}$  and  $I_{D_2}$  represents the current generated by the photo diode  $D_1$  and  $D_2$  respectively.


The two currents  $I_{D_1}$  and  $I_{D_2}$  are related as  $I_{D_2} = I_{D_1}(1 + A_{GE})$ . The transfer function for the voltage mode is

$$V_o = RF \left[ \left( \frac{V_{IN}}{R_{IN}} + \frac{V_{OS1}}{R_{IN}} - I_{REF_1} + I_{os} \right) (1 + A_{GE}) + I_{REF_2} \right] + V_{OS0}$$

The transfer function for the input current is

$$V_o = RF [I_{IN} - I_{REF_1} + I_{os}] (1 + A_{GE})$$

 It is noted that the power supply connections  $V_{P1}$ ,  $V_{N1}$ ,  $V_{P0}$  and  $V_{N0}$  to the input and output stages are isolated.



Pin configuration of 180100 ISO amplifier

## Applications:

The advantages of 180100 are its small size, low offset, low drift, wide bandwidth, ultra low leakage and low leakages.

The precautions are observed are as follows:

- \* Input common and IN lines at pins 17 and 18 must be grounded through separate lines. This is to avoid any large dc current flowing in input common feedback to signal input.
- \* The external capacitance across the isolation barrier is to be minimised.